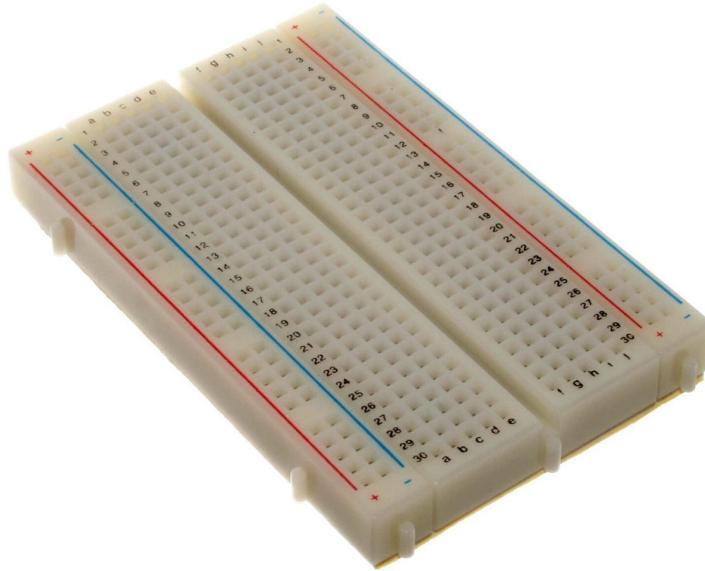


D.C. circuits

A-Level Physics

Practical circuits



A breadboard lets you build and test practical circuits without soldering.

Image: oomlout, CC BY-SA 2.0 (commons.wikimedia.org)

e.m.f. and p.d.


The **electromotive force** 电动势 (e.m.f.) ε of a source is the **energy** 能量 given to each unit of charge by the source as it drives the charge around a full circuit. Unit: volt.

The **potential difference** 电势差 (p.d.) across a component is the energy changed from electrical to other forms by each unit of charge as it passes through that component.

Both are in volts; they differ in energy direction:

- e.m.f. —energy put **into** the circuit by the source (chemical $\rightarrow$ electrical in a battery, mechanical $\rightarrow$ electrical in a generator).
- p.d. —energy taken **out** of the electrical form (electrical $\rightarrow$ thermal in a resistor, $\rightarrow$ light in a lamp, $\rightarrow$ kinetic in a motor).

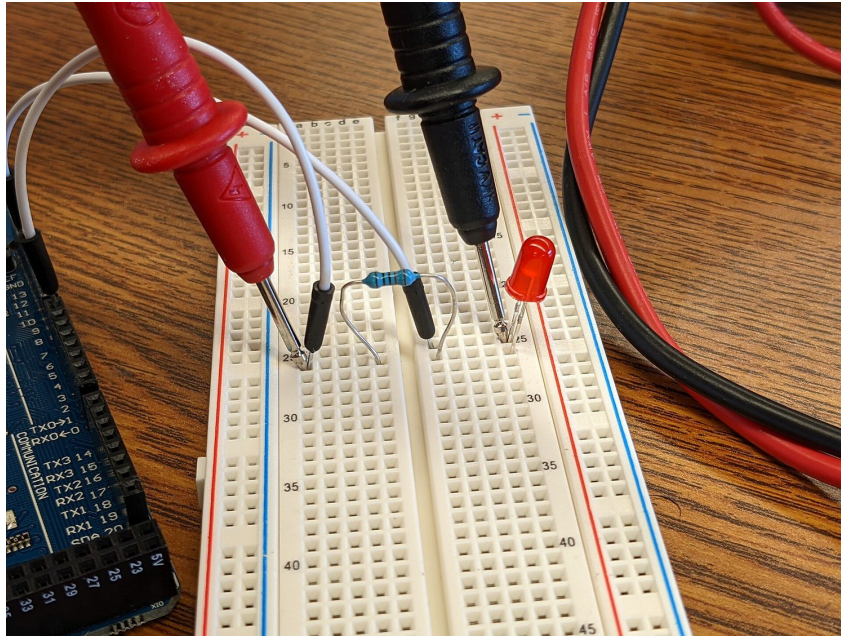In the lab you often build a circuit on a **breadboard** 面包板 (a board with rows of holes that connect components without soldering) and measure currents and p.d.s with a **multimeter** 万用表.



A real circuit on a breadboard, being measured with a multimeter

Image: Zeroping, CC BY 4.0 (commons.wikimedia.org)

Internal resistance

A real source has some **internal resistance** 内阻 r —usually the resistance of the **electrolyte** 电解质 in a **cell** 电池, or the wire windings in a generator. When current I flows, an internal p.d. of Ir is "lost" inside the source, so the **terminal p.d.** 端电压 across the outside circuit is

$$V_{\text{terminal}} = \varepsilon - Ir.$$

So:


- **no current (open circuit 开路, $I = 0$):** the terminal p.d. equals the e.m.f.
- **larger current:** the terminal p.d. falls.
- **short circuit 短路 ($R_{\text{external}} \rightarrow 0$):** $I = \varepsilon/r$, a large current, with all the energy turned to heat inside the source.

To measure r , change the outside resistance and plot V_{terminal} against I : the line has y -intercept ε and gradient $-r$.


Worked example. A cell of e.m.f. 1.5 V and internal resistance $0.50 \, \Omega$ is connected to a $2.5 \, \Omega$ resistor. Find the current and the terminal p.d.

The e.m.f. drives the current through both resistances: $I = \frac{\varepsilon}{R + r} = \frac{1.5}{2.5 + 0.50} = 0.50 \, \text{A}$.
Then
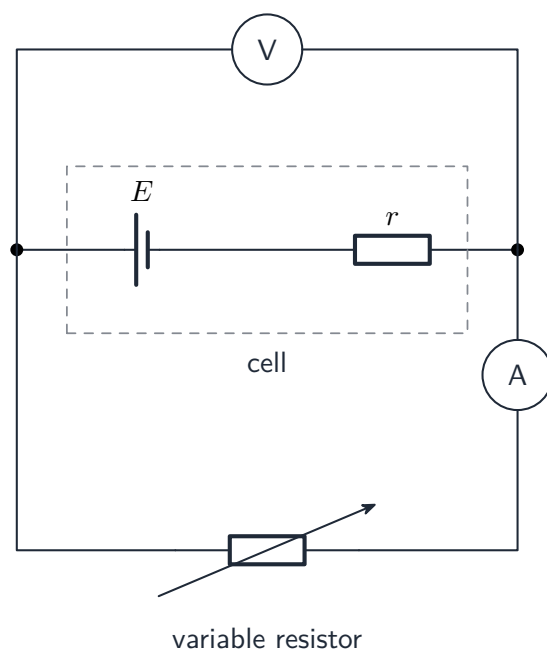
$$V_{\text{terminal}} = \varepsilon - Ir = 1.5 - 0.50 \times 0.50 = 1.25 \, \text{V}.$$



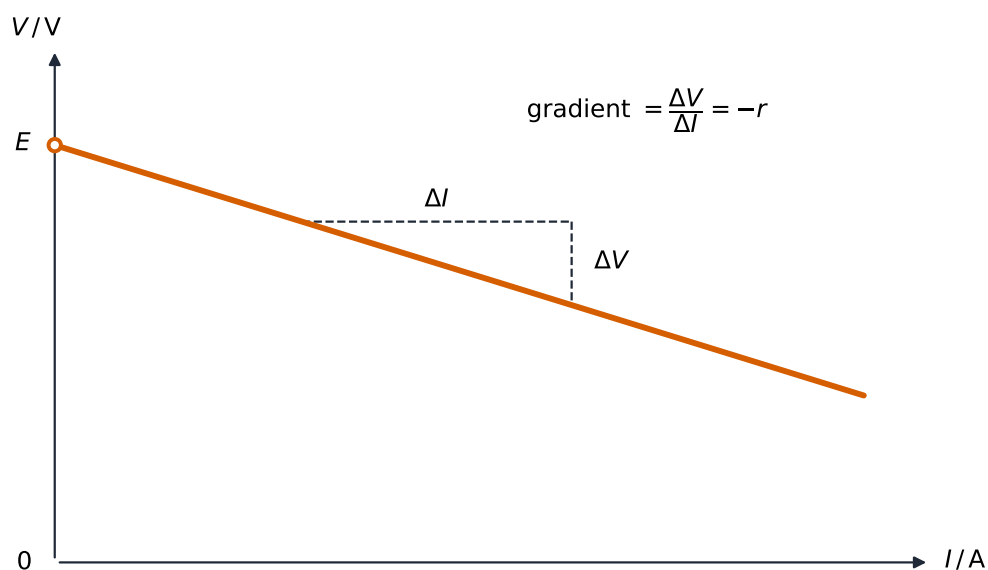Circuit for measuring the e.m.f. and internal resistance of a cell




Terminal p.d. against current — the intercept is the e.m.f. and the gradient is minus the internal resistance

The **power** 功率 given to the outside load is $P_{\text{ext}} = (\varepsilon - Ir)I$; the power lost inside is $P_{\text{int}} = I^2r$; the total power from the source is εI .

Circuit symbols

You must recognise and draw the standard symbols in the syllabus: cell, battery, switch, resistor, variable resistor, **ammeter** 电流表, **voltmeter** 电压表, lamp, **diode** (and **LED** 发光二极管), **capacitor** 电容器, inductor, thermistor, light-dependent resistor, **fuse** 保

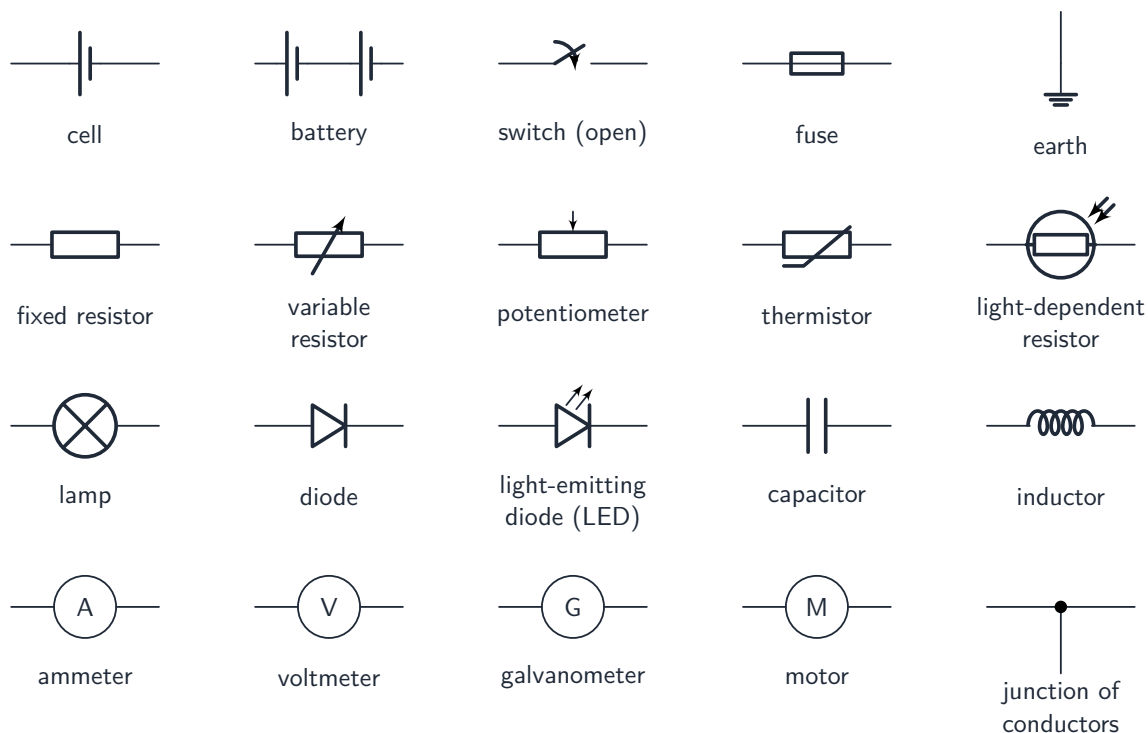保险丝, earth, junction. An ideal ammeter has zero **resistance** 电阻 and goes in **series** 串联. An ideal voltmeter has infinite resistance and goes in **parallel** 并联.




The standard circuit symbols you need to recognise and draw

Kirchhoff's laws

First law (junction rule)

At any **junction** 节点, the **total current flowing in equals the total current flowing out**. This follows from **conservation of charge** 电荷守恒—charge cannot build up at a point in a steady circuit, so charge in per second equals charge out per second.

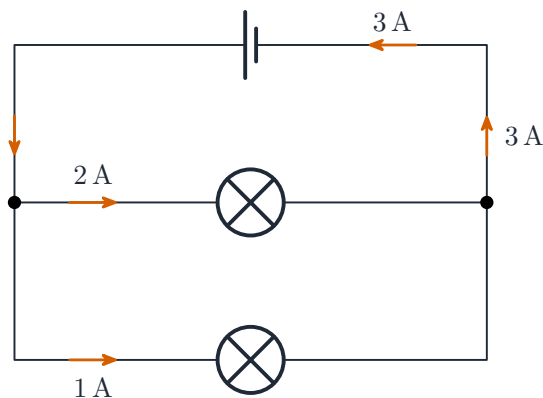For a junction with three wires: $I_1 = I_2 + I_3$ if currents 2 and 3 flow out and current 1 flows in.



at each junction: $3\text{ A} = 2\text{ A} + 1\text{ A}$

Current divides at a junction in a parallel circuit (3 A in equals 2 A plus 1 A)

Second law (loop rule)

Around any closed loop 回路, the total e.m.f. equals the total p.d. across the components in that loop. This follows from **conservation of energy** 能量守恒: as a unit of charge goes once round a loop, the energy it gains from sources equals the energy it gives up to components.


Pick a direction round the loop. Take an e.m.f. as positive when the loop direction goes from $-$ to $+$ of the source, and a p.d. as positive when the loop direction is the conventional current direction through the resistor.

Combining resistors

Resistors in series carry the same current; the total p.d. is the sum:

$$\varepsilon = IR_1 + IR_2 + \dots = I(R_1 + R_2 + \dots),$$

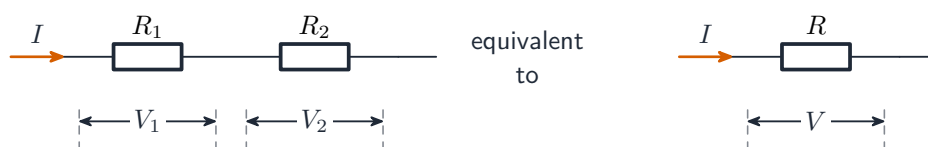so $R_{\text{series}} = R_1 + R_2 + \dots$




Two resistors in series and their single equivalent resistor

Resistors in parallel have the same p.d.; the total current is the sum:

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \dots = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots \right),$$

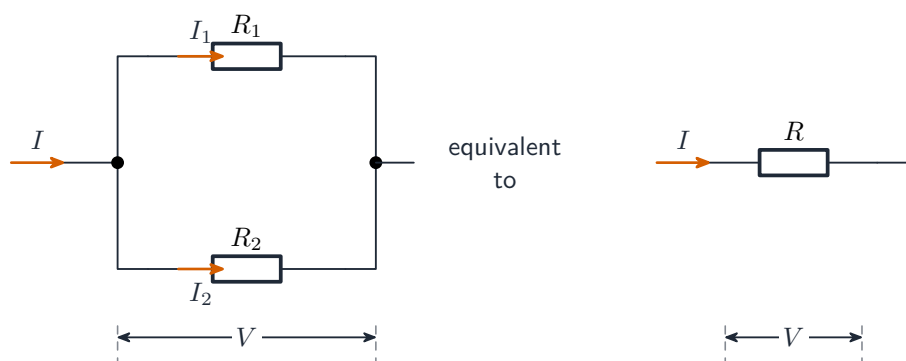so $\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$



Two resistors in parallel and their single equivalent resistor

Two equal resistors R in parallel give $R/2$; N equal ones give R/N . A parallel combination is **always smaller** than any of its resistors; a series combination is always larger.

Worked example. A $4.0\ \Omega$ resistor and a $12\ \Omega$ resistor are connected in parallel. Find their combined resistance.

$$\frac{1}{R} = \frac{1}{4.0} + \frac{1}{12} = \frac{3}{12} + \frac{1}{12} = \frac{4}{12} = \frac{1}{3} \quad \Rightarrow \quad R = 3.0\ \Omega.$$

Solving a circuit

1. **Label** every current with a symbol and a chosen direction.
2. Use **Kirchhoff's first law** 基尔霍夫第一定律 at each junction to link the currents.
3. Use **Kirchhoff's second law** 基尔霍夫第二定律 around each loop to get equations in the p.d.s.
4. Use $V = IR$ for each resistor.
5. Solve the equations together.

For symmetric resistor networks, use the symmetry to spot branches with equal currents—the branch with the most current gives the most power ($P = I^2 R$).

Potential dividers


A **potential divider** 分压器 is two (or more) resistors in series across a source. The p.d. across each resistor is in **direct proportion** to its resistance:

$$V_1 = V_{\text{in}} \cdot \frac{R_1}{R_1 + R_2}, \quad V_2 = V_{\text{in}} \cdot \frac{R_2}{R_1 + R_2}.$$

The output (tapped between R_1 and R_2) can be set to any **voltage** 电压 between 0 and V_{in} by choosing the resistances. A **rheostat** 变阻器 (a slider on a uniform-resistance wire) gives a smoothly variable divider.

Worked example. A 6.0 V supply is connected across a 2.0 kΩ resistor in series with a 4.0 kΩ resistor. Find the output voltage tapped across the 4.0 kΩ resistor.
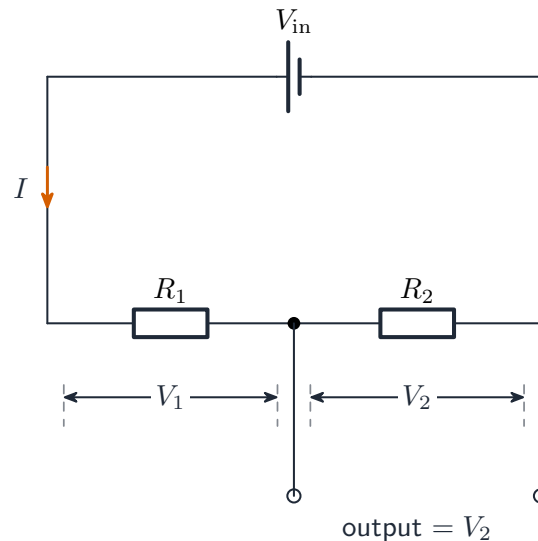
$$V_2 = V_{\text{in}} \cdot \frac{R_2}{R_1 + R_2} = 6.0 \times \frac{4.0}{2.0 + 4.0} = 4.0 \text{ V}.$$




A potential divider — the p.d. splits between R_1 and R_2 in proportion to their resistances

Sensor circuits

Replace one fixed resistor with a **sensor** 传感器 whose resistance changes with a physical quantity:

- **thermistor** 热敏电阻 (NTC): R falls as temperature rises. In a divider, the output voltage changes with temperature in a fixed direction.
- **light-dependent resistor** 光敏电阻 (LDR): R falls as **light intensity** 光强 rises, giving a brightness-dependent output.

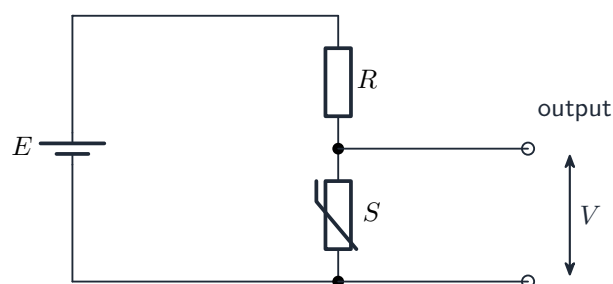Connect the output to a **transistor** 晶体管 base or a **comparator** 比较器 to switch a load on or off when the temperature or light passes a **threshold** 阈值.



A thermistor in a potential divider gives an output voltage that changes with temperature

Potentiometer and the null method


A **potentiometer** 电位差计 is a uniform resistance wire of length L_0 with a sliding contact (**jockey** 滑动触头). The resistance per unit length is uniform, so the p.d. from one end to the jockey is proportional to the length:

$$V_x = V_{\text{full}} \cdot \frac{x}{L_0}.$$

To **compare two e.m.f.s** (an unknown cell against a standard cell), connect each in turn with the jockey through a **galvanometer** 检流计. Slide the jockey until the galvanometer reads zero (a **null** —no current flows through the cell being measured, because the potentiometer's voltage there exactly opposes the cell's e.m.f.). The two balance lengths are in the ratio of the e.m.f.s:

$$\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2}.$$

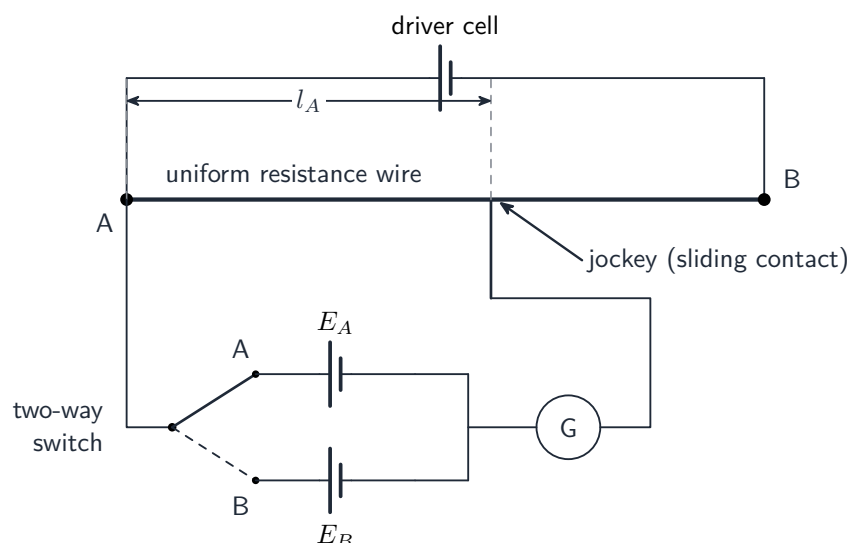This is a **null method** 零点法: you find the balance (zero current) instead of measuring a current's value. Its advantage is that at balance the unknown cell gives no current, so its internal resistance does not affect the result.



A potentiometer comparing two cell e.m.f.s by the null method

Exam tips

- Apply **Kirchhoff's laws**: current into a junction = current out (charge conserved); $\sum \text{e.m.f.} = \sum \text{p.d. round a loop}$ (energy conserved).
- Combine resistors: **series** $R = R_1 + R_2$; **parallel** $1/R = 1/R_1 + 1/R_2$.
- A **potential divider** splits voltage in the ratio of the resistances.
- Include **internal resistance**: $\text{e.m.f.} = I(R + r)$ —the "lost volts" are Ir .