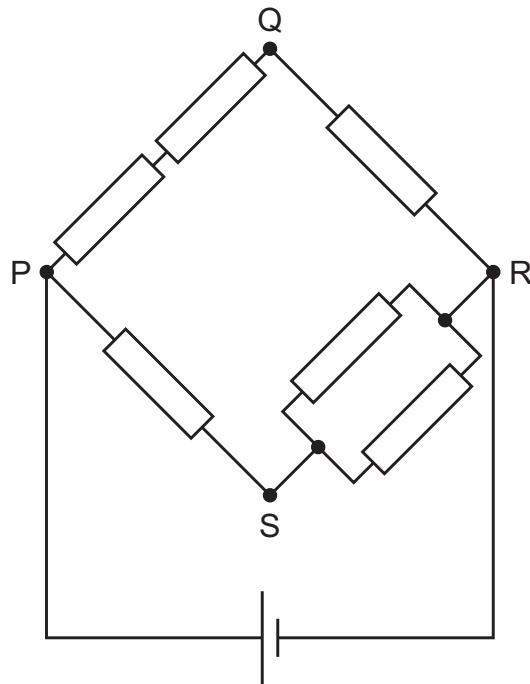


34 The diagram shows six identical resistors connected in a circuit.



In which branch of the circuit is the most power dissipated?

A PQ

B QR

C RS

D SP