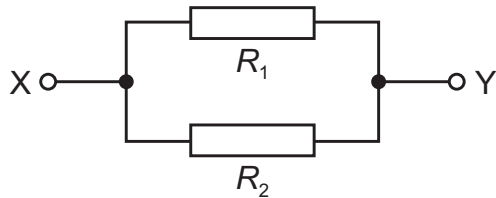


36 Two resistors of resistances R_1 and R_2 are connected in parallel.



What is the combined resistance between X and Y?

- A** $R_1 + R_2$ **B** $\frac{R_1 R_2}{R_1 + R_2}$ **C** $\frac{R_1 + R_2}{R_1 R_2}$ **D** $\frac{R_1}{R_2}$