

37 Each of Kirchhoff's two laws presumes that some quantity is conserved.

Which row states Kirchhoff's **first** law and names the quantity that is conserved?

	statement	quantity
A	The algebraic sum of currents at a junction is zero.	charge
B	The algebraic sum of currents at a junction is zero.	energy
C	The e.m.f. in a loop is equal to the algebraic sum of the product of current and resistance round the loop.	charge
D	The e.m.f. in a loop is equal to the algebraic sum of the product of current and resistance round the loop.	energy