

32 The current in a resistor of constant resistance is 8.0 mA. The power dissipated by the resistor is P .

The current in the resistor is increased to 12.0 mA.

What is the new power dissipated by the resistor?

A $0.44P$

B $0.67P$

C $1.5P$

D $2.3P$