

Exercise walk-through

3.2.1

**Drawing logic circuits,
three-input truth tables and
reading an expression back out**

A-Level Computer Science

You must be able to

- construct a **logic circuit** from a logic expression, from a problem statement, and from a truth table
- construct a **truth table** from a logic circuit, using a working column for each gate's output
- construct a **logic expression** from a truth table, from a circuit, and from a problem statement
- use **NAND**, **NOR** and **XOR** inside a larger circuit

1

The method

Method — From an expression to a circuit

Three rules, and they settle every drawing question:

- 1 **One gate per operator.** Count the operators in the expression and you know how many gates to draw.
- 2 **Innermost brackets first.** Whatever is inside a bracket is computed before it can be fed into the gate outside it, so it sits to the **left** in the drawing.
- 3 **A variable used twice is still one input.** Draw a single wire from that input and put a **junction dot** where it branches. Two separate wires labelled B is the drawing error the mark scheme looks for.

Worked example. Draw the circuit for $X = (A \text{ AND } NOT\ B) \text{ OR } (B \text{ AND } C)$.

Four operators, so four gates: a NOT, two ANDs and an OR. B appears twice, so it is one input with a junction.

- **Label each gate's output** (P , Q) as you draw. It costs nothing and it is what makes the truth table below easy.

Method — From an expression to a circuit

Three rules, and they settle every drawing question: Worked example.

NAND



NOR




XOR



The symbols for the NAND, NOR and XOR gates

Method — From an expression to a circuit

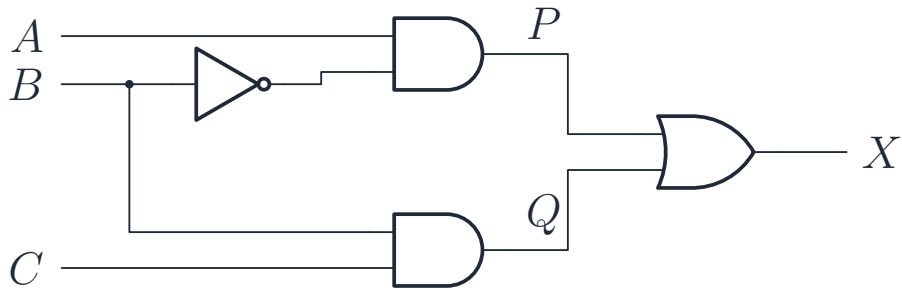Three rules, and they settle every drawing question: Worked example.



Method — A three-input truth table, with working columns

Three inputs means $2^3 = 8$ rows. Write them by **counting up in binary** from 000 to 111 – that way none is missed and none repeats.

Then add one column per gate. Work left to right across the circuit, filling a whole column at a time rather than a whole row.

<i>A</i>	<i>B</i>	<i>C</i>	<i>P</i> = <i>A</i> AND NOT <i>B</i>	<i>Q</i> = <i>B</i> AND <i>C</i>	<i>X</i> = <i>P</i> OR <i>Q</i>
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	0	1	1

Method — A three-input truth table, with working columns

- The working columns are worth marks of their own when the question prints a **working space**. Fill it in: a wrong final column with correct working usually still earns something, and a right answer with nothing shown can earn nothing on a “show your working” question.

Method — From a truth table to an expression

Look only at the rows where $X = 1$. Each one becomes a term:

- write each input that is **1** as itself, and each input that is **0** as **NOT** that input,
- **AND** the three together,
- then **OR** all the terms from all the 1-rows.

Worked example. *A truth table gives $X = 1$ on the rows $ABC = 001, 010$ and 111 , and 0 everywhere else.*

$$X = (\text{NOT } A \text{ AND NOT } B \text{ AND } C) \text{ OR } (\text{NOT } A \text{ AND } B \text{ AND NOT } C) \text{ OR } (A \text{ AND } B \text{ AND } C)$$

- One term per 1-row, and every term carries **all three** inputs. Leaving one out changes the expression.
- Rows where $X = 0$ contribute nothing. Do not write terms for them.

Method — From a problem statement

Read the sentence and translate it piece by piece: each **condition** becomes an input, each **“and”** an AND gate, each **“or”** an OR gate, and each **“not”, “is off”** or **“is 0”** a NOT gate. Keep the order of the sentence, and bracket whatever the sentence groups together.

“A pump runs when the tank is not full and the switch is on” becomes $X = (\text{NOT } A) \text{ AND } B$, then one NOT gate feeding one AND gate.

2

Practice

Practice 2.1 ■ 3 marks

Draw the logic circuit for $X = (A \text{ OR } B) \text{ AND } (\text{NOT } C)$.

Solution 2.1

Method: From an expression to a circuit — p.4

Worked steps

- an OR gate with A and B as its inputs (B1)
- a NOT gate with C as its input (B1)
- both outputs feeding an AND gate, whose output is labelled X (B1)
- the OR and the NOT must both come **before** the AND: the brackets say so

Practice 2.2 ■ 3 marks

Complete the truth table for the circuit in 2.1. Use the working columns.

<i>A</i>	<i>B</i>	<i>C</i>	<i>A OR B</i>	NOT <i>C</i>	<i>X</i>
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Solution 2.2

Method: A three-input truth table, with working columns — p.7

Worked steps

- $A \text{ OR } B$ column correct: 0, 0, 1, 1, 1, 1, 1, 1 **B1**
- NOT C column correct: 1, 0, 1, 0, 1, 0, 1, 0 **B1**
- X column correct **B1**

Solution 2.2

<i>A</i>	<i>B</i>	<i>C</i>	<i>A OR B</i>	<i>NOT C</i>	<i>X</i>
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	0

Solution 2.2

- $X = 1$ only when $C = 0$ and at least one of A, B is 1

Practice 2.3 ■ 2 marks

Name the **single** gate that does the same job as each of these.

Practice 2.3 (a)

NOT (A AND B)

Solution 2.3 (a)

Method: From an expression to a circuit — p.4

Worked steps

NAND **B1**

Practice 2.3 (b)

NOT (A OR B)

Solution 2.3 (b)

Worked steps

NOR **B1**

Practice 2.4 ■ 2 marks

A truth table gives $X = 1$ on the rows $ABC = 001$ and 110 , and $X = 0$ on every other row.
Write the logic expression for X .

Solution 2.4

Method: From a truth table to an expression — p.9

Worked steps

- row 001 gives NOT A AND NOT B AND C ; row 110 gives A AND B AND NOT C **M1**
- $X = (\text{NOT } A \text{ AND NOT } B \text{ AND } C) \text{ OR } (A \text{ AND } B \text{ AND NOT } C)$ **A1**

Practice 2.5 ■ 1 mark

A circuit uses input B as an input to two different gates. State how this is shown on the circuit diagram.

Solution 2.5

Worked steps

- the wire from B **branches**, with a **junction dot** drawn at the branch point; B is still a single input **B1**

3

Exam-style

Exam-style 3.1 ■ 5 marks

A chemical tank has three sensors. An alarm X sounds when the temperature sensor A reads 1 **and** the pressure sensor B reads 0, **or** when the manual override C reads 1.

Exam-style 3.1 (a) ■ 2 marks

Write the logic expression for X .

Solution 3.1 (a)

Method: From an expression to a circuit — p.4

Worked steps

“ A reads 1 and B reads 0” is $A \text{ AND NOT } B$ **B1**

- “or C reads 1” adds an OR with C : $X = (A \text{ AND NOT } B) \text{ OR } C$ **B1**

Exam-style 3.1 (b) ■ 3 marks

Draw the logic circuit for X .


Solution 3.1 (b)

Worked steps

- a NOT gate with B as its input (B1)
- an AND gate taking A and the NOT gate's output (B1)
- an OR gate taking that AND output and C directly, giving X (B1)
- C goes straight into the OR gate: nothing in the sentence acts on it first

Exam-style 3.2 ■ 6 marks

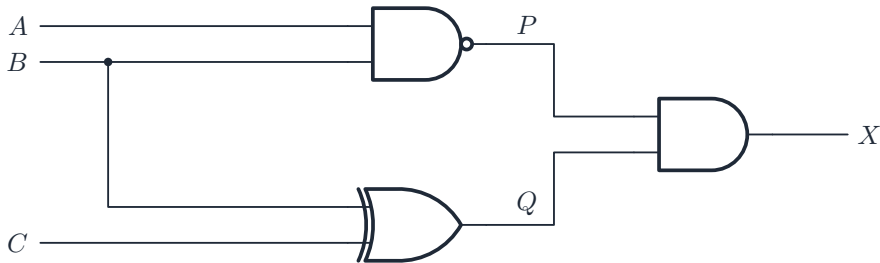A logic circuit is shown. P and Q are the outputs of the first two gates.




Exam-style 3.2 (a) ■ 4 marks

Complete the truth table, filling the working columns P and Q .

A	B	C	P	Q	X
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Exam-style 3.2 (a) ■ 4 marks

Complete the truth table, filling the working columns ... and

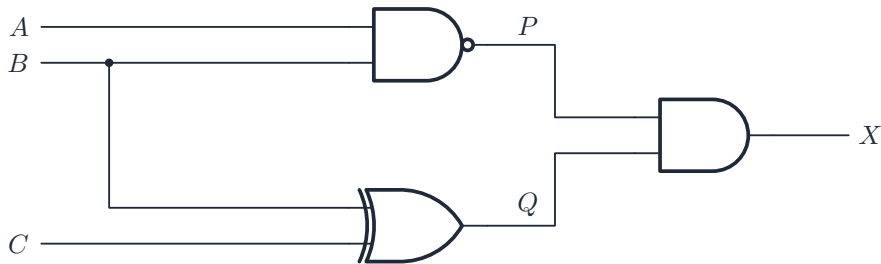

Solution 3.2 (a)

Method: From an expression to a circuit — p.4

Worked steps

P column correct – P is NOT (A AND B), so it is 1 everywhere except the last two rows **B1**


- Q column correct – Q is 1 when B and C **differ** **B1**
- X column correct, $X = P$ AND Q **B1** **B1**

Solution 3.2 (a)

A	B	C	P	Q	X
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	0	0

Exam-style 3.2 (b) ■ 2 marks

State the values of A , B and C for which $X = 1$.

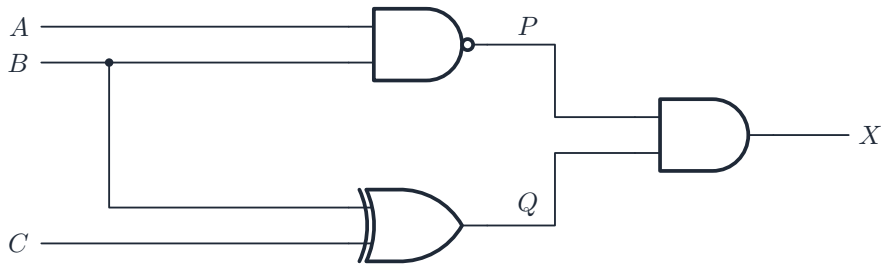

Solution 3.2 (b)

Worked steps

$X = 1$ on $ABC = 001, 010$ and 101 **B1**

- in words: B and C must differ, and A and B must not both be 1 **B1**

Exam-style 3.3 ■ 3 marks

A truth table gives $X = 1$ on the rows $ABC = 000, 011$ and 110 , and $X = 0$ on every other row.
Write the logic expression for X .

Solution 3.3

Method: From a truth table to an expression — p.9

Worked steps

- row 000: NOT A AND NOT B AND NOT C (B1)
- row 011: NOT A AND B AND C (B1)
- row 110: A AND B AND NOT C , and the three ORed together (B1)

$X = (\text{NOT } A \text{ AND NOT } B \text{ AND NOT } C) \text{ OR } (\text{NOT } A \text{ AND } B \text{ AND } C) \text{ OR } (A \text{ AND } B \text{ AND NOT } C)$

Exam-style 3.4 ■ 3 marks

Draw the logic circuit for $X = (A \text{ XOR } B) \text{ AND } (\text{NOT } C)$.

Solution 3.4

Method: From an expression to a circuit — p.4

Worked steps

- an XOR gate with A and B as its inputs (B1)
- a NOT gate with C as its input (B1)
- both feeding an AND gate whose output is X (B1)
- the XOR symbol is the OR shape with a **second curved line** across its back; drawing a plain OR loses the first mark

Exam-style 3.5 ■ 3 marks

A student is asked to draw the circuit for $X = A \text{ AND } (B \text{ OR } C)$, but wires it as $(A \text{ AND } B) \text{ OR } C$.

Explain, naming **one** row of the truth table, how the two circuits behave differently.

Solution 3.5

Method: From an expression to a circuit — p.4

Worked steps

- the brackets change which gate comes first: $A \text{ AND } (B \text{ OR } C)$ ORs B and C **before** the AND, while $(A \text{ AND } B) \text{ OR } C$ ANDs first and lets C reach the output on its own (B1)
- so in the second circuit $C = 1$ forces $X = 1$ whatever A is, which the first circuit does not do (B1)
- any row with $A = 0$ and $C = 1$ shows it, for example $A = 0, B = 0, C = 1$: the correct circuit gives $X = 0$ and the student's gives $X = 1$ (B1)
- $A = 0, B = 1, C = 1$ is also accepted; a row where the two agree proves nothing