

# 15.2.1 The full adder, flip-flops drawn and traced, and four-variable Karnaugh maps

Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

Total: 30 marks

**KEY WORDS** boolean 布尔 • karnaugh map 卡诺图 • boolean algebra 布尔代数  
 • flip-flop 触发器 • de morgan's laws 德摩根定律

## Objective

Build the skills to answer the **Boolean algebra** 布尔代数 questions at the depth Paper 3 sets them. Sheet 15.2 touches all four statements: it simplifies a two-variable expression, reads a **K-map** group, completes a **half adder** and asks for one difference between the flip-flops. This sheet is the harder half of the same four: the **full adder** 全加器, **drawing** an **SR** and a **JK flip-flop** 触发器 and deriving its truth table, and a **four-variable** K-map where the groups **wrap round the edges**.


**You must be able to:**

- produce truth tables for logic circuits including half adders and **full adders**, with gates of more than two inputs
- **draw a logic circuit** for an SR and a JK flip-flop and **derive its truth table**, and explain the role of a flip-flop as a data storage element
- perform Boolean algebra using **De Morgan's laws**, and simplify an expression or a circuit
- solve logic problems using **Karnaugh maps**, and state the benefits of using them

## 1 Worked examples

Study these first. Each one shows a **method** that a question later on this sheet needs.

### ■ The full adder

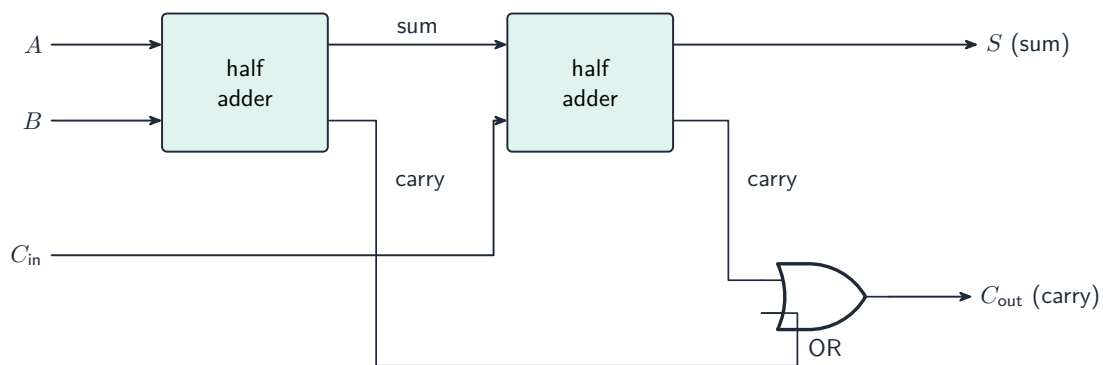


A **half adder** adds two bits and has no way to take a carry **in**, so it can only ever add the rightmost column. A **full adder** takes three inputs –  $A$ ,  $B$  and  $C_{in}$  – and is what every other column needs.

$$\text{Sum} = A \oplus B \oplus C_{in} \quad C_{out} = A \cdot B + C_{in} \cdot (A \oplus B)$$

| $A$ | $B$ | $C_{in}$ | Sum | $C_{out}$ |
|-----|-----|----------|-----|-----------|
| 0   | 0   | 0        | 0   | 0         |
| 0   | 0   | 1        | 1   | 0         |
| 0   | 1   | 0        | 1   | 0         |
| 0   | 1   | 1        | 0   | 1         |
| 1   | 0   | 0        | 1   | 0         |
| 1   | 0   | 1        | 0   | 1         |
| 1   | 1   | 0        | 0   | 1         |
| 1   | 1   | 1        | 1   | 1         |

- Read the Sum column: it is 1 on the rows with an **odd** number of 1s, which is what a chain of XORs does. The carry out is 1 whenever **at least two** inputs are 1.
- A full adder is built from **two half adders and an OR gate**. Saying so earns the structure mark when the question asks how one is constructed.
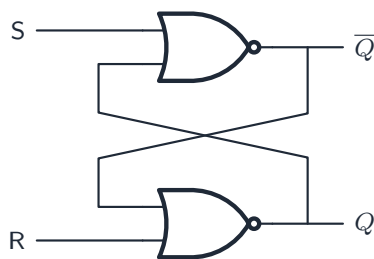
#### ■ Flip-flops: drawing them and deriving the table




two NOR gates, each output fed back to the other's input

| S | R | Q | $\bar{Q}$ | effect                   |
|---|---|---|-----------|--------------------------|
| 0 | 0 | Q | $\bar{Q}$ | hold: no change (memory) |
| 1 | 0 | 1 | 0         | set Q to 1               |
| 0 | 1 | 0 | 1         | reset Q to 0             |
| 1 | 1 | 0 | 0         | invalid: both outputs 0  |

An **SR flip-flop** is two **NOR** gates **cross-coupled**: the output of each is an input to the other. That feedback is what lets it hold a value with no input applied, which is why a flip-flop is a **data storage element** – one bit of it.

| S | R | Q | What it does                                                                         |
|---|---|---|--------------------------------------------------------------------------------------|
| 0 | 0 | Q | <b>hold</b> the previous value                                                       |
| 0 | 1 | 0 | <b>reset</b>                                                                         |
| 1 | 0 | 1 | <b>set</b>                                                                           |
| 1 | 1 | – | <b>invalid</b> : both outputs would be 0, so Q and $\bar{Q}$ are no longer opposites |

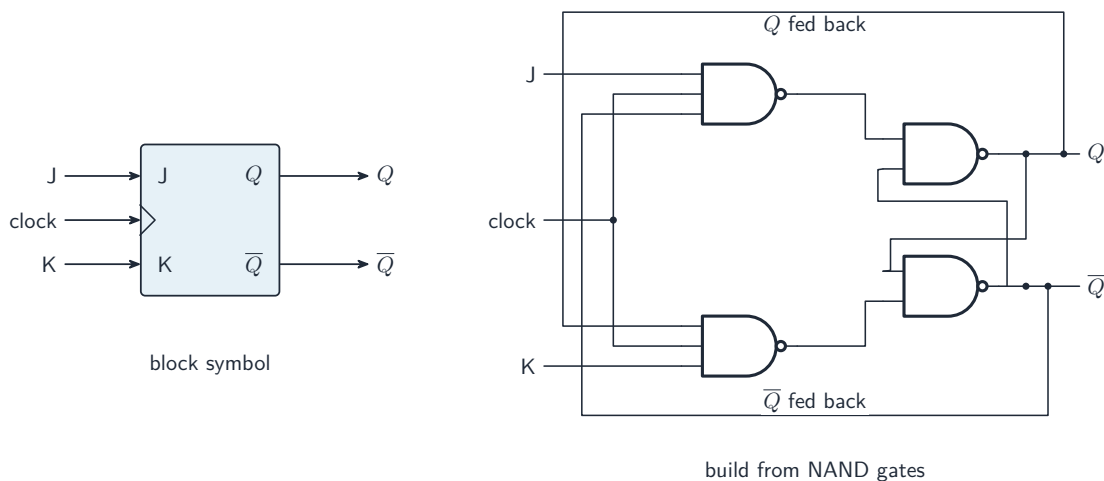

The **JK flip-flop** exists to remove that invalid state. Its first three rows behave exactly as SR does, and the fourth **toggles**:

| J | K | $Q_{\text{next}}$           |
|---|---|-----------------------------|
| 0 | 0 | Q (hold)                    |
| 0 | 1 | 0 (reset)                   |
| 1 | 0 | 1 (set)                     |
| 1 | 1 | $\bar{Q}$ ( <b>toggle</b> ) |

- The JK is also **clocked**, so it changes only on a clock edge. That makes a chain of them predictable, which is what a register or a counter is built from.
- “State one difference” wants the **invalid state**: SR has one, JK replaces it with a toggle.

#### ■ De Morgan’s laws, and simplifying

$$\overline{A \cdot B} = \overline{A} + \overline{B} \qquad \overline{A + B} = \overline{A} \cdot \overline{B}$$

In words: **break the bar and change the sign**. Both are needed, in both directions.

The laws worth recognising on sight:


| Law                                                  |                                     |
|------------------------------------------------------|-------------------------------------|
| $A + \overline{A}B = A + B$                          | absorption with a complement        |
| $A(A + B) = A$                                       | absorption                          |
| $AB + A\overline{B} = A$                             | $B$ makes no difference, so it goes |
| $\overline{\overline{A} + B} = A \cdot \overline{B}$ | De Morgan, then double negation     |

**Worked example.** Simplify  $\overline{\overline{A} + B}$ .


De Morgan on the whole bar:  $\overline{\overline{A} + B} = \overline{\overline{A}} \cdot \overline{B}$ . Then  $\overline{\overline{A}} = A$ , so the answer is  $A \cdot \overline{B}$ .

#### ■ A four-variable Karnaugh map

three variables: the worked example

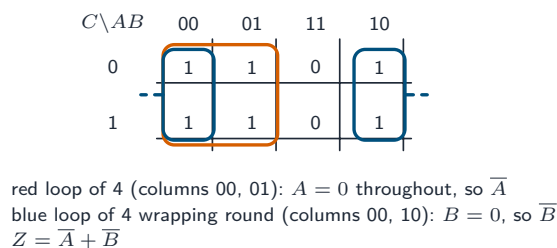

four variables: a wrap-around loop

 

Two rules make a K-map work, and both are about the **order**:

1. The rows and columns run in **Gray code** – 00, 01, 11, 10 – **not** in binary counting order. Adjacent cells then differ in exactly one variable, which is what lets a group cancel that variable.
2. The map **wraps round**: the left column is adjacent to the right, and the top row to the bottom. So the **four corners** form a legitimate group of four.

To use one: mark a 1 in every cell where the output is 1; make the **largest possible** groups of 1, 2, 4 or 8 adjacent 1s, overlapping where that makes a group bigger; then write each group as the variables that **stay the same** across it, and OR the groups together.

**Worked example.** *The output is 1 for  $ABCD = 0000, 0010, 1000$  and  $1010$  only.*

Those are the four **corners**. Across all four,  $B = 0$  and  $D = 0$ , while  $A$  and  $C$  each take both values and so cancel.

$$F = \overline{B} \cdot \overline{D}$$

- The **benefits** of a K-map, which is a question in its own right: it gives a **simplified** expression directly, without the algebra; the simplified circuit uses **fewer gates**, so it is cheaper, smaller and faster; and grouping is a visual step, so it is **less error-prone** than a chain of algebraic manipulations.
- A group must be a power of two in size, and rectangular. Three adjacent 1s are grouped as a 2 and an overlapping 2, never as a 3.

## 2 Practice

Now use the methods above.

**2.1** State the **two** components a full adder has that a half adder does not, in terms of its inputs and what it is built from. [2]

---

---

---

**2.2** Give the Boolean expression for the **Sum** output and for the **carry out** of a full adder. [2]

---

---

---

**2.3** Use De Morgan's laws to simplify  $\overline{\overline{A} + B}$ . [2]

**2.4** State what happens to the output of a **JK** flip-flop when  $J = 1$  and  $K = 1$ . [1]

---

---

**2.5** State why the rows and columns of a Karnaugh map are written in **Gray code** rather than in binary counting order. [2]

---

---


---

### 3 Exam-style questions

**3.1** Complete the truth table for a **full adder** with inputs  $A$ ,  $B$  and  $C_{\text{in}}$ . [4]

| $A$ | $B$ | $C_{\text{in}}$ | Sum | $C_{\text{out}}$ |
|-----|-----|-----------------|-----|------------------|
| 0   | 0   | 0               |     |                  |
| 0   | 0   | 1               |     |                  |
| 0   | 1   | 0               |     |                  |
| 0   | 1   | 1               |     |                  |
| 1   | 0   | 0               |     |                  |
| 1   | 0   | 1               |     |                  |
| 1   | 1   | 0               |     |                  |
| 1   | 1   | 1               |     |                  |

 **3.2** (a) Draw the logic circuit for an **SR flip-flop**, labelling the inputs  $S$  and  $R$  and the outputs  $Q$  and  $\overline{Q}$ . [3]



(b) Complete the truth table for the flip-flop, and state which row is **invalid** and why. [4]

---

---

---

---

---

**3.3** Explain why a flip-flop can act as a **data storage element**. [2]


---

---

---

**3.4** A logic circuit with four inputs  $A$ ,  $B$ ,  $C$  and  $D$  gives an output of 1 only when  $ABCD$  is 0000, 0010, 1000 or 1010.

 (a) Use a Karnaugh map to obtain the simplified Boolean expression for the output. [3]




(b) State **two** benefits of using a Karnaugh map rather than Boolean algebra. [2]

---

---

---

 **3.5** Simplify  $Z = A + \overline{A}B$ , showing each step and naming the law used. [3]



## Solutions

---

Each answer shows the steps, then the **result**.

### 2.1

- it has a **third input**, the carry in  $C_{\text{in}}$ , so it can add a column that receives a carry from the column to its right
- it is built from **two half adders and an OR gate**

### 2.2

- $\text{Sum} = A \oplus B \oplus C_{\text{in}}$
- $C_{\text{out}} = A \cdot B + C_{\text{in}} \cdot (A \oplus B)$  – any equivalent form is accepted

### 2.3

- De Morgan on the whole bar:  $\overline{\overline{A} \cdot \overline{B}}$
- double negation gives  $\mathbf{A \cdot \overline{B}}$

### 2.4

- the output **toggles**: it changes to the opposite of its previous value

### 2.5

- in Gray code, **adjacent cells differ in exactly one variable**
- so a group of adjacent 1s has that one variable taking both values, which lets it be cancelled; in binary counting order adjacent cells could differ in two variables and grouping them would be invalid

### 3.1

- Sum column correct: 0, 1, 1, 0, 1, 0, 0, 1
- $C_{\text{out}}$  column correct: 0, 0, 0, 1, 0, 1, 1, 1

| $A$ | $B$ | $C_{\text{in}}$ | Sum | $C_{\text{out}}$ |
|-----|-----|-----------------|-----|------------------|
| 0   | 0   | 0               | 0   | 0                |
| 0   | 0   | 1               | 1   | 0                |
| 0   | 1   | 0               | 1   | 0                |
| 0   | 1   | 1               | 0   | 1                |
| 1   | 0   | 0               | 1   | 0                |
| 1   | 0   | 1               | 0   | 1                |
| 1   | 1   | 0               | 0   | 1                |
| 1   | 1   | 1               | 1   | 1                |

- the Sum is 1 on the rows with an **odd** number of 1s; the carry out is 1 whenever at least two inputs are 1

### 3.2

(a) two **NOR** gates

- **cross-coupled**: the output of each is an input to the other
- $S$  and  $R$  labelled as the remaining input of one gate each, and the outputs labelled  $Q$  and  $\overline{Q}$

(b)  $S = 0, R = 0$ :  $Q$  **holds** its previous value

- $S = 0, R = 1$ :  $Q = 0$ , reset;  $S = 1, R = 0$ :  $Q = 1$ , set
- $S = 1, R = 1$  is the **invalid** row
- because both outputs would be forced to 0, so  $Q$  and  $\overline{Q}$  would no longer be complements of each other, and what happens next depends on which input changes first

### 3.3

- the outputs are **fed back** as inputs, so with both inputs at 0 the circuit holds whatever state it was last put into
- that state persists until it is deliberately set or reset, so one flip-flop stores **one bit**; a register is a row of them

### 3.4

(a) the four cells are the **corners** of the map, and a K-map **wraps round**, so they form one valid group of four

- across all four,  $B = 0$  and  $D = 0$ ;  $A$  and  $C$  each take both values and cancel
- $\mathbf{F} = \overline{\mathbf{B}} \cdot \overline{\mathbf{D}}$
- four separate groups of one, giving four ANDed terms, earns the first mark only: the question is about grouping

(b) any two: it gives the simplified expression **directly**, without a chain of algebra

- the simplified circuit needs **fewer gates**, so it is cheaper, smaller and faster; and grouping is visual, so it is less error-prone than algebraic manipulation

### 3.5

- $A + \overline{A}B$ : apply the **distributive** law,  $A + \overline{A}B = (A + \overline{A})(A + B)$
- $A + \overline{A} = 1$  – the **complement** law
- $1 \cdot (A + B) = \mathbf{A} + \mathbf{B}$  – the identity law
- quoting the absorption result  $A + \overline{A}B = A + B$  directly earns the answer mark but not the working marks, and the question says to show each step