

3.2.1 Drawing logic circuits, three-input truth tables and reading an expression back out

Name: _____ Class: _____ Date: _____

Total: 31 marks

KEY WORDS logic circuit 逻辑电路 • truth table 真值表 • working column 工作列
• ram 随机存取存储器 • rom 只读存储器

Objective

Build the skills to answer the **logic circuit** 逻辑电路 questions that sheet 3.2 does not reach. That sheet names the six gates and writes short expressions; this one is about the three things the syllabus asks you to **construct** and that carry most of the marks: **drawing a circuit**, filling a three-input **truth table** 真值表 with a **working column** 工作列 for each gate, and reading a **logic expression** back out of a completed truth table.

You must be able to:

- construct a **logic circuit** from a logic expression, from a problem statement, and from a truth table
- construct a **truth table** from a logic circuit, using a working column for each gate's output
- construct a **logic expression** from a truth table, from a circuit, and from a problem statement
- use **NAND**, **NOR** and **XOR** inside a larger circuit

1 Worked examples

Study these first. Each one shows a **method** that a question later on this sheet needs.

■ From an expression to a circuit

NAND



NOR



XOR




Three rules, and they settle every drawing question:

- One gate per operator.** Count the operators in the expression and you know how many gates to draw.
- Innermost brackets first.** Whatever is inside a bracket is computed before it can be fed into the gate outside it, so it sits to the **left** in the drawing.
- A variable used twice is still one input.** Draw a single wire from that input and put a **junction dot** where it branches. Two separate wires labelled B is the drawing error the mark scheme looks for.

Worked example. Draw the circuit for $X = (A \text{ AND NOT } B) \text{ OR } (B \text{ AND } C)$.

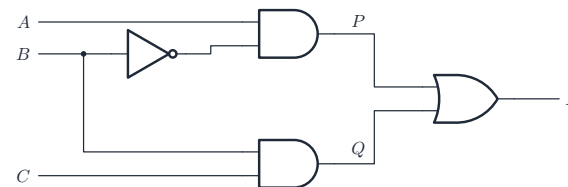Four operators, so four gates: a NOT, two ANDs and an OR. B appears twice, so it is one input with a junction.



- Label each gate's output** (P , Q) as you draw. It costs nothing and it is what makes the truth table below easy.

■ A three-input truth table, with working columns

Three inputs means $2^3 = 8$ rows. Write them by **counting up in binary** from 000 to 111 – that way none is missed and none repeats.

Then add one column per gate. Work left to right across the circuit, filling a whole column at a time rather than a whole row.

A	B	C	$P = A \text{ AND NOT } B$	$Q = B \text{ AND } C$	$X = P \text{ OR } Q$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	1	1	1

- The working columns are worth marks of their own when the question prints a **working space**. Fill it in: a wrong final column with correct working usually still earns something, and a right answer with nothing shown can earn nothing on a “show your working” question.

■ From a truth table to an expression

Look only at the rows where $X = 1$. Each one becomes a term:

- write each input that is **1** as itself, and each input that is **0** as **NOT** that input,
- **AND** the three together,
- then **OR** all the terms from all the 1-rows.

Worked example. A truth table gives $X = 1$ on the rows $ABC = 001, 010$ and 111 , and 0 everywhere else.

$X = (\text{NOT } A \text{ AND NOT } B \text{ AND } C) \text{ OR } (\text{NOT } A \text{ AND } B \text{ AND NOT } C) \text{ OR } (A \text{ AND } B \text{ AND } C)$

- One term per 1-row, and every term carries **all three** inputs. Leaving one out changes the expression.
- Rows where $X = 0$ contribute nothing. Do not write terms for them.

■ From a problem statement

Read the sentence and translate it piece by piece: each **condition** becomes an input, each “**and**” an AND gate, each “**or**” an OR gate, and each “**not**”, “**is off**” or “**is 0**” a NOT gate. Keep the order of the sentence, and bracket whatever the sentence groups together.

“A pump runs when the tank is not full and the switch is on” becomes $X = (\text{NOT } A) \text{ AND } B$, then one NOT gate feeding one AND gate.

2 Practice

Now use the methods above.

2.1 Draw the logic circuit for $X = (A \text{ OR } B) \text{ AND } (\text{NOT } C)$. [3]

2.2 Complete the truth table for the circuit in 2.1. Use the working columns. [3]

A	B	C	$A \text{ OR } B$	$\text{NOT } C$	X
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

2.3 Name the **single** gate that does the same job as each of these. [2]

(a) NOT ($A \text{ AND } B$)

(b) NOT ($A \text{ OR } B$)

2.4 A truth table gives $X = 1$ on the rows $ABC = 001$ and 110 , and $X = 0$ on every other row.

Write the logic expression for X . [2]

2.5 A circuit uses input B as an input to two different gates. State how this is shown on the circuit diagram. [1]


3 Exam-style questions

3.1 A chemical tank has three sensors. An alarm X sounds when the temperature sensor A reads 1 **and** the pressure sensor B reads 0, **or** when the manual override C reads 1.

(a) Write the logic expression for X . [2]

(b) Draw the logic circuit for X . [3]

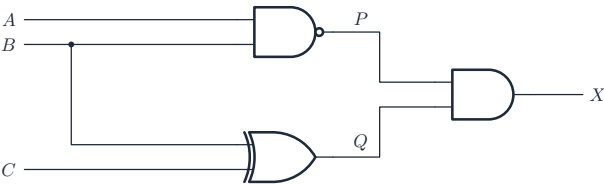3.2 A logic circuit is shown. P and Q are the outputs of the first two gates.



(a) Complete the truth table, filling the working columns P and Q . [4]


A	B	C	P	Q	X
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

(b) State the values of A , B and C for which $X = 1$. [2]

3.3 A truth table gives $X = 1$ on the rows $ABC = 000$, 011 and 110 , and $X = 0$ on every other row.

Write the logic expression for X . [3]

 3.4 Draw the logic circuit for $X = (A \text{ XOR } B) \text{ AND } (\text{NOT } C)$. [3]



3.5 A student is asked to draw the circuit for $X = A \text{ AND } (B \text{ OR } C)$, but wires it as $(A \text{ AND } B) \text{ OR } C$.

Explain, naming **one** row of the truth table, how the two circuits behave differently. [3]
