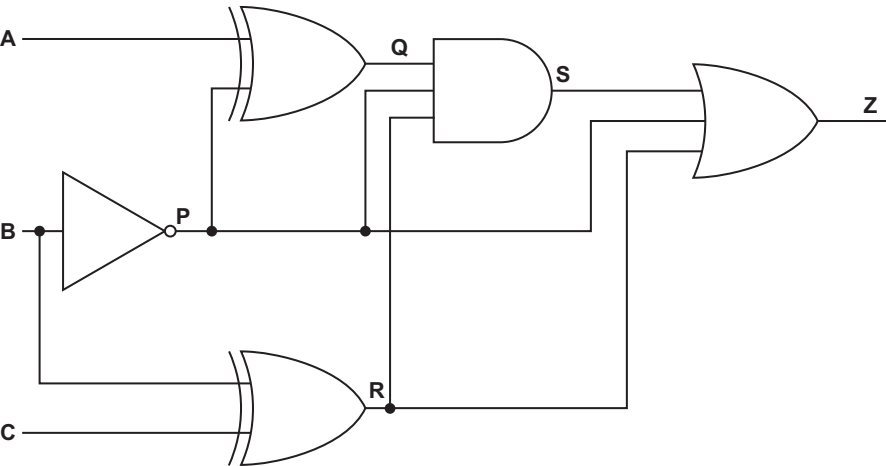


6 (a) The diagram shows a logic circuit.



Complete the truth table for the given logic circuit.
Show your working.

			Working space				
A	B	C	P	Q	R	S	Z
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

[3]

(b) (i) Complete the Karnaugh map (K-map) for the Boolean expression:

$$\overline{A}.\overline{B}.C + \overline{A}.B.C + A.\overline{B}.C + A.B.\overline{C}$$

		BC			
A		00	01	11	10
	0				
	1				

[2]

(ii) Draw loop(s) around appropriate group(s) in the K-map to produce an optimal sum-of-products. [2]

(iii) Write the Boolean expression from your answer to part b(ii) as a simplified sum-of-products. Do **not** carry out any further simplification.

.....

..... [2]

6 (a) The Karnaugh map (K-map) represents a logic circuit with four inputs.

		AB			
CD		00	01	11	10
	00	0	0	0	0
	01	1	1	1	0
	11	0	1	1	1
	10	0	0	1	1

(i) Draw loop(s) around appropriate group(s) in the K-map to produce an optimal sum-of-products. [3]

(ii) Write the Boolean expression from your answer to part a(i) as a simplified sum-of-products. Do **not** carry out any further simplification.

.....
 [2]

(b) Simplify the following expression using De Morgan's laws and Boolean algebra.

Show all the stages in your simplification.

$$X = \overline{A+B+C} + \overline{\overline{B}+C}$$

.....

 [3]

6 The truth table for a logic circuit is shown.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

(a) Write the Boolean logic expression that corresponds to the given truth table as the sum-of-products.

X =
 [3]

(b) Complete the Karnaugh map (K-map) for the given truth table.

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

[2]

(c) Draw loop(s) around appropriate group(s) in the K-map to produce an optimal sum-of-products.

[2]

(d) Write the Boolean logic expression from your answer to part (c) as the simplified sum-of-products.

X =

..... [2]

7 The truth table for a logic circuit is shown.

INPUT				OUTPUT
A	B	C	D	T
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

(a) Write the Boolean logic expression that corresponds to the given truth table as the sum-of-products.

T =

..... [3]

(b) Complete the Karnaugh map (K-map) for the given truth table.

		AB			
CD		00	01	11	10
	00				
	01				
	11				
	10				

[2]

(c) Draw loop(s) around appropriate group(s) in the K-map to produce an optimal sum-of-products.

[2]

(d) (i) Write the Boolean logic expression from your answer to part (c) as the simplified sum-of-products.

T =

..... [2]

(ii) Use Boolean algebra to write your answer to part (d)(i) in its simplest form.

T = [1]