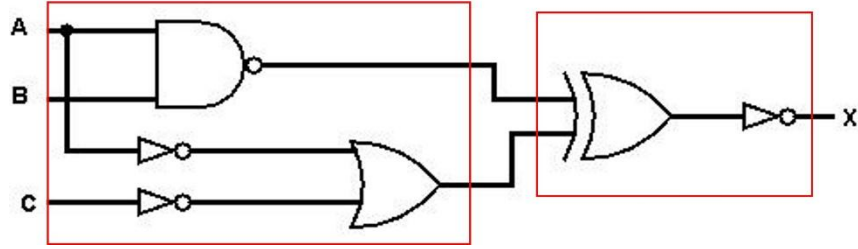


3(a)	One mark per bullet point, max 2 marks • (A NAND B) and (NOT A OR NOT C) • XOR and NOT 
3(b)	1 mark per bullet point, max 2 marks • One correct term: (R AND S AND NOT T) // (NOT R AND NOT S AND T) • Second correct term plus the OR in correct place Answer: $Q = (R \text{ AND } S \text{ AND NOT } T) \text{ OR } (\text{NOT } R \text{ AND NOT } S \text{ AND } T)$

3(a)


1 mark per shaded area, max 2 marks

A	B	C		X
0	0	0		1
0	0	1		0
0	1	0		1
0	1	1		1
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		1

3(b)

1 mark per bullet point, max 2 marks

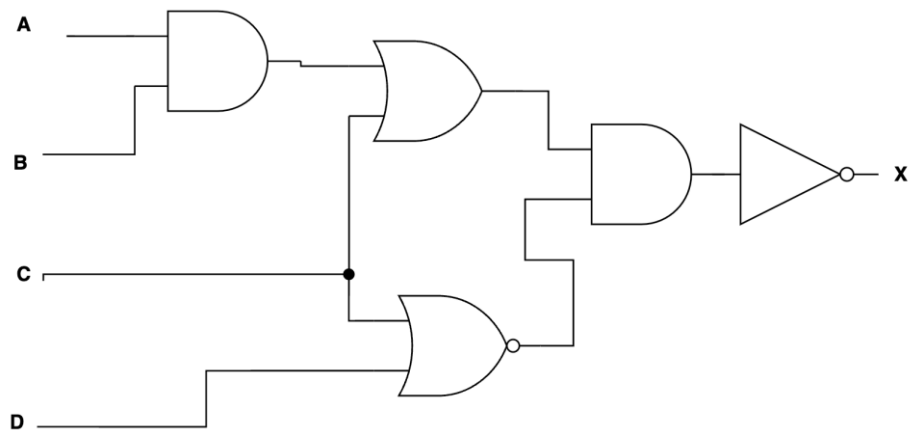- A AND B OR C
- C NOR D and final two gates



6(a)	
------	--

1(a)	1 mark each: $X = Q \text{ AND } (\text{NOT } P \text{ OR } R)$ $Y = S \text{ XOR } (Q \text{ NOR } R)$				
1(b)	1 mark for first 4 rows, 1 mark for second 4 rows				
	A	B	C	Working space	X
	0	0	0		1
	0	0	1		1
	0	1	0		0
	0	1	1		1
	1	0	0		0
	1	0	1		0
	1	1	0		1
	1	1	1		1

7(a)	One mark for working, (all four columns P, Q, R and S) One mark for first eight rows of column Z (Shaded) One mark for second eight rows of column Z (Unshaded) <table><tr><th colspan="4"></th><th colspan="4">Working space</th><th></th></tr><tr><th>A</th><th>B</th><th>C</th><th>D</th><th>P</th><th>Q</th><th>R</th><th>S</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr></table>					Working space					A	B	C	D	P	Q	R	S	Z	0	0	0	0	1	0	0	1	0	0	0	0	1	1	0	0	1	0	0	0	1	0	0	1	0	1	0	0	0	1	1	0	1	0	1	0	0	1	0	0	1	0	0	1	0	0	1	0	1	1	0	0	1	0	0	1	1	0	0	0	0	0	1	0	1	1	1	0	0	1	0	0	1	0	0	0	1	0	0	1	0	1	0	0	1	1	0	0	1	0	1	0	1	0	0	0	0	0	1	1	0	1	1	0	0	0	0	1	1	1	0	0	1	0	0	1	0	1	1	0	1	1	0	0	1	0	1	1	1	0	0	0	0	0	1	1	1	1	1	0	0	1	0	0
				Working space																																																																																																																																																															
A	B	C	D	P	Q	R	S	Z																																																																																																																																																											
0	0	0	0	1	0	0	1	0																																																																																																																																																											
0	0	0	1	1	0	0	1	0																																																																																																																																																											
0	0	1	0	0	1	0	1	0																																																																																																																																																											
0	0	1	1	0	1	0	1	0																																																																																																																																																											
0	1	0	0	1	0	0	1	0																																																																																																																																																											
0	1	0	1	1	0	0	1	0																																																																																																																																																											
0	1	1	0	0	0	0	0	1																																																																																																																																																											
0	1	1	1	0	0	1	0	0																																																																																																																																																											
1	0	0	0	1	0	0	1	0																																																																																																																																																											
1	0	0	1	1	0	0	1	0																																																																																																																																																											
1	0	1	0	0	0	0	0	1																																																																																																																																																											
1	0	1	1	0	0	0	0	1																																																																																																																																																											
1	1	0	0	1	0	0	1	0																																																																																																																																																											
1	1	0	1	1	0	0	1	0																																																																																																																																																											
1	1	1	0	0	0	0	0	1																																																																																																																																																											
1	1	1	1	0	0	1	0	0																																																																																																																																																											
7(b)	One mark for correct answer (terms may be in any order) $Z = \bar{A}.B.C.\bar{D} + A.\bar{B}.C.\bar{D} + A.\bar{B}.C.D + A.B.C.\bar{D}$																																																																																																																																																																		


7(c)	One mark for each mark point • Correct application of De Morgan's laws • Correct application of Idempotent, Distributive or Absorption laws • Correct application of Idempotent, Distributive or Absorption laws • Correct final answer $(\overline{A+B}).(\overline{A.B+B.C})$ $(\overline{A.B}).(\overline{A+B+B.C})$ DeMorgan's laws $(\overline{A.B}).(\overline{A+B+C})$ Idempotent laws $(\overline{A.A+A.B+A.C}).(\overline{B.A+B.B+B.C})$ Distributive laws $(\overline{A+A.B+A.C}).(\overline{A.B+B+B.C})$ Idempotent laws $(\overline{A+A.C}).(\overline{B+B.C})$ Absorption laws $\overline{A.B} // \overline{A+B}$ Absorption laws / Final Answer
------	--

3(a)	Two marks for all six correct terms One mark for any four correct terms $Z = \bar{A}.\bar{B}.C.\bar{D} + \bar{A}.\bar{B}.C.D + \bar{A}.B.\bar{C}.\bar{D} + A.\bar{B}.C.\bar{D} + A.\bar{B}.C.D + A.B.\bar{C}.\bar{D}$																									
3(b)(i)	Two marks if no errors present One mark if one error present AB CD <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>11</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>10</td><td>1</td><td>0</td><td>0</td><td>1</td></tr></table>		00	01	11	10	00	0	1	1	0	01	0	0	0	0	11	1	0	0	1	10	1	0	0	1
	00	01	11	10																						
00	0	1	1	0																						
01	0	0	0	0																						
11	1	0	0	1																						
10	1	0	0	1																						
3(b)(ii)	One mark for each correct loop (Max 2) AB CD <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>11</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>10</td><td>1</td><td>0</td><td>0</td><td>1</td></tr></table>		00	01	11	10	00	0	1	1	0	01	0	0	0	0	11	1	0	0	1	10	1	0	0	1
	00	01	11	10																						
00	0	1	1	0																						
01	0	0	0	0																						
11	1	0	0	1																						
10	1	0	0	1																						

3(b)(iii)	One mark for each mark point - One correct Boolean term - Boolean terms and operator correct and no other terms present $Z = \bar{B}.C + B.\bar{C}.\bar{D} // B.\bar{C}.\bar{D} + \bar{B}.C$
-----------	---

5(a)	1 mark for all 3 appropriate sensors <table border="1"> <thead> <tr> <th>Scenario</th><th>Type of sensor</th></tr> </thead> <tbody> <tr> <td>A door is open.</td><td>Pressure sensor // Infra-red</td></tr> <tr> <td>The external daylight-level is below a set amount.</td><td>Light sensor</td></tr> <tr> <td>A person is detected within 2 metres.</td><td>Infra-red</td></tr> </tbody> </table>	Scenario	Type of sensor	A door is open.	Pressure sensor // Infra-red	The external daylight-level is below a set amount.	Light sensor	A person is detected within 2 metres.	Infra-red
Scenario	Type of sensor								
A door is open.	Pressure sensor // Infra-red								
The external daylight-level is below a set amount.	Light sensor								
A person is detected within 2 metres.	Infra-red								
5(b)	1 mark for each correct expression $X = E \text{ AND } A \text{ AND } C$ $Y = E \text{ AND } (B \text{ OR } C \text{ OR } D)$								
5(c)	1 mark for each bullet point (max 3) for a correct justification No marks for the identification of the system Monitoring system - There is no use of feedback // The light and the alarm are just warnings - The output of the floodlight or the audio alarm does not affect the input of data from the sensors - The system does not have any actuators								

1(a)	1 mark for: Output is only 1 if one input is 1 and the other is 0 // Output is only 1 if both inputs are different // Output is only 0 if both inputs are the same
1(b)	1 mark each: $((A \text{ NOR } B) \text{ AND } (A \text{ OR } B))$ $\text{NAND } (B \text{ AND } C)$ $X = ((A \text{ NOR } B) \text{ AND } (A \text{ OR } B)) \text{ NAND } (B \text{ AND } C)$
1(c)	1 mark for NOT gate, 2 correct AND gates and the NAND gate 1 mark for OR gate and the final AND gate

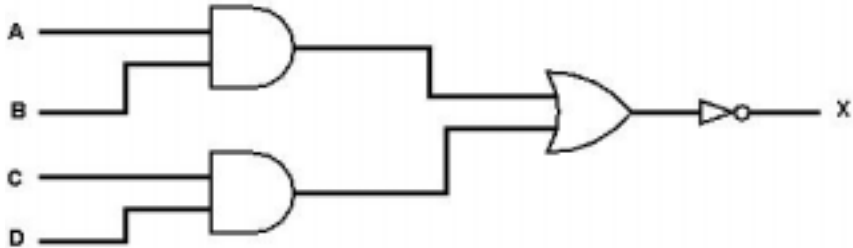1(a)	1 mark for each correct answer: <i>NAND</i> - The output is 0 when both inputs are 1, otherwise the output is 1 <i>NOR</i> - The output is 1 when both inputs are 0, otherwise the output is 0 <i>XOR</i> - The output is 1 when one of the inputs is 1 and the other input is 0, otherwise the output is 0 <i>OR</i> - The output is 0 when both inputs are 0, otherwise the output is 1
1(b)	1 mark for both AND gates with correct inputs 1 mark for correct OR and NOT gates with correct inputs and no superfluous gates:  <pre> graph LR A --- AND1[AND] B --- AND1 C --- AND2[AND] D --- AND2 AND1 --- OR[OR] AND2 --- OR OR --- NOT[NOT] NOT --- X </pre>