

Alternating currents

A-Level Physics

Alternating current basics




A substation's transformers step alternating voltage up or down.

An **alternating current** (a.c.) keeps reversing direction. Mains supply is sinusoidal a.c.: I or V follows a sine wave in time:

$$I = I_0 \sin(\omega t), \quad V = V_0 \sin(\omega t).$$

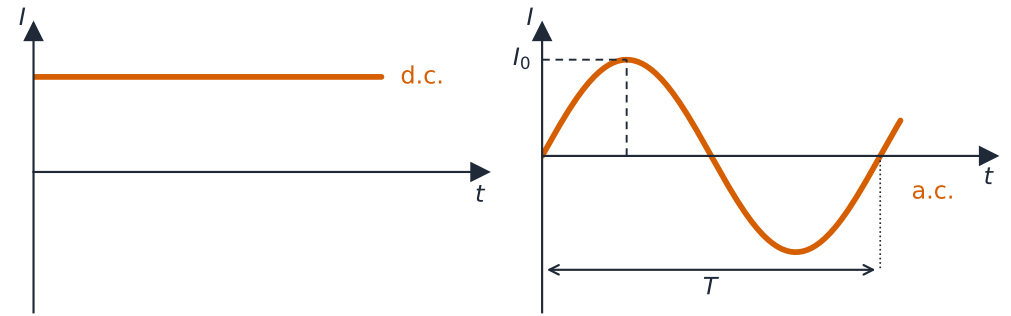(For a purely resistive load the **voltage** and **current** are in phase, which is the case in this syllabus.)



d.c. constant polarity · a.c. reverses each cycle

A steady direct current compared with a sinusoidal alternating current of peak I_0 and period T

■ Key terms

- **period** T – the time for one full cycle. Unit: s.
- **frequency** f – cycles per second; $f = 1/T$. Mains is often 50 Hz or 60 Hz.
- **angular frequency** $\omega = 2\pi f = 2\pi/T$.
- **peak value** I_0 or V_0 – the largest value in a cycle (also called the amplitude).
- **peak-to-peak value** $2I_0$ – from $+I_0$ to $-I_0$. Useful when reading an oscilloscope.

The two-mark definitions. The frequency of an alternating current is the number of complete cycles per unit time (say “per second” or “per unit time”, and “complete cycles” or “oscillations”). The period is the time for one complete cycle, and the peak value is the maximum value of the current or voltage during a cycle. Note that the **mean** value of a sinusoidal current over a cycle is **zero**, which is exactly why the r.m.s. value is needed to describe it.

Reading the equation. In $V = V_0 \sin(\omega t)$ the number in front is the peak value and the number multiplying t is $\omega = 2\pi f$; the angle ωt is in **radians**, so set the calculator to radians before evaluating. A supply written with $\cos$ instead of $\sin$ is the same wave starting at its peak rather than at zero.

Worked example. The output of a supply is $V = 320 \sin(100\pi t)$ (volts, seconds). Find the peak value, the frequency, the period and the r.m.s. value, and the first time after $t = 0$ at which $V = 160$ V.

Peak $V_0 = 320$ V. $\omega = 100\pi$ rad s⁻¹, so $f = \omega/2\pi = 50$ Hz and $T = 1/f = 0.020$ s. $V_{\text{r.m.s.}} = 320/\sqrt{2} = 226$ V. For $V = 160$ V: $\sin(100\pi t) = 0.5$, so $100\pi t = \pi/6$ and $t = 1/600 = 1.7 \times 10^{-3}$ s. (For $V = 18 \cos(40\pi t)$ the same reading gives $V_0 = 18$ V, $f = 20$ Hz, $T = 50$ ms, and a sketch that starts at +18 V.)


■ Reading a CRO trace

Same as for any wave (Topic 7), using a **cathode-ray oscilloscope** :

- horizontal divisions $\times$ **time-base** $\rightarrow$ period T , so $f = 1/T$.
- vertical divisions $\times$ y -gain $\rightarrow$ peak voltage V_0 (measure centre to peak, or peak-to-peak then halve).

Power delivered to a resistor

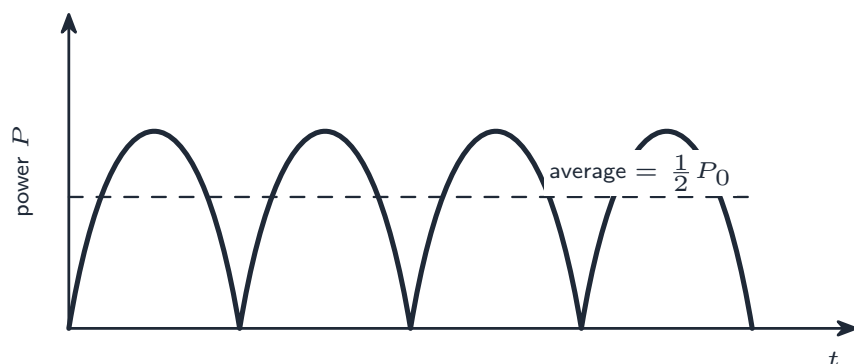For a resistive load R , the instant **power** is $P(t) = I(t)^2 R$. With $I = I_0 \sin(\omega t)$:



The power in a resistor pulses; its average is half the peak

$$P(t) = I_0^2 R \sin^2(\omega t).$$

This is always positive, with peak $I_0^2 R$ and minimum zero, oscillating at twice the frequency of I . The mean of $\sin^2(\omega t)$ over a cycle is $\frac{1}{2}$, so the **average power** is

$$\langle P \rangle = \frac{1}{2} I_0^2 R = \frac{1}{2} P_{\text{peak}}.$$


Average a.c. power in a resistor is **half the peak power**.

”Show by calculation that the mean power is half the peak power.” A supply of peak value 12 V drives a 680 Ω resistor. Peak power: $P_0 = V_0^2/R = 12^2/680 = 0.212$ W, the instantaneous power at the moment the voltage is at its peak. Mean power: use the r.m.s. value, $V_{\text{r.m.s.}} = 12/\sqrt{2} = 8.49$ V, so $\langle P \rangle = V_{\text{r.m.s.}}^2/R = 8.49^2/680 = 0.106$ W, exactly half. The two calculations must be shown separately; writing “ $\frac{1}{2}$ of 0.212” scores nothing, because that is the thing being shown. The $\frac{1}{2}$ is $(1/\sqrt{2})^2$: squaring the r.m.s. factor.

Root-mean-square (r.m.s.) values

The r.m.s. current $I_{\text{r.m.s.}}$ is the **steady direct current** that would give the same average power in the same **resistance** R . From $\langle P \rangle = I_{\text{r.m.s.}}^2 R = \frac{1}{2} I_0^2 R$:
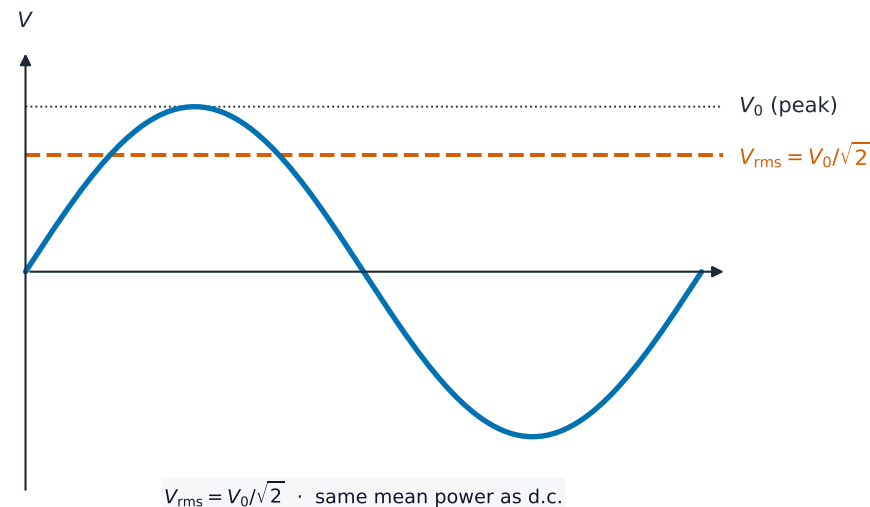
$$I_{\text{r.m.s.}} = \frac{I_0}{\sqrt{2}}, \quad V_{\text{r.m.s.}} = \frac{V_0}{\sqrt{2}}.$$




The r.m.s. value is the steady d.c. level ($V_0/\sqrt{2}$) that delivers the same average power as the a.c.

Worked example. An a.c. supply has a peak voltage of 12 V. Find its r.m.s. voltage.

$$V_{\text{r.m.s.}} = \frac{V_0}{\sqrt{2}} = \frac{12}{\sqrt{2}} \approx 8.5 \text{ V}.$$

The $\sqrt{2}$ comes from the name **root-mean-square** : $I_{\text{r.m.s.}} = \sqrt{\langle I^2 \rangle}$ and $\langle \sin^2 \rangle = \frac{1}{2}$. (Only the sinusoidal case is needed.)

The two-mark definition. *The r.m.s. value of an alternating current is the value of the direct (steady) current that would dissipate the same (mean) power in the same resistor.* ”By reference to the heating effect” means exactly this sentence: same resistor, same power (or same heating), direct current. A definition that only says “ $I_0/\sqrt{2}$ ” scores nothing, because that formula is true only for a sine wave.

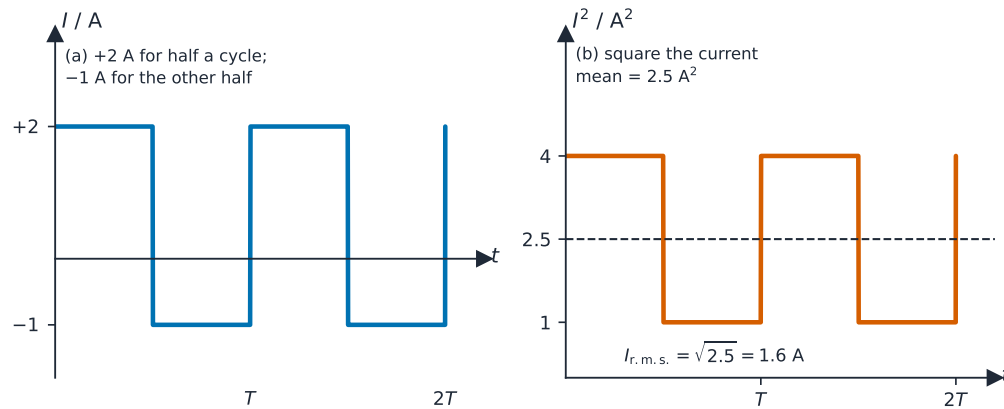

Root-mean-square, taken literally: square the current, average the squares over a cycle, take the square root. For a non-sinusoidal current this is the only way; $I_0/\sqrt{2}$ applies to a sine wave alone

Worked example (non-sinusoidal). A current through a resistor is +2.0 A for the first half of each cycle and -1.0 A for the second half, a **square wave**. Find its r.m.s. value and the mean power in a 10 Ω resistor.

Square the current: 4.0 A² for half the time and 1.0 A² for the other half, so the mean square is $(4.0 + 1.0)/2 = 2.5 \text{ A}^2$ and $I_{\text{r.m.s.}} = \sqrt{2.5} = 1.6 \text{ A}$. Mean power = $I_{\text{r.m.s.}}^2 R = 2.5 \times 10 = 25 \text{ W}$. The sign of the current does not matter to the heating (it is squared away), and $I_0/\sqrt{2}$ would have given the wrong answer, 1.4 A: that shortcut is for sine waves only.

■ Why r.m.s. matters

Quoted a.c. values are r.m.s. values. "230 V mains" means $V_{\text{r.m.s.}} = 230 \text{ V}$, with peak $V_0 = 230\sqrt{2} \approx 325 \text{ V}$. Components must be rated for the peak, not the r.m.s. Average power then takes the d.c. form:

$$\langle P \rangle = I_{\text{r.m.s.}}^2 R = V_{\text{r.m.s.}}^2 / R = V_{\text{r.m.s.}} I_{\text{r.m.s.}}$$


Worked example. A heater of resistance 50 Ω is connected to the 230 V r.m.s. mains. Find the r.m.s. current and the average power dissipated.

$$I_{\text{r.m.s.}} = \frac{V_{\text{r.m.s.}}}{R} = \frac{230}{50} = 4.6 \text{ A}, \quad \langle P \rangle = V_{\text{r.m.s.}} I_{\text{r.m.s.}} = 230 \times 4.6 \approx 1.1 \times 10^3 \text{ W}.$$

Worked example. A sinusoidal supply of r.m.s. value 4.2 V and frequency 50 kHz is connected across a 150 Ω resistor. Find the peak current, the mean power, and write down an equation for the current.

$V_0 = 4.2\sqrt{2} = 5.9 \text{ V}$, so $I_0 = V_0/R = 5.9/150 = 0.040 \text{ A}$ (or $I_{\text{r.m.s.}} = 4.2/150 = 0.028 \text{ A}$ and then $\times \sqrt{2}$). Mean power = $V_{\text{r.m.s.}}^2/R = 4.2^2/150 = 0.12 \text{ W}$. With $\omega = 2\pi f = 2\pi \times 5.0 \times 10^4 = 3.1 \times 10^5 \text{ rad s}^{-1}$: $I = 0.040 \sin(3.1 \times 10^5 t)$ (amps, seconds). Keep the two families apart: peak values go into the equation and into component ratings; r.m.s. values go into power.

Rectification

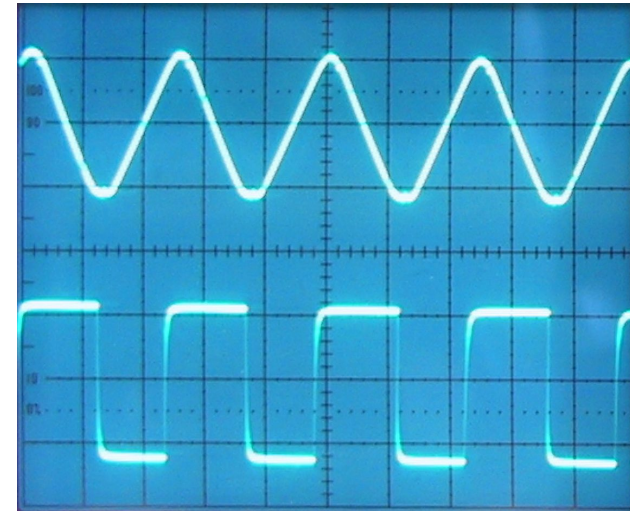

An oscilloscope shows how a voltage varies with time.


Rectification turns an alternating voltage into a one-direction (d.c.-like) voltage, using **diodes** (which conduct in only one direction).

“State what is meant by rectification.” The conversion of an alternating current (or voltage) into a direct current (or voltage): one that flows in one direction only, however much it varies. A **diode** conducts only when it is **forward-biased**, that is, when its anode (the flat end of the symbol's triangle) is more positive than its cathode (the bar); otherwise it is reverse-biased and behaves like an open switch. Treat it as ideal: zero resistance one way, infinite the other.


■ Half-wave rectification

A **single diode** in series with the load passes only the positive half of each cycle; in the negative half the diode is **reverse-biased** and no current flows. This is **half-wave rectification**.

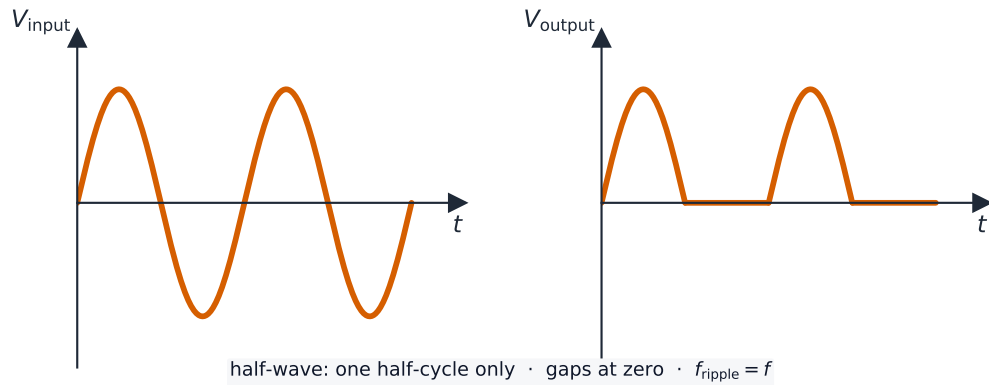Output: positive half-waves with flat zero gaps. The mean output is $V_0/\pi \approx 0.32V_0$. Drawback: half the input is wasted and the output is very uneven.



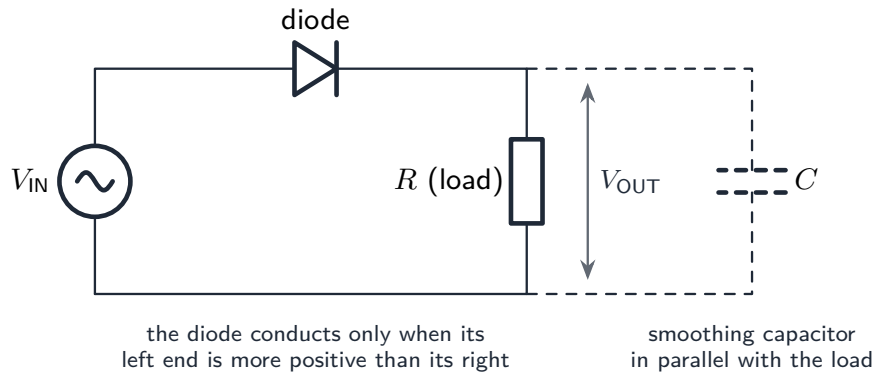In half-wave rectification a single diode passes only the positive half-cycles




The half-wave rectifier the exam asks you to draw: source, diode, load in series, output across the load; a smoothing capacitor, if wanted, goes in parallel with the load, never in series

Completing the circuit. "Complete the diagram to produce half-wave rectification" needs one diode in **series** between the supply and the load, with the triangle pointing the way the output current must flow, and V_{OUT} taken across the **load**. If a capacitor is to smooth the output it goes **across the load** (in parallel); a capacitor in series would block the d.c. altogether.

■ Full-wave rectification (bridge rectifier)

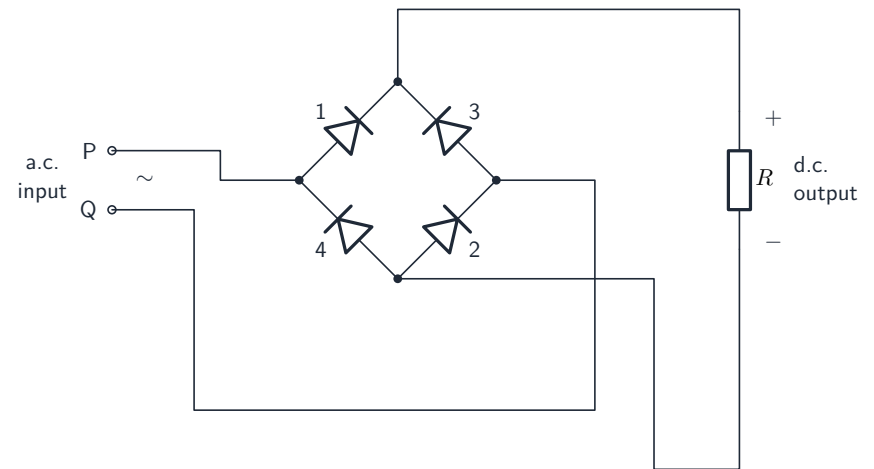
A **bridge rectifier** uses **four diodes** arranged so the current through the load always flows the same way, whichever a.c. terminal is positive – **full-wave rectification**. On each half-cycle a different pair of diodes conducts, but the load always sees the same direction.



A four-diode bridge sends the load current the same way whichever a.c. terminal is positive

Explaining the bridge (the standard four-marker). When terminal P is positive, current leaves P, passes through the diode pointing away from P to the **top** of the load, flows **down** through the load and returns to Q through the diode pointing towards Q; the other two diodes are reverse-biased and carry nothing. When Q is positive the other pair conducts, but they are arranged so that the current still enters the load at the top: the load current is in the **same direction** in both half-cycles. Name the diodes in each half-cycle and say which end of the load is positive.

Completing a bridge. Given a bridge with diodes missing, remember the rule for every diode: conventional current flows through it in the direction of the triangle. Both diodes joined to the **positive** output terminal must point **towards** it; both joined to the **negative** output terminal must point **away** from it. A bridge with a diode the wrong way round either short-circuits the supply on one half-cycle or passes nothing. Output: a continuous run of positive half-waves (no gaps), at **twice** the input frequency. The mean output is $2V_0/\pi \approx 0.64V_0$ – double the half-wave value. It uses all the input and is smoother and easier to filter.

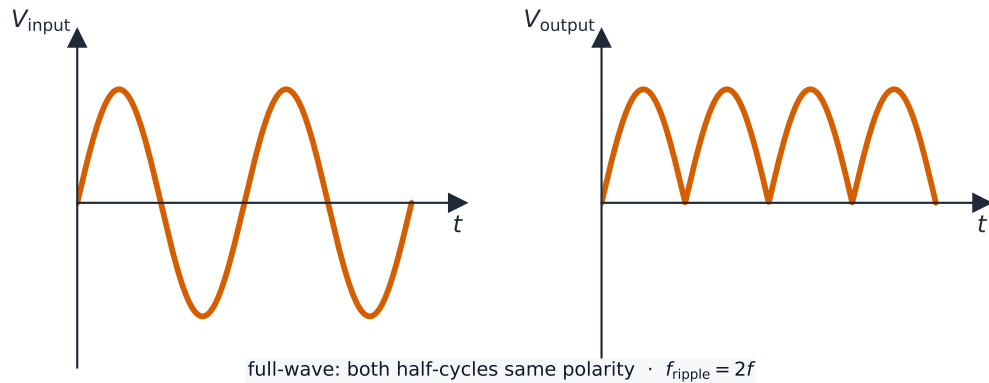

In full-wave rectification every half-cycle is used, giving a continuous run of positive humps

■ Drawing the diagrams

- half-wave: a.c. source – single diode – load R , in series.
- full-wave bridge: four diodes as the arms of a "diamond"; the a.c. input goes to one pair of opposite corners, the load R across the other pair. The diode directions make the load terminals keep the same polarity for either input polarity.

"State the difference between half-wave and full-wave rectification." In half-wave rectification only **one** half of each input cycle appears at the output and the other half is blocked (the output is zero for half the time); in full-wave rectification **both** halves appear, one of them inverted, so there are no gaps and the output has twice the input frequency. A sketch should show, for half-wave, positive humps separated by flat zero sections of equal length; for full-wave, positive humps joined at the zero line.


Smoothing with a capacitor

A rectifier's output is still bumpy. To smooth it, put a **capacitor** C in parallel with the load R .


■ How it works

- on the **rising part** of each pulse, the capacitor charges up to near the peak.
- on the **falling part** (and any gap), the diodes are reverse-biased, so the capacitor **discharges through the load**, keeping current flowing. The voltage falls with **time constant** RC (Topic 19).
- at the next peak, the capacitor charges again, and the cycle repeats.

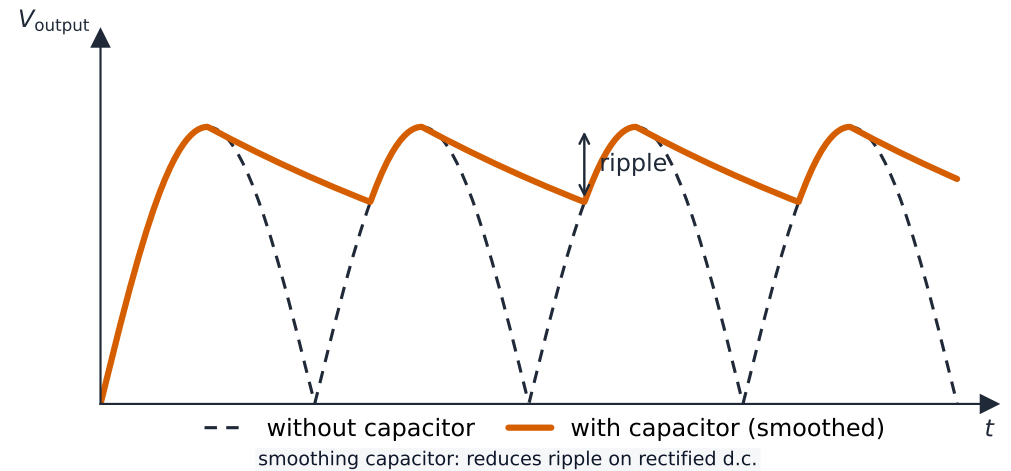The output now sits near the peak with small dips. The size of the dips is the **ripple** (this whole step is called **smoothing**).



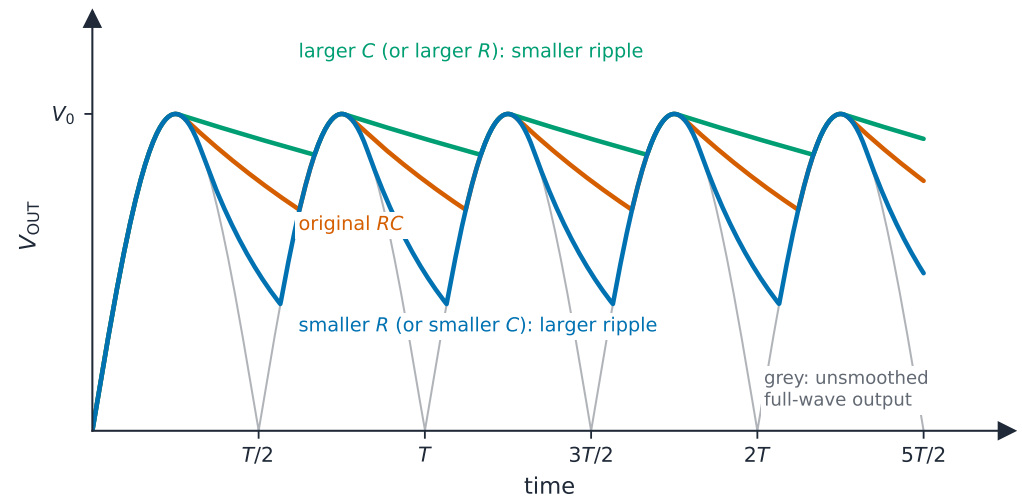A capacitor across the load smooths the rectified output, leaving only a small ripple



The same rectified supply smoothed with different time constants: a larger RC (more capacitance, or a larger load resistance) decays less between peaks, so the ripple is smaller

Worked example. A half-wave rectifier fed from a 50 Hz supply has a $470 \mu\text{F}$ capacitor across its $1.2 \text{ k}\Omega$ load. Estimate the fractional fall in the output between peaks, and say how it changes with a bridge rectifier.

The peaks are $T = 1/50 = 20 \text{ ms}$ apart (half-wave: one peak per cycle). The time constant is $RC = (1.2 \times 10^3)(470 \times 10^{-6}) = 0.56 \text{ s}$. Between peaks the capacitor discharges to $V_0 e^{-t/RC} = V_0 e^{-0.020/0.56} = 0.965 V_0$, a fall of about 3.5%. With full-

wave rectification the peaks are 10 ms apart, so the fall is only 1.8%; doubling the capacitance would halve it again. Because $t \ll RC$ the fall is approximately $V_0 t/(RC)$: the ripple is proportional to the time between peaks and inversely proportional to both R and C . (A network of capacitors across the output combines by the rules of Topic 19 before it is used here.)

■ **What reduces the ripple**

- **larger** $C \rightarrow$ more stored charge $\rightarrow$ smaller dip between peaks $\rightarrow$ smaller ripple.
- **larger** $R \rightarrow$ smaller load current $\rightarrow$ slower discharge $\rightarrow$ smaller ripple.
- **higher rectified frequency** (full-wave is twice the input) $\rightarrow$ less time to discharge between peaks $\rightarrow$ smaller ripple.

In short, a large RC compared with the time between peaks gives a smoother output.

Sketching the smoothed output. Draw the unsmoothed humps faintly first. The smoothed curve **touches each peak**, then falls along a gentle curve (steepest just after the peak) until the next hump rises to meet it, where it turns sharply upwards and follows the hump to the peak. It never falls to zero, and it never rises above the peak. For half-wave rectification the decay has to last through the missing half-cycle as well, so the ripple is about twice that of full-wave for the same RC . If the question changes C or R , redraw on the same axes: a larger RC hugs the peak line more closely; a smaller RC sags further.

■ **Purpose in summary**

The smoothing capacitor reduces the ripple, giving a steadier d.c. voltage suitable for sensitive electronics.

Definitions the examiner accepts

A definition question is marked against fixed wording. Learn these exactly, and give one answer only.

Term	Definition
alternating current	a current that reverses its direction periodically (varies sinusoidally with time about zero)
period	the time for one complete cycle
frequency	the number of complete cycles per unit time
peak value	the maximum value of the current or voltage in a cycle
r.m.s. value	the value of the direct (steady) current that would dissipate the same power in the same resistor
rectification	the conversion of an alternating current into a direct (one-direction) current

Term	Definition
half-wave rectification	only one half of each cycle is passed to the output; the other half is blocked
full-wave rectification	both halves of each cycle appear at the output in the same direction
smoothing	using a capacitor across the load to reduce the variation (ripple) of a rectified output

Exam tips

- $V = V_0 \sin \omega t$ with $\omega = 2\pi f$ in radians per second: read V_0 and ω straight off the equation; radian mode for any time calculation.
- $I_{\text{r.m.s.}} = I_0/\sqrt{2}$ and $V_{\text{r.m.s.}} = V_0/\sqrt{2}$ for a **sine wave only**; otherwise square, average, root. Quoted mains values are r.m.s.; components are rated for the peak.
- Mean power in a resistor is $I_{\text{r.m.s.}}^2 R = V_{\text{r.m.s.}}^2 / R = \frac{1}{2} I_0^2 R$, half the peak power; the mean **current** is zero, the mean **power** is not.
- One diode in series gives half-wave rectification; a four-diode bridge gives full-wave, with the load current always in the same direction and the output at twice the input frequency.
- Smoothing: capacitor **across the load**; ripple falls with a larger C , a larger R (smaller load current) and a higher rectified frequency, because the decay between peaks is $V_0 e^{-t/RC}$.
- Sketches are marked on shape: humps that touch the peak line, a decay that never reaches zero, flat zero gaps for half-wave, none for full-wave.

■ **Common mistakes**

- Using the peak value in a power calculation, or the r.m.s. value as the amplitude in $V = V_0 \sin \omega t$.
- Writing $\omega = f$ or $\omega = 2\pi/f$; it is $2\pi f = 2\pi/T$.
- Defining the r.m.s. value as "the peak divided by $\sqrt{2}$ ", or leaving out "same power" and "same resistor".
- Applying $I_0/\sqrt{2}$ to a square or triangular wave.
- Drawing a diode backwards, or a bridge in which two diodes joined to the same output terminal point opposite ways.
- Putting the smoothing capacitor in series with the load.
- A smoothed output sketched falling to zero between peaks, or rising above the peak.
- Saying a larger load resistance gives a larger ripple; a larger R means a smaller current, a slower discharge and a **smaller** ripple.

- Stating that full-wave rectification gives a steady d.c.; without a capacitor it is a series of humps with a large ripple.