

Exercise walk-through

# 10.1.1

## e.m.f., internal resistance and the V-I graph

---

A-Level Physics

## You must be able to

- recall, draw and interpret the standard **circuit symbols** 电路符号 and circuit diagrams
- define the e.m.f. of a source as the **energy transferred per unit charge** in driving charge round a complete circuit
- distinguish between e.m.f. and potential difference in terms of energy
- understand the effect of the internal resistance of a source on the terminal potential difference

1


The method

---

## Method — The symbols, and how a diagram is marked

- Draw with a **ruler**, with straight wires and square corners; a wire that simply ends is a lost mark.
- An **ammeter** goes **in series** with the component whose current you want; a **voltmeter** goes **in parallel** across the component whose p.d. you want. Swapping them is the commonest diagram error.
- Junctions that are connected get a **dot**; wires that cross without connecting do not.
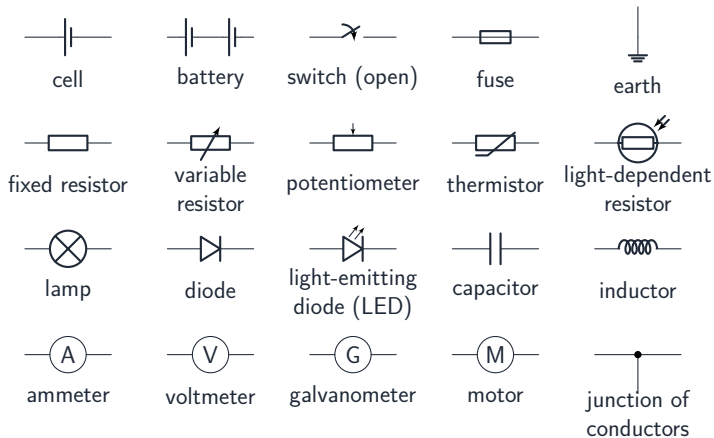
# Method — The symbols, and how a diagram is marked



## Method — Two definitions, and they differ only in direction

| definition                                 |                                                                                                                                     | where the energy goes                                              |
|--------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------|
| <b>electromotive force</b><br>(e.m.f.) $E$ | the energy transferred <b>to</b> each unit of charge, from some other form into electrical, in driving it around a complete circuit | chemical $\rightarrow$ electrical, inside the source               |
| <b>p.d.</b> $V$                            | the energy transferred <b>from</b> each unit of charge into another form, in a component                                            | electrical $\rightarrow$ thermal, light, kinetic, in the component |

- Both are **joules per coulomb**, so both are measured in **volts**. That is why the distinction has to be made in words about **energy**, and why “e.m.f. is the voltage of the battery” earns nothing.
- E.m.f. is **not a force**, despite its name.

## Method — A real cell: an ideal source with a resistance in series

Follow one coulomb round the circuit:

$$E = V + Ir \quad \Longleftrightarrow \quad V = E - Ir \quad \Longleftrightarrow \quad E = I(R + r)$$

- It is given  $E$  joules by the source.
- It gives up  $Ir$  joules **inside** the cell, warming it – these are sometimes called the “lost volts”.
- It gives up  $V$  joules **outside**, in the rest of the circuit.  $V$  is the **terminal p.d.**: what the circuit actually receives.

Two limiting cases the exam likes:

| situation                     | what happens                                                                                                   |
|-------------------------------|----------------------------------------------------------------------------------------------------------------|
| no current drawn ( $I = 0$ )  | $V = E$ : the terminal p.d. <b>equals</b> the e.m.f., because nothing is lost inside                           |
| terminals shorted ( $R = 0$ ) | $I = \frac{E}{r}$ , the <b>largest current</b> the cell can deliver, and all of the energy is wasted inside it |

## Method — A real cell: an ideal source with a resistance in series

*Worked example. A cell of e.m.f. 1.5 V and internal resistance 0.50  $\Omega$  is connected to a 2.5  $\Omega$  resistor. Find the current and the terminal p.d.*

- the e.m.f. drives the current through **both** resistances


$$I = \frac{E}{R + r} = \frac{1.5 \text{ V}}{2.5 \Omega + 0.50 \Omega} = 0.50 \text{ A}$$

- then the terminal p.d. is what is left after the internal drop

$$V = E - Ir = 1.5 \text{ V} - 0.50 \text{ A} \times 0.50 \Omega = \mathbf{1.25 \text{ V}}$$

## Method — A real cell: an ideal source with a resistance in series

Find the current and the terminal p.d

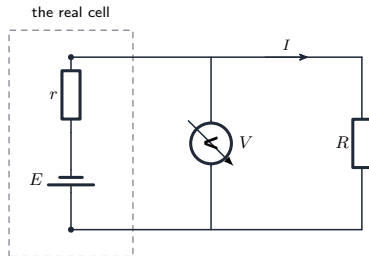

$V$  is the **terminal p.d.**:  
what the rest of the  
circuit actually receives

Each coulomb is given  $E$  joules by the source, gives up  $Ir$  joules inside the cell and  $V$  joules outside it, so  $E = V + Ir$ , or  $V = E - Ir$ . Nothing is lost – the missing energy is dissipated *inside* the cell, which is why a battery gets warm.

## Method — The experiment: one graph, two answers

Vary the external resistance, record  $V$  and  $I$  each time, and plot  $V$  against  $I$ . Since


$$V = E - rI$$

is  $y = c + mx$ :

- the **intercept** on the  $V$  axis is the **e.m.f.**  $E$ ;
- the **gradient** is  $-r$ , so the internal resistance is **minus** the gradient, and it is positive.
- This is how an e.m.f. is measured, because a real voltmeter always draws a **small current**, so the reading straight across the cell is always slightly **less** than  $E$ . The graph extrapolates to the  $I = 0$  case that cannot quite be reached.
- **Power:** the source supplies  $EI$  in total, of which  $I^2r$  is wasted inside and  $VI$  is delivered outside.
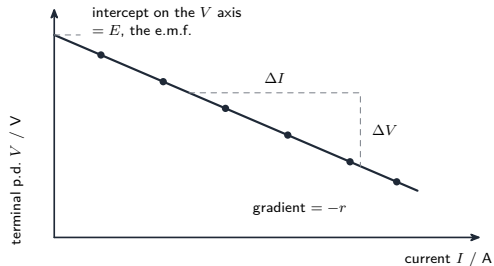
## Method — The experiment: one graph, two answers

Vary the external resistance, record ... and ... each time, and plot ... against ... .



Vary the external resistance, plot  $V$  against  $I$ , and  $V = E - Ir$  gives a straight line: the **intercept** is the e.m.f. and the **gradient** is minus the internal resistance. Extrapolating back to  $I = 0$  is how you measure an e.m.f. you can never read directly, because any real voltmeter draws some current.

2

Practice

---

## Practice 2.1 ■ 2 marks

Define the **e.m.f.** of a source.

## Solution 2.1

### Worked steps

- the **energy transferred to each unit of charge** from another form into electrical form **B1**
- in driving that charge **around a complete circuit** **B1**

## Practice 2.2 ■ 2 marks

Explain, in terms of energy, the difference between the e.m.f. of a cell and the potential difference across a resistor.

## Solution 2.2

Method: A real cell: an ideal source with a resistance in series — p.7

### Worked steps

- the **e.m.f.** is the energy given **to** each coulomb by the source, as chemical energy becomes electrical **B1**
- the **p.d.** is the energy given **up** by each coulomb in the component, as electrical energy becomes thermal or another form **B1**

## Practice 2.3 ■ 2 marks

A cell of e.m.f.  $1.5\text{ V}$  and internal resistance  $0.40\ \Omega$  delivers a current of  $0.60\text{ A}$ . Calculate the terminal p.d.

## Solution 2.3

Method: A real cell: an ideal source with a resistance in series — p.7

### Worked steps

■ use  $V = E - Ir$  (M1)

$$V = 1.5 \text{ V} - 0.60 \text{ A} \times 0.40 \text{ } \Omega = \mathbf{1.26 \text{ V}} \quad (\text{A1})$$

## Practice 2.4 ■ 2 marks

Explain why the terminal p.d. of a cell falls as the current drawn from it increases.

## Solution 2.4

Method: A real cell: an ideal source with a resistance in series — p.7

### Worked steps

- a larger current means a larger p.d.  $Ir$  across the **internal resistance** (B1)
- the e.m.f. is fixed, so with more of it used inside the cell, less is left for the external circuit and  $V = E - Ir$  falls (B1)

## Practice 2.5 ■ 2 marks

State the terminal p.d. of a cell when **no** current is drawn from it, and explain your answer.

## Solution 2.5

Method: A real cell: an ideal source with a resistance in series — p.7

### Worked steps

- the terminal p.d. **equals the e.m.f.** (B1)
- with  $I = 0$  there is no p.d. across the internal resistance, so nothing is lost inside the cell (B1)

## Practice 2.6 ■ 2 marks

Calculate the largest current the cell in **2.3** could deliver, and state the condition under which this happens.

## Solution 2.6

Method: A real cell: an ideal source with a resistance in series — p.7

### Worked steps

- the largest current flows when the external resistance is **zero** – the terminals are short-circuited **B1**

$$I_{\max} = \frac{E}{r} = \frac{1.5 \text{ V}}{0.40 \text{ } \Omega} = 3.75 \text{ A}$$

**B1**

3

Exam-style

---

## Exam-style 3.1 ■ 1 mark

As the current drawn from a cell increases, the terminal potential difference

- A** increases, because more energy is transferred each second.
- B** stays the same, because the e.m.f. of the cell is fixed.
- C** decreases, because more energy is dissipated in the internal resistance.
- D** decreases, because the e.m.f. of the cell falls.

## Solution 3.1

Method: A real cell: an ideal source with a resistance in series — p.7

- A increases, because more energy is transferred each second.
- B stays the same, because the e.m.f. of the cell is fixed.
- C decreases, because more energy is dissipated in the internal resistance. 
- D decreases, because the e.m.f. of the cell falls.

### Worked steps

C

- the internal resistance is unchanged, but a larger current gives a larger  $Ir$  inside the cell, so less of the fixed e.m.f. is left as terminal p.d. **B1**

## Exam-style 3.2 ■ 6 marks

A battery of e.m.f.  $12\text{ V}$  and internal resistance  $0.50\ \Omega$  is connected to a  $2.5\ \Omega$  resistor in series with a parallel combination of a  $6.0\ \Omega$  and a  $3.0\ \Omega$  resistor.

## Exam-style 3.2 (a) ■ 2 marks

Draw a circuit diagram of this arrangement, including an ammeter to measure the current from the battery and a voltmeter to measure the terminal p.d.

## Solution 3.2 (a)

Method: A real cell: an ideal source with a resistance in series — p.7

### Worked steps

- the battery, the  $2.5\ \Omega$  resistor and the parallel pair correctly in **series**, with the  $6.0\ \Omega$  and  $3.0\ \Omega$  in **parallel** with each other (B1)
- the **ammeter in series** with the battery and the **voltmeter in parallel** across its terminals, with correct symbols (B1)

## Exam-style 3.2 (b) ■ 2 marks

Calculate the total resistance of the external circuit.

## Solution 3.2 (b)

### Worked steps

---

- combine the parallel pair first **M1**

$$\frac{1}{R_p} = \frac{1}{6.0 \, \Omega} + \frac{1}{3.0 \, \Omega} = \frac{1}{2.0 \, \Omega}, \quad R_p = 2.0 \, \Omega$$

$$R_{\text{ext}} = 2.5 \, \Omega + 2.0 \, \Omega = 4.5 \, \Omega$$

**A1**

## Exam-style 3.2 (c) ■ 2 marks

Calculate the current delivered by the battery.

## Solution 3.2 (c)

## Worked steps

- the e.m.f. drives the current through the external resistance **and** the internal resistance M1

$$I = \frac{E}{R_{\text{ext}} + r} = \frac{12 \text{ V}}{4.5 \, \Omega + 0.50 \, \Omega} = 2.4 \text{ A}$$

A1

## Exam-style 3.3 ■ 11 marks

A student varied the resistance of the external circuit and recorded the terminal p.d.  $V$  and the current  $I$ .

| $I / \text{A}$ | 0.20 | 0.45 | 0.70 | 0.95 | 1.20 |
|----------------|------|------|------|------|------|
| $V / \text{V}$ | 5.72 | 5.45 | 5.18 | 4.91 | 4.64 |

## Exam-style 3.3 (a) ■ 3 marks

State the equation relating  $V$  and  $I$  for this circuit, and state what the gradient and the intercept of a graph of  $V$  against  $I$  represent.

## Solution 3.3 (a)

Method: The experiment: one graph, two answers — p.10

### Worked steps

- $V = E - Ir$  (B1)
- the **intercept** on the  $V$  axis is the **e.m.f.**  $E$  (B1)
- the **gradient** is  $-r$ , so the internal resistance is minus the gradient (B1)

## Exam-style 3.3 (b) ■ 3 marks

Use the first and last pairs of readings to calculate the internal resistance of the source.

## Solution 3.3 (b)

## Worked steps

- the internal resistance is minus the gradient of  $V$  against  $I$  **M1**

$$\text{gradient} = \frac{4.64 \text{ V} - 5.72 \text{ V}}{1.20 \text{ A} - 0.20 \text{ A}} = -1.08 \Omega \quad \text{M1}$$

$$r = 1.08 \Omega \quad \text{A1}$$

## Exam-style 3.3 (c) ■ 2 marks

Calculate the e.m.f. of the source.

## Solution 3.3 (c)

## Worked steps

- substitute one pair of readings into  $E = V + Ir$  **M1**

$$E = 5.72 \text{ V} + 0.20 \text{ A} \times 1.08 \text{ } \Omega = \mathbf{5.94 \text{ V}}$$

**A1**

## Exam-style 3.3 (d) ■ 2 marks

Calculate the power dissipated inside the source when the current is 1.20 A.

## Solution 3.3 (d)

## Worked steps

- the power dissipated inside the source is  $I^2 r$  **M1**

$$P = (1.20 \text{ A})^2 \times 1.08 \Omega = \mathbf{1.6 \text{ W}}$$

**A1**

## Exam-style 3.3 (e) ■ 1 mark

Explain why connecting a voltmeter directly across the terminals of the source does not give exactly its e.m.f.

## Solution 3.3 (e)

### Worked steps

- a real voltmeter draws a small current, so there is a small p.d.  $Ir$  inside the cell and the reading is slightly **less** than the e.m.f. B1