

Exercise walk-through

10.2.1

Kirchhoff's laws, deriving the resistor formulae and solving networks

A-Level Physics

You must be able to

- recall **Kirchhoff's first law** 基尔霍夫第一定律 and understand that it is a consequence of **conservation of charge** 电荷守恒
- recall **Kirchhoff's second law** 基尔霍夫第二定律 and understand that it is a consequence of **conservation of energy** 能量守恒
- derive, using Kirchhoff's laws, a formula for the combined resistance of two or more resistors in **series**
- use the formula for the combined resistance of two or more resistors in series
- derive, using Kirchhoff's laws, a formula for the combined resistance of two or more resistors in **parallel**
- use the formula for the combined resistance of two or more resistors in parallel
- use Kirchhoff's laws to solve simple circuit problems


1

The method

Method — The two laws, and what each one conserves

- **First law.** At any **junction** 节点, the total current in equals the total current out. Charge cannot pile up at a point, so this is conservation of charge.
- **Second law.** Round any closed loop, the total **electromotive force** 电动势 equals the total p.d. across the components. A unit of charge gives up exactly the energy it gained, so this is conservation of energy.
- The pairing is examined almost every session, and the two are easy to swap. First law $\rightarrow$ charge. Second law $\rightarrow$ energy.

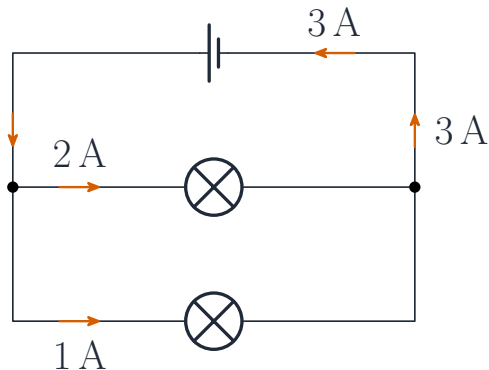Method — The two laws, and what each one conserves



at each junction: $3\text{ A} = 2\text{ A} + 1\text{ A}$


Method — Deriving the series formula

A derivation must name the law at each step; that is what earns the marks.

- 1 There is no junction between the resistors, so by the **first law** the same current I is in both.
- 2 By the **second law**, the p.d. across the combination is the sum of the p.d.s:
 $V = V_1 + V_2$.
- 3 Each p.d. is IR , so $IR = IR_1 + IR_2$.
- 4 Divide every term by I : $R = R_1 + R_2$.

Method — Deriving the series formula

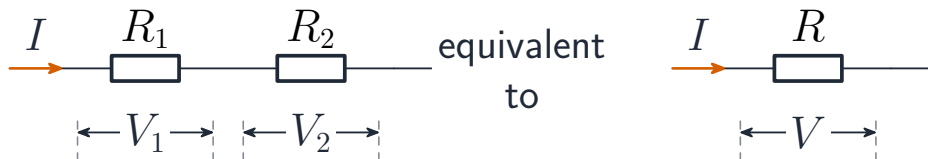
A derivation must name the law at each step; that is what earns the marks



Method — Deriving the parallel formula

- 1 Each resistor forms its own loop with the source, so by the **second law** the same p.d. V is across both.
- 2 By the **first law** the current arriving at the junction is shared: $I = I_1 + I_2$.
- 3 Each current is V/R , so $\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$.
- 4 Divide every term by V : $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$.

Method — Deriving the parallel formula

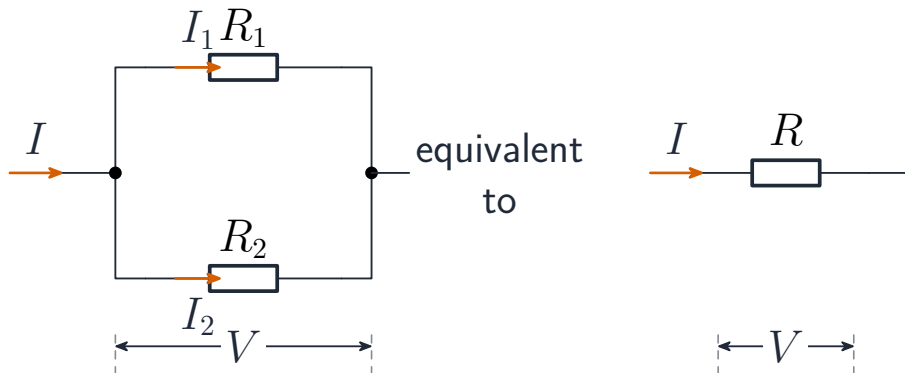


Method — Reducing a network one step at a time

Never try to see the whole network at once. Replace one group, redraw, repeat.

- 1 The parallel pair: $\frac{1}{R_p} = \frac{1}{12} + \frac{1}{6.0} = \frac{1}{12} + \frac{2}{12} = \frac{3}{12}$, so $R_p = 4.0 \, \Omega$.
 - 2 What is left is three resistances in series: $5.0 + 4.0 + 3.0$.
 - 3 $R_{XY} = 12 \, \Omega$.
- For **two** resistors only, $R_p = \frac{R_1 R_2}{R_1 + R_2}$ is quicker. It is wrong for three.
 - A parallel combination is always **smaller** than its smallest resistor; a series one is always larger than its largest. Use that to check every answer.

Method — Reducing a network one step at a time

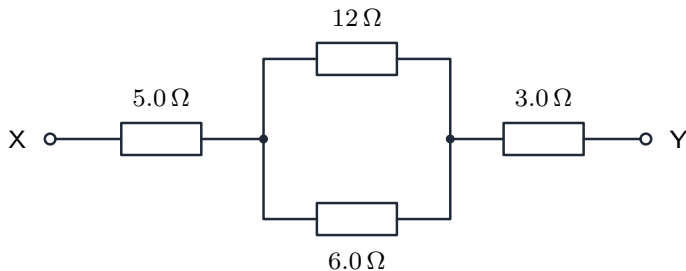Never try to see the whole network at once.



Method — Which component dissipates the most power

Two rules settle this with no arithmetic at all, and which one applies depends on what the components share.

- **Same current** (in series): $P = I^2 R$, so the **larger** resistance dissipates more.

- **Same p.d.** (in parallel): $P = \frac{V^2}{R}$, so the **smaller** resistance dissipates more.

A $4.0 \, \Omega$ and an $8.0 \, \Omega$ resistor are joined to a $12 \, \text{V}$ supply of negligible internal resistance.

1 **In series:** $R = 12 \, \Omega$, so $I = 1.0 \, \text{A}$ in both. $P_4 = (1.0)^2(4.0) = 4.0 \, \text{W}$ and $P_8 = (1.0)^2(8.0) = 8.0 \, \text{W}$ – the larger resistor wins.

2 **In parallel:** both have $12 \, \text{V}$ across them. $P_4 = \frac{12^2}{4.0} = 36 \, \text{W}$ and

$P_8 = \frac{12^2}{8.0} = 18 \, \text{W}$ – now the smaller resistor wins.

Method — Which component dissipates the most power

- In a mixed circuit, the resistor carrying the **whole** current usually dissipates the most, because every parallel branch carries only a share of it.


Method — A loop with two cells that oppose

The second law handles this with no extra ideas: go once round the loop and add the e.m.f.s with their signs.

- 1 The cells are connected the opposite way round, so the net e.m.f. is $9.0 - 4.5 = 4.5 \text{ V}$.
- 2 The two **internal resistances** 内阻 are in series with the resistor:
 $R_{\text{total}} = 1.5 + 0.50 + 4.0 = 6.0 \ \Omega$.
- 3 $I = \frac{4.5}{6.0} = \mathbf{0.75 \text{ A}}$, driven the way the larger e.m.f. pushes.
- 4 The terminal p.d. of the 9.0 V cell is $\varepsilon - Ir = 9.0 - (0.75)(1.5) = \mathbf{7.9 \text{ V}}$.
 - The smaller cell is being driven backwards, so it is charging; its terminal p.d. is $4.5 + (0.75)(0.50)$, which is *larger* than its e.m.f.

Method — A loop with two cells that oppose

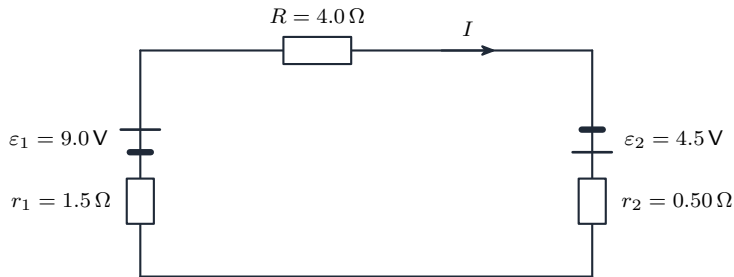The second law handles this with no extra ideas: go once round the loop and add the e.m.f.s with their signs



2

Practice

Practice 2.1 ■ 2 marks

Calculate the combined resistance of $2.0\ \Omega$, $3.0\ \Omega$ and $6.0\ \Omega$ connected in parallel.

Solution 2.1

Worked steps

$$\blacksquare \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \text{M1}$$

$$\frac{1}{R} = \frac{1}{2.0} + \frac{1}{3.0} + \frac{1}{6.0} = \frac{3}{6.0} + \frac{2}{6.0} + \frac{1}{6.0} = 1.0 \Rightarrow R = \mathbf{1.0 \, \Omega} \quad \text{A1}$$

- the answer is smaller than the smallest resistor, as it must be

Practice 2.2 ■ 3 marks

For the network between X and Y in the worked example above, the $12\ \Omega$ resistor is replaced by a second $6.0\ \Omega$ resistor. Calculate the new resistance between X and Y.

Solution 2.2

Worked steps

- the parallel pair is now two equal resistors, so $R_p = \frac{6.0}{2} = 3.0 \, \Omega$ **M1** **A1**
- in series with the others: $R_{XY} = 5.0 + 3.0 + 3.0 = 11 \, \Omega$ **A1**

Practice 2.3 ■ 2 marks

Explain why connecting a second resistor in parallel with the first always **decreases** the resistance between the same two points.

Solution 2.3

Worked steps

- the second resistor gives the charge an extra path, so for the same p.d. the total current is larger **B1**
- $R = V/I$, so a larger current for the same p.d. means a smaller resistance **B1**

Practice 2.4 ■ 2 marks

A $4.0\ \Omega$ and an $8.0\ \Omega$ resistor are connected in **series** across a supply. State which dissipates the greater power, and by what factor.

Solution 2.4

Method: Which component dissipates the most power — p.12

Worked steps

- in series the current is the same in both, and $P = I^2 R$ **B1**
- the $8.0 \, \Omega$ resistor, dissipating **twice** the power of the $4.0 \, \Omega$ **B1**

Practice 2.5 ■ 2 marks

The same two resistors are now connected in **parallel** across the same supply. State which dissipates the greater power, and explain why the answer has changed.

Solution 2.5

Method: Which component dissipates the most power — p.12

Worked steps

- in parallel the p.d. is the same across both, and $P = V^2/R$, so the 4.0Ω resistor dissipates the greater power **B1**
- the answer changes because the resistors now share the p.d. instead of the current **B1**

3

Exam-style

Exam-style 3.1 ■ 1 mark

A $6.0\ \Omega$ resistor and a $3.0\ \Omega$ resistor are connected in parallel. This combination is in series with a $4.0\ \Omega$ resistor across a supply of e.m.f. $12\ \text{V}$ and negligible internal resistance. What is the current from the supply?

A $0.50\ \text{A}$

B $1.0\ \text{A}$

C $2.0\ \text{A}$

D $3.0\ \text{A}$

Solution 3.1

Method: Which component dissipates the most power — p.12

A 0.50 A

B 1.0 A

C 2.0 A



D 3.0 A

Worked steps

C

■ parallel pair: $\frac{1}{R_p} = \frac{1}{6.0} + \frac{1}{3.0} = \frac{1}{2.0}$, so $R_p = 2.0 \, \Omega$ **B1**

Solution 3.1

- total = $4.0 + 2.0 = 6.0 \, \Omega$, so $I = \frac{12}{6.0} = 2.0 \, \text{A}$

Exam-style 3.2 ■ 4 marks

Two resistors of resistances R_1 and R_2 are connected in parallel. Use Kirchhoff's laws to show that the combined resistance R is given by

$$R = \frac{R_1 R_2}{R_1 + R_2}.$$

Name the law used at each step.

Solution 3.2

Method: Reducing a network one step at a time — p.10

Worked steps

- by **Kirchhoff's second law** each resistor is in its own loop with the source, so the same p.d. V is across both **B1**
- by **Kirchhoff's first law** the currents at the junction add: $I = I_1 + I_2$ **B1**
- substitute $I = V/R$ for each: $\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$, so $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ **M1**
- put the right-hand side over a common denominator and invert:

$$\frac{1}{R} = \frac{R_2 + R_1}{R_1 R_2} \Rightarrow R = \frac{R_1 R_2}{R_1 + R_2}$$

A1

Exam-style 3.3 ■ 9 marks

A battery of e.m.f. 18 V and negligible internal resistance is connected to a $6.0\ \Omega$ resistor in series with a parallel combination of a $9.0\ \Omega$ resistor and an $18\ \Omega$ resistor.

Exam-style 3.3 (a) ■ 2 marks

Show that the resistance of the parallel combination is $6.0 \, \Omega$.

Solution 3.3 (a)

Method: Which component dissipates the most power — p.12

Worked steps

$$\frac{1}{R_p} = \frac{1}{9.0} + \frac{1}{18} = \frac{2}{18} + \frac{1}{18} = \frac{3}{18} \quad \text{M1}$$

$$\blacksquare R_p = \frac{18}{3} = 6.0 \, \Omega \quad \text{A1}$$

Exam-style 3.3 (b) ■ 2 marks

Calculate the current in the battery.

Solution 3.3 (b)

Worked steps

$$\text{total resistance} = 6.0 + 6.0 = 12 \, \Omega \quad \text{M1}$$

$$I = \frac{18}{12} = 1.5 \, \text{A} \quad \text{A1}$$

Exam-style 3.3 (c) ■ 3 marks

Calculate the p.d. across the parallel combination and the current in each of its branches.

Solution 3.3 (c)

Worked steps

$$V_p = IR_p = (1.5)(6.0) = \mathbf{9.0\ V} \quad \text{M1 A1}$$

$$\blacksquare I_9 = \frac{9.0}{9.0} = \mathbf{1.0\ A} \text{ and } I_{18} = \frac{9.0}{18} = \mathbf{0.50\ A} \quad \text{A1}$$

■ check: $1.0 + 0.50 = 1.5\ \text{A}$, the current in the battery

Exam-style 3.3 (d) ■ 2 marks

State, with a reason, which of the three resistors dissipates the greatest power.

Solution 3.3 (d)


Worked steps

the $6.0\ \Omega$ resistor **B1**

- it carries the whole 1.5 A while each branch carries only part of it, and $P = I^2 R$: 13.5 W against 9.0 W and 4.5 W **B1**


Exam-style 3.4 ■ 10 marks

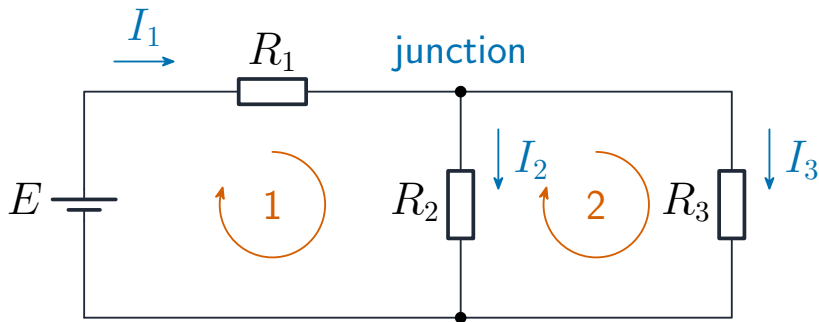A cell of e.m.f. 12 V and negligible internal resistance is connected to $R_1 = 3.0\ \Omega$ in series with a parallel combination of $R_2 = 12\ \Omega$ and $R_3 = 4.0\ \Omega$, as shown.



Exam-style 3.4 (a) ■ 1 mark

Write down the equation that Kirchhoff's first law gives for the junction.

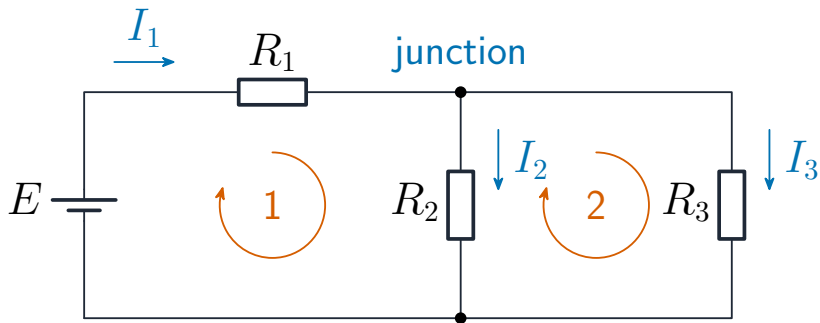

Solution 3.4 (a)


Method: The two laws, and what each one conserves — p.4

Worked steps

$$I_1 = I_2 + I_3 \quad \text{B1}$$

Exam-style 3.4 (b) ■ 4 marks

Calculate the current I_1 in the cell and the currents I_2 and I_3 in the two branches.

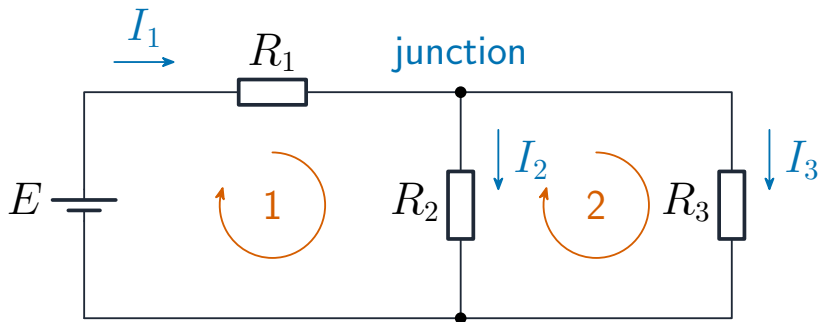

Solution 3.4 (b)

Worked steps

parallel pair: $\frac{1}{R_p} = \frac{1}{12} + \frac{1}{4.0} = \frac{1}{12} + \frac{3}{12} = \frac{4}{12}$, so $R_p = 3.0 \, \Omega$ **M1**


■ total = $3.0 + 3.0 = 6.0 \, \Omega$, so $I_1 = \frac{12}{6.0} = \mathbf{2.0 \, A}$ **A1**

■ p.d. across the pair = $(2.0)(3.0) = 6.0 \, \text{V}$ **M1**

■ $I_2 = \frac{6.0}{12} = \mathbf{0.50 \, A}$ and $I_3 = \frac{6.0}{4.0} = \mathbf{1.5 \, A}$ **A1**

Exam-style 3.4 (c) ■ 2 marks

Calculate the p.d. across R_1 .

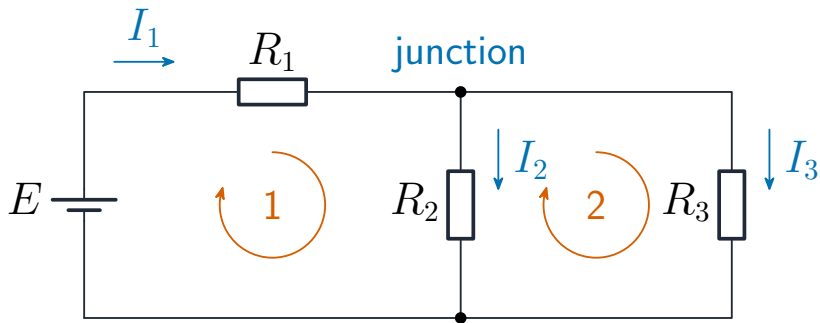

Solution 3.4 (c)

Worked steps


$$V_1 = I_1 R_1 \quad \text{M1}$$

$$V_1 = (2.0)(3.0) = \mathbf{6.0 \text{ V}}$$

A1

Exam-style 3.4 (d) ■ 3 marks

Show that the total power dissipated in the three resistors equals the power supplied by the cell, and state which conservation law this illustrates.

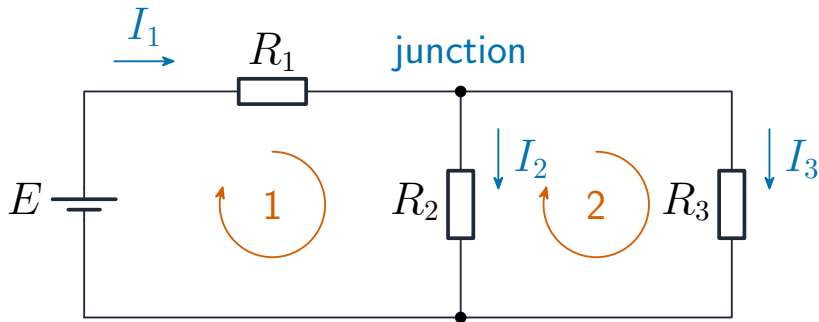

Solution 3.4 (d)

Worked steps

$P = I^2 R$ for each resistor M1

■ $P_1 = (2.0)^2(3.0) = 12 \text{ W}$, $P_2 = (0.50)^2(12) = 3.0 \text{ W}$,

$P_3 = (1.5)^2(4.0) = 9.0 \text{ W}$, total = **24 W** A1

- the cell supplies $\varepsilon I_1 = (12)(2.0) = 24 \text{ W}$, the same, illustrating **conservation of energy** – which is what Kirchhoff's second law expresses B1