

Exercise walk-through

Kirchhoff's laws ■ 10.2

eXercise

You must be able to


- state both **Kirchhoff's laws** and the conservation law each follows from
- combine resistors in **series** and **parallel**
- analyse a **combined** circuit: total resistance, total current, then each **branch** current and p.d.

Method — Kirchhoff's laws

First law (junction): current **in** = **current out** — from conservation of **charge**:

Second law (loop): around any closed loop, the **total e.m.f.** = **total p.d.** — from conservation of **energy**.

Method — Kirchhoff's laws

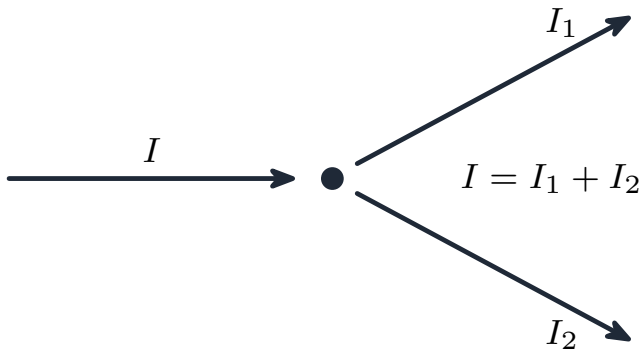

Method — Combining resistors

■ **Series** (same current): $R = R_1 + R_2 + \dots$

■ **Parallel** (same p.d.): $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

Worked example. $3.0\ \Omega$ and $6.0\ \Omega$ in parallel: $\frac{1}{R} = \frac{1}{3.0} + \frac{1}{6.0} = \frac{1}{2.0}$, so $R = 2.0\ \Omega$.

Method — Analysing a combined circuit

Real exam circuits mix series and parallel. Work in **steps**: collapse the parallel part, find the total current, then split it.

Worked example. $\varepsilon = 12 \text{ V}$ (negligible internal resistance), $R_1 = 4.0 \text{ } \Omega$ in series with $R_2 = 6.0 \text{ } \Omega$ and $R_3 = 3.0 \text{ } \Omega$ in parallel.


1 Parallel pair: $\frac{1}{R_p} = \frac{1}{6.0} + \frac{1}{3.0} = \frac{1}{2.0}$, so $R_p = 2.0 \text{ } \Omega$.

2 Total: $R = R_1 + R_p = 4.0 + 2.0 = 6.0 \text{ } \Omega$; current $I = \frac{\varepsilon}{R} = \frac{12}{6.0} = 2.0 \text{ A}$.

3 P.d. across the parallel part: $V_p = IR_p = 2.0 \times 2.0 = 4.0 \text{ V}$.

4 Branch currents: $I_2 = \frac{V_p}{R_2} = \frac{4.0}{6.0} = 0.67 \text{ A}$, $I_3 = \frac{V_p}{R_3} = \frac{4.0}{3.0} = 1.33 \text{ A}$ (check: $0.67 + 1.33 = 2.0 \text{ A } \checkmark$).

Method — Analysing a combined circuit

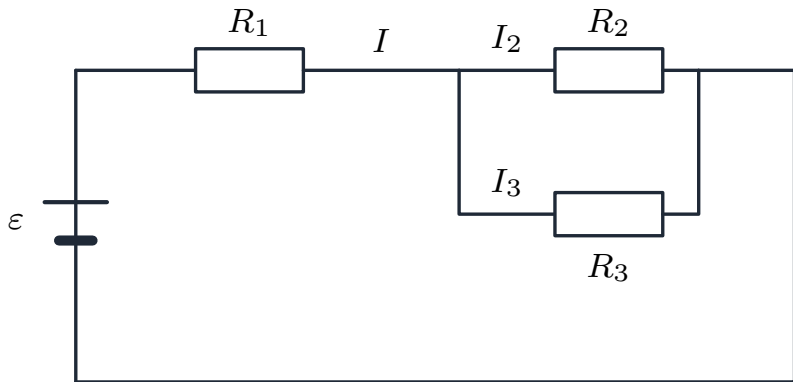

Practice 2.1 ■ 2 marks

State **Kirchhoff's first law** and which conservation law it follows from.

Solution 2.1

Method: Kirchhoff's laws

Worked steps

The **total current into a junction equals the total current out**; it follows from conservation of **charge** [B1](#) [B1](#).

Practice 2.2 ■ 2 marks

State **Kirchhoff's second law** and which conservation law it follows from.

Solution 2.2

Method: Kirchhoff's laws

Worked steps

Around any closed loop, the **total e.m.f. equals the total p.d.**; it follows from conservation of **energy** **B1** **B1**.

Practice 2.3 ■ 1 mark

Find the combined resistance of $4.0\ \Omega$ and $6.0\ \Omega$ in **series**.

Solution 2.3

Method: Analysing a combined circuit

Worked steps

$$R = 4.0 + 6.0 = 10 \, \Omega \quad \text{B1}.$$

Practice 2.4 ■ 2 marks

Find the combined resistance of two $4.0\ \Omega$ resistors in **parallel**.

Solution 2.4

Method: Analysing a combined circuit

Worked steps

$$\frac{1}{R} = \frac{1}{4.0} + \frac{1}{4.0} = \frac{1}{2.0} \quad \text{M1}, \text{ so } R = 2.0 \, \Omega \quad \text{A1}.$$

Exam-style 3.1 ■ 1 mark

Three $6.0\ \Omega$ resistors in **parallel** have a combined resistance of:

A $2.0\ \Omega$

B $6.0\ \Omega$

C $18\ \Omega$

D $0.50\ \Omega$

Solution 3.1

Method: Analysing a combined circuit

A $2.0\ \Omega$



B $6.0\ \Omega$

C $18\ \Omega$

D $0.50\ \Omega$

Worked steps

A — $6.0/3 = 2.0\ \Omega$.

Exam-style 3.2 ■ 4 marks

A 12 V battery drives current through a $3.0\ \Omega$ and a $6.0\ \Omega$ resistor in **series**. Calculate the current and the p.d. across each resistor.

Solution 3.2

Method: Analysing a combined circuit

Worked steps

$R = 3.0 + 6.0 = 9.0 \, \Omega$ **M1**; $I = 12/9.0 = 1.33 \, \text{A}$ **A1**; $V_3 = IR = 1.33 \times 3.0 = 4.0 \, \text{V}$, $V_6 = 1.33 \times 6.0 = 8.0 \, \text{V}$ **A1** **A1**.

Exam-style 3.3 ■ 3 marks

A battery of e.m.f. 6.0 V and negligible internal resistance is connected to $R_1 = 2.0\ \Omega$ in series with two resistors $R_2 = 4.0\ \Omega$ and $R_3 = 4.0\ \Omega$ in **parallel** (as in the worked example).

- (a) Calculate the total resistance and the current from the battery.
- (b) Calculate the current in **each** of R_2 and R_3 .

Solution 3.3

Method: Analysing a combined circuit

Worked steps

(b) $V_p = IR_p = 1.5 \times 2.0 = 3.0 \text{ V}$ **M1**; each branch $I = \frac{3.0}{4.0} = 0.75 \text{ A}$ **A1**, and the two are equal because $R_2 = R_3$ **A1**.

Exam-style 3.4 ■ 1 mark

At a junction, 5.0 A enters and one branch carries 2.0 A away. Find the current in the other branch.

Solution 3.4

Method: Analysing a combined circuit

Worked steps

$$5.0 - 2.0 = 3.0 \text{ A } \text{B1}.$$