

Past-paper walk-through

Potential dividers ■ 10.3

eXercise

Questions in this set

- 9702/12 N25 Q35 ■ 1 mark
- 9702/12 N25 Q36 ■ 1 mark
- 9702/14 J25 Q36 ■ 1 mark

Question 35

9702/12 N25 ■ Q35 ■ 1 mark

The diagram shows a circuit with a battery of electromotive force (e.m.f.) 60 V and negligible internal resistance, a 20 k Ω resistor, a thermistor and a voltmeter. The resistance of the thermistor is 20 k Ω .

The temperature of the thermistor decreases, and this causes its resistance to change by 50%.

After this change, what is the reading on the voltmeter?

[1]**A** 20 V**B** 24 V**C** 36 V**D** 40 V

Solution 35

A 20 V

B 24 V



C 36 V

D 40 V

Why

- A thermistor's resistance *rises* as it gets colder, so $20\text{ k}\Omega$ becomes $20 \times 1.5 = 30\text{ k}\Omega$.
- The two form a potential divider across 60 V, with a total of $50\text{ k}\Omega$.
- The voltmeter reads the fixed resistor's share: $60 \times 20/50 = 24\text{ V}$.

Question 36

9702/12 N25 ■ Q36 ■ 1 mark

- 36** A potentiometer circuit is used to determine the electromotive force (e.m.f.) E_x of a cell. The circuit includes a second cell of known e.m.f. E_0 and negligible internal resistance, and a uniform resistance wire PQ of known length.

E_x is less than E_0 .


The movable connection J can be positioned anywhere along the length of the resistance wire.

Which circuit is suitable for determining E_x ?


A

B

Question 36


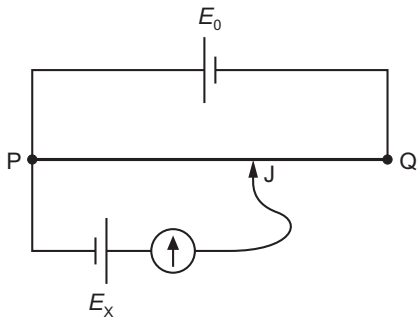


C

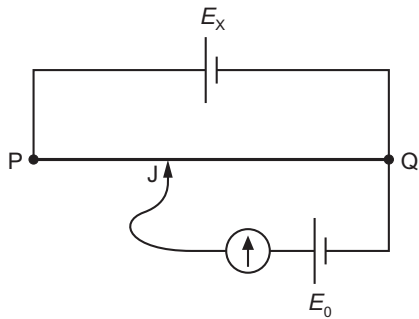

D

Question 36

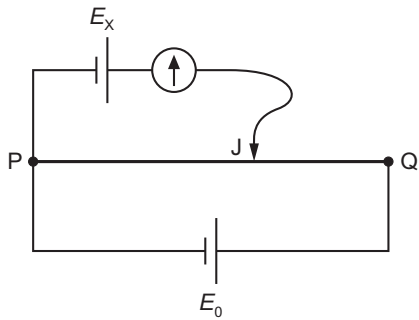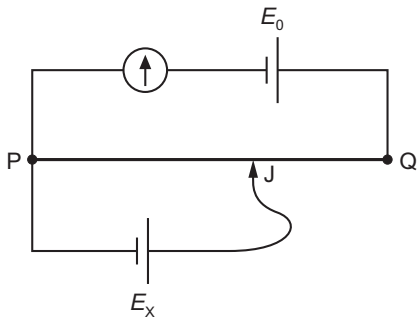

Solution 36

Answer: **D**

Why



- The known cell E_0 must drive current through the whole wire PQ, setting up a uniform potential gradient along it.
- E_X goes in the second loop with the galvanometer, from one end of the wire to the sliding contact J.
- The two cells must oppose; since $E_X < E_0$, a null point then exists somewhere along PQ.

Question 36



9702/14 J25 ■ Q36 ■ 1 mark

- 36** A potentiometer circuit may be used to determine the unknown electromotive force (e.m.f.) E of a cell. The circuit diagrams shown include a battery of known e.m.f. and negligible internal resistance, a uniform resistance wire XY and a galvanometer.

Which circuit diagram shows a suitable arrangement for determining E ?

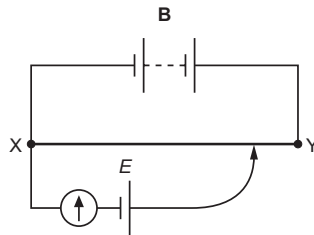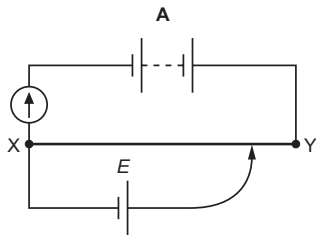

Question 36

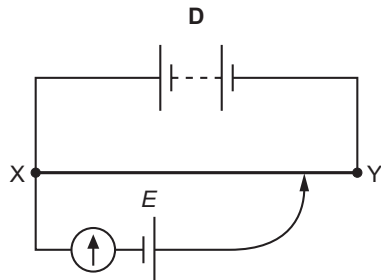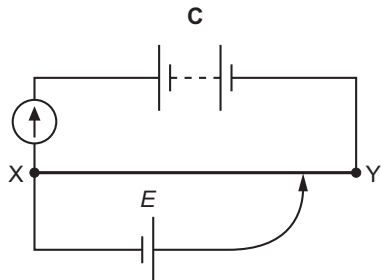

Solution 36

Answer: **B**

Why

- The driver cell must sit across the *whole* wire XY, so there is a uniform potential gradient along it.
- The unknown cell goes in the other loop, in series with the galvanometer, joined to one end of the wire and to the sliding contact.
- The two cells must oppose each other, otherwise no balance point (zero deflection) can exist.