

Past-paper walk-through

Potential difference and power ■ 9.2

eXercise

Questions in this set

- 9702/11 N25 Q31 ■ 1 mark
- 9702/12 N25 Q32 ■ 1 mark
- 9702/11 J25 Q34 ■ 1 mark
- 9702/14 J25 Q30 ■ 1 mark
- 9702/22 J25 Q6 ■ 10 marks

Reading the mark scheme

- **B1** a mark that stands on its own – the point is either made or not.
- **M1** a *method* mark: the right approach, even if the number is wrong.
- **A1** an *answer* mark, and it usually needs its M mark first.
- **C1** a working mark on the way to the answer.
- **//** separates answers the examiner accepts equally.
- **ecf** = error carried forward: a later part is marked on your own earlier answer.
- **owtte** = “or words to that effect” – the wording need not match.

Question 31

9702/11 N25 ■ Q31 ■ 1 mark

There is a potential difference V across a resistor of resistance R . The current in the resistor is I .

Which equation gives the power P dissipated by the resistor?

[1]

A $P = V^2 I$

B $P = \frac{V^2}{I}$

C $P = V^2 R$

D $P = \frac{V^2}{R}$

Solution 31

A $P = V^2 I$

B $P = \frac{V^2}{I}$

C $P = V^2 R$

D $P = \frac{V^2}{R}$



Why

- Power is $P = VI$, and Ohm's law gives $I = V/R$.
- Substituting: $P = V \times V/R = V^2/R$.
- $P = I^2 R$ is the other valid form; A and B mix the two together.

Question 32

9702/12 N25 ■ Q32 ■ 1 mark

The current in a resistor of constant resistance is 8.0 mA. The power dissipated by the resistor is P .

The current in the resistor is increased to 12.0 mA.

What is the new power dissipated by the resistor?

[1]

A $0.44P$

B $0.67P$

C $1.5P$

D $2.3P$

Solution 32

A $0.44P$

B $0.67P$

C $1.5P$

D $2.3P$



Why

- With the resistance constant, $P = I^2 R$, so the power goes as the *square* of the current.
- $(12.0/8.0)^2 = 1.5^2 = 2.25$.
- The new power is $2.3P$; C assumes it scales with I rather than I^2 .

Question 34

9702/11 J25 ■ Q34 ■ 1 mark

The diagram shows six identical resistors connected in a circuit.

In which branch of the circuit is the most power dissipated?

[1]


A PQ

B QR

C RS

D SP

Question 34

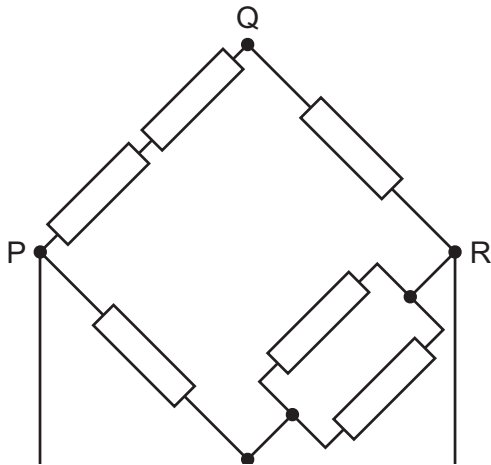

Solution 34

A PQ

B QR

C RS

D SP 

Why

- Read the branches: PQ is two resistors in series ($2R$) and RS is two in parallel ($R/2$).
- So the top path P-Q-R is $3R$ and the bottom path P-S-R is $1.5R$ – the bottom path carries twice the current.
- $P = I^2 R$, so SP (a full resistor at the larger current) dissipates $4V^2/9R$, beating PQ and RS at $2V^2/9R$.

Question 30

9702/14 J25 ■ Q30 ■ 1 mark

30 What is equivalent to one volt?

- A** one coulomb per second
- B** one joule per coulomb
- C** one joule per second

D one joule second per coulomb squared

Solution 30

Answer: **B**

Why


- Potential difference is the energy transferred per unit charge.
- So $1 \text{ V} = 1 \text{ J C}^{-1}$.
- A is the ampere, C is the watt, and D (J s C^{-2}) is the ohm.

Question 6

9702/22 J25 ■ Q6 ■ 10 marks

- (a) Define electric potential difference across a component. [1]
- (b)(i) Determine the charge passing through the battery in a time of 4.0 minutes. [2]
- (b)(ii) Calculate I_1 . [2]
- (b)(iii) Calculate I_2 . [1]
- (b)(iv) Determine R . [2]
- (c) The variable resistor in (b) is fitted with a scale so that its resistance can be accurately determined. The resistor of resistance $240\ \Omega$ is now replaced by a new resistor X of unknown resistance. A galvanometer is connected as shown in Fig. 6.2.
- Fig. 6.2
- With reference to ratios of resistances, explain how this circuit can be used to determine the resistance of X. [2]

Question 6

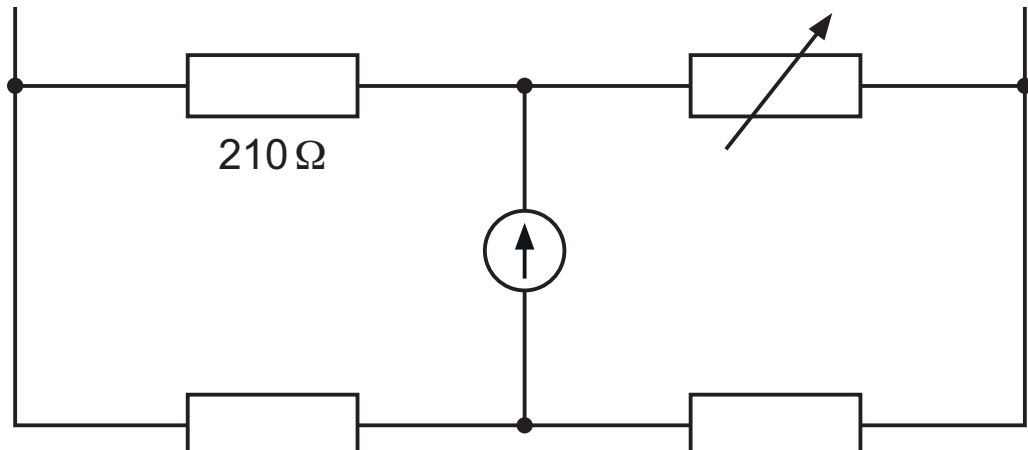

Question 6



Solution 6

(a)

Mark scheme

- energy transferred (to the component) per (unit) charge **B1**

Solution 6

(b)(i)

Worked steps

- $Q = It$, with the time in **seconds**: 4.0 minutes = 240 s.
- $Q = 0.030 \times 240$
- $Q = 7.2 \text{ C}$

Mark scheme

- $Q = It$
- $= 0.030 \times 4.0 \times 60$ (C1)
- $= 7.2 \text{ C}$ (A1)

Solution 6

(b)(ii) Worked steps

Both branches sit across the full 8.0 V, so treat each on its own.

- The two resistors in this branch are in series: $430 + 240 = 670 \, \Omega$.
- $I_1 = \frac{V}{R} = \frac{8.0}{670}$
- $I_1 = 0.012 \, \text{A}$

Solution 6

Mark scheme

- $I = V / R$
- $I_1 = 8.0 / (430+240)$ **C1**
- $= 0.012 \text{ A}$ **A1**

Solution 6

(b)(iii)

Worked steps

Kirchhoff's first law at the junction: the branch currents add up to the battery current.

- $I_2 = 0.030 - I_1 = 0.030 - 0.012$

- $I_2 = 0.018 \text{ A}$

Mark scheme

- $I_2 = 0.030 - I_1$

- $= 0.030 - 0.012$

- $= 0.018 \text{ A}$ **A1**

Solution 6

(b)(iv) Worked steps

The second branch also has 8.0 V across it, shared between the $210\ \Omega$ resistor and R.

- P.d. across the $210\ \Omega$ resistor $= 0.018 \times 210 = 3.8\ \text{V}$.
- P.d. across R $= 8.0 - 3.8 = 4.2\ \text{V}$.
- $R = \frac{4.2}{0.018}$
- $R = 230\ \Omega$

Mark scheme

- $R = V / I_2$

Solution 6

- $= (8.0 - (0.018 \times 210)) / 0.018$ (C1)
- $= 230 \Omega$ (A1)
- OR resistance of top branch $= 8.0 / 0.018$
- $R = 8.0 / 0.018 - 210$
- (C1)
- $= 230 \Omega$
- (A1)
- OR total circuit resistance $= 8.0 / 0.030 = 267$
- $1 / 267 = 1 / (210 + R) + 1 / (430 + 240)$
- $1 / 267 - 1 / 670 = 1 / (210 + R)$

Solution 6

- $210 + R = 443$
- (C1)
- $R = 230 \, \Omega$
- (A1)

Solution 6

(c) Worked steps

This is a Wheatstone bridge, and the whole method rests on one condition.

- Adjust the variable resistor until the **galvanometer reads zero**. No current then flows across the bridge, so the two junctions are at the same potential.
- That happens when the two branches divide their 8.0 V in the same ratio, i.e. when the ratio of the resistances in one branch equals the ratio in the other.
- Three of the four resistances are known (the two fixed ones and the variable one read off its scale), so X follows from that ratio.

Solution 6

Mark scheme

- (When) the galvanometer reads 0 (A) (M1)
- The ratio of the resistances in the top branch will equal the ratio of the resistances in the bottom branch (so the resistance of X can be determined) (A1)
- OR
- The ratio of the left pair of resistances will equal the ratio of the right pair of resistances
- (A1)