

Exercise walk-through

Resistance and resistivity ■ 9.3

eXercise

You must be able to

- define **resistance** and state **Ohm's law**
- sketch the I–V graphs of a **metal wire**, a **filament lamp** and a **diode**
- use $R = \rho L/A$, getting A from a **diameter** ($A = \pi d^2/4$)
- describe the **circuit and steps** to measure the resistivity of a wire

Method — Resistance and Ohm's law


$$R = \frac{V}{I} \text{ } (\Omega).$$

Ohm's law: for a metal at constant temperature, $I \propto V$, so R is constant (a straight-line I–V graph).


Method — I–V characteristics

A **filament lamp**'s resistance **rises** as current increases: more current heats the filament, raising its temperature and resistance, so the graph flattens.


Method — I-V characteristics

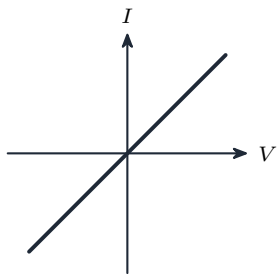

ohmic conductor

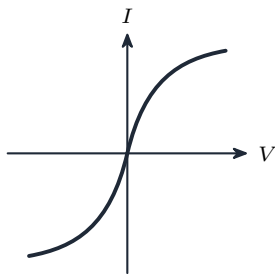

filament lamp

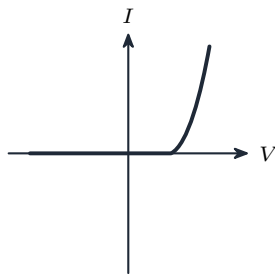

diode

Method — Resistivity, LDR, thermistor

$$R = \frac{\rho L}{A}.$$

An **LDR**'s resistance **falls** as light gets brighter; a **thermistor**'s resistance **falls** as temperature rises.

Method — Measuring resistivity


A very common experiment: find ρ for a wire. Connect an **ammeter in series** with the wire and a **voltmeter across** it:

- 1 Read V and $I \rightarrow$ resistance $R = V/I$.
- 2 Measure the **diameter** $d \rightarrow$ area $A = \pi d^2/4$ (use the radius $d/2$).
- 3 Measure the length $L \rightarrow \rho = \frac{RA}{L}$.

Worked example. $V = 1.5 \text{ V}$, $I = 0.45 \text{ A} \rightarrow R = 3.33 \Omega$. Diameter $d = 0.40 \text{ mm} \rightarrow A = \pi(0.20 \times 10^{-3})^2 = 1.26 \times 10^{-7} \text{ m}^2$. Length $L = 0.80 \text{ m}$:

$$\rho = \frac{RA}{L} = \frac{(3.33)(1.26 \times 10^{-7})}{0.80} = 5.2 \times 10^{-7} \Omega \text{ m}.$$

Method — Measuring resistivity

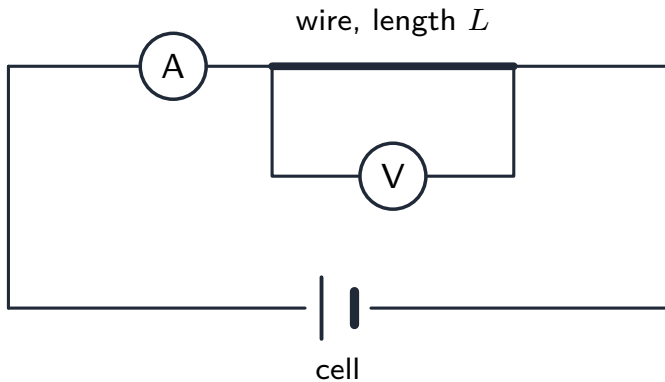

Practice 2.1 ■ 1 mark

Define **resistance**.

Solution 2.1

Worked steps

$$\text{Resistance} = \frac{\text{p.d.}}{\text{current}} \quad (R = V/I) \quad \text{B1}.$$

Practice 2.2 ■ 1 mark

State **Ohm's law**.

Solution 2.2

Worked steps

The current is **proportional** to the p.d. (at constant temperature) **B1**.

Practice 2.3 ■ 2 marks

A component has 6.0 V across it and 0.30 A through it. Find its **resistance**.

Solution 2.3

Method: Measuring resistivity

Worked steps

$$R = V/I = 6.0/0.30 = 20 \, \Omega \quad \text{M1} \quad \text{A1}.$$

Practice 2.4 ■ 2 marks

A wire has diameter 0.50 mm. Calculate its cross-sectional **area** in m^2 .

Solution 2.4

Method: Measuring resistivity

Worked steps

$$A = \frac{\pi d^2}{4} = \frac{\pi(0.50 \times 10^{-3})^2}{4} = 2.0 \times 10^{-7} \text{ m}^2 \quad \text{M1} \quad \text{A1}.$$

Practice 2.5 ■ 1 mark

State what happens to a **thermistor's** resistance as its temperature **rises**.

Solution 2.5

Method: Resistivity, LDR, thermistor

Worked steps

It **decreases** **B1**.

Exam-style 3.1 ■ 1 mark

Which component has a **straight-line** I – V graph through the origin?

- A** a filament lamp
- B** a diode
- C** a metal wire at constant temperature
- D** a thermistor

Solution 3.1

Method: I–V characteristics

- A a filament lamp
- B a diode
- C a metal wire at constant temperature 
- D a thermistor

Worked steps

C — a metal wire at constant temperature.

Exam-style 3.2 ■ 2 marks

Explain why the **resistance** of a filament lamp **increases** as the current increases.

Solution 3.2

Method: I–V characteristics

Worked steps

A larger current **heats** the filament, raising its temperature **B1**; a hotter metal has a **higher resistance** (the ions vibrate more and impede the electrons) **B1**.

Exam-style 3.3 ■ 2 marks

A student measures the resistivity of a metal wire.

(a) Draw a circuit, using an ammeter and a voltmeter, to measure the **resistance** of the wire.

(b) The readings are $V = 1.5 \text{ V}$ and $I = 0.45 \text{ A}$; the wire has length 0.80 m and diameter 0.40 mm . Calculate the **resistivity** of the metal.

Solution 3.3

Method: Measuring resistivity

Worked steps

$$\begin{aligned} \text{(b) } R &= V/I = 1.5/0.45 = 3.33 \, \Omega \quad \text{M1}; \quad A = \frac{\pi d^2}{4} = \frac{\pi(0.40 \times 10^{-3})^2}{4} = 1.26 \times 10^{-7} \, \text{m}^2 \\ \text{M1}; \quad \rho &= \frac{RA}{L} = \frac{(3.33)(1.26 \times 10^{-7})}{0.80} \quad \text{M1} = 5.2 \times 10^{-7} \, \Omega \text{m} \quad \text{A1}. \end{aligned}$$

Exam-style 3.4 ■ 1 mark

State what happens to the resistance of an **LDR** as the light intensity **increases**.

Solution 3.4

Worked steps

It decreases **B1**.