

19.1 Capacitors and capacitance

Name: _____ Class: _____ Date: _____

Total: 12 marks

Objective

Build the skills to answer exam questions on **capacitance** — $C = Q/V$ and combining capacitors.

You must be able to:


- define **capacitance** and use $C = Q/V$
- combine capacitors in **series** and **parallel**


1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.

■ Capacitance

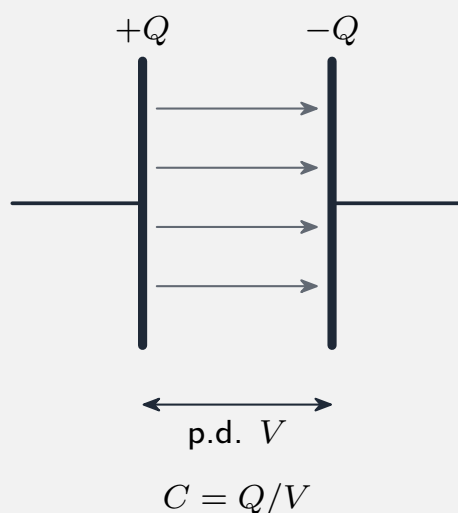A **capacitor** stores charge: $+Q$ on one plate, $-Q$ on the other, with p.d. V across the gap:



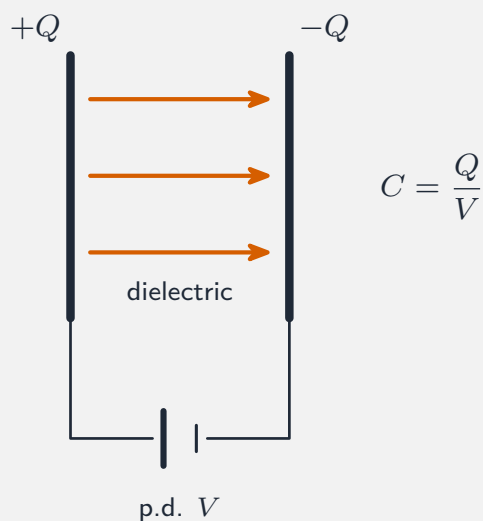

A parallel-plate capacitor

$$C = \frac{Q}{V} \quad (\text{farad, } \text{F} = \text{C V}^{-1}).$$

■ **Combining capacitors (opposite to resistors)**

- **parallel:** $C = C_1 + C_2 + \dots$
- **series:** $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

2 Practice

Now apply the methods above.

2.1 Define capacitance.

[1]

2.2 State the unit of capacitance.

[1]

2.3 A capacitor holds $60 \mu\text{C}$ of charge at 12 V. Find its capacitance.

[2]

2.4 Write the formula for capacitors in **parallel**. [1]

3 Exam-style questions

3.1 The unit of capacitance is the: [1]

- **A** coulomb
 - **B** farad
 - **C** volt
 - **D** ohm
-

3.2 A $100\ \mu\text{F}$ capacitor is charged to $9.0\ \text{V}$. Calculate the **charge** stored. [2]

3.3 A $4.0\ \mu\text{F}$ and a $2.0\ \mu\text{F}$ capacitor are connected in **series**. Calculate the combined capacitance. [3]

3.4 Write the formula for capacitors in **series**. [1]

4 Go further

You are now ready for the real exam questions on this subtopic. Open the **19.1 Capacitors and capacitance** past-paper sheet in the Library, or try these in **Practice mode**:

- 9702/41 N25 —Q6 (capacitance, structured)
- 9702/43 N25 —Q6 (capacitors, combining)
- 9702/42 J25 —Q7 (capacitance from a graph)
- 9702/44 J25 —Q5 ($C = Q/V$)

- 9702/42 M25 —Q5 (capacitor circuit)

Solutions

2.1 The **charge stored per unit potential difference** ($C = Q/V$).

2.2 The **farad** (F).

2.3 $C = Q/V = (60 \times 10^{-6})/12 = 5.0 \mu\text{F}$.

2.4 $C = C_1 + C_2 + \dots$

3.1 **B** —farad.

3.2 $Q = CV = (100 \times 10^{-6})(9.0) = 9.0 \times 10^{-4} \text{ C}$.

3.3 $\frac{1}{C} = \frac{1}{4.0} + \frac{1}{2.0} = \frac{3}{4.0}$; $C = 1.3 \mu\text{F}$.

3.4 $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$