

19.3 Discharging a capacitor

Name: _____ Class: _____ Date: _____

Total: 19 marks

Objective

Build the skills to answer exam questions on a **capacitor discharging** through a resistor.

You must be able to:


- use the **time constant** $\tau = RC$
- use $x = x_0 e^{-t/RC}$ for charge, p.d. or current
- interpret the discharge graphs


1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.

■ Exponential decay

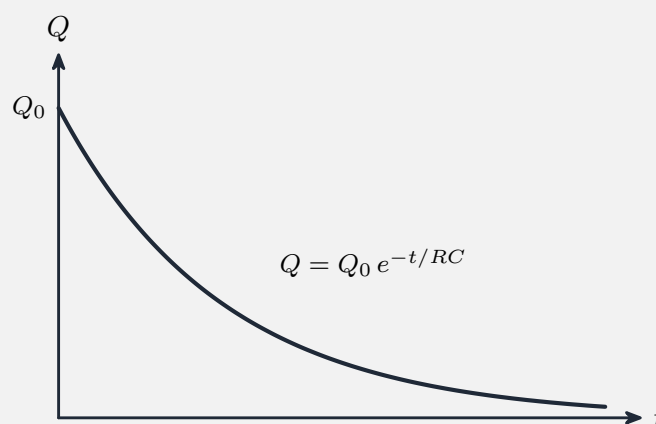When a charged capacitor discharges through a resistor, the charge (and V , I) decays **exponentially**:



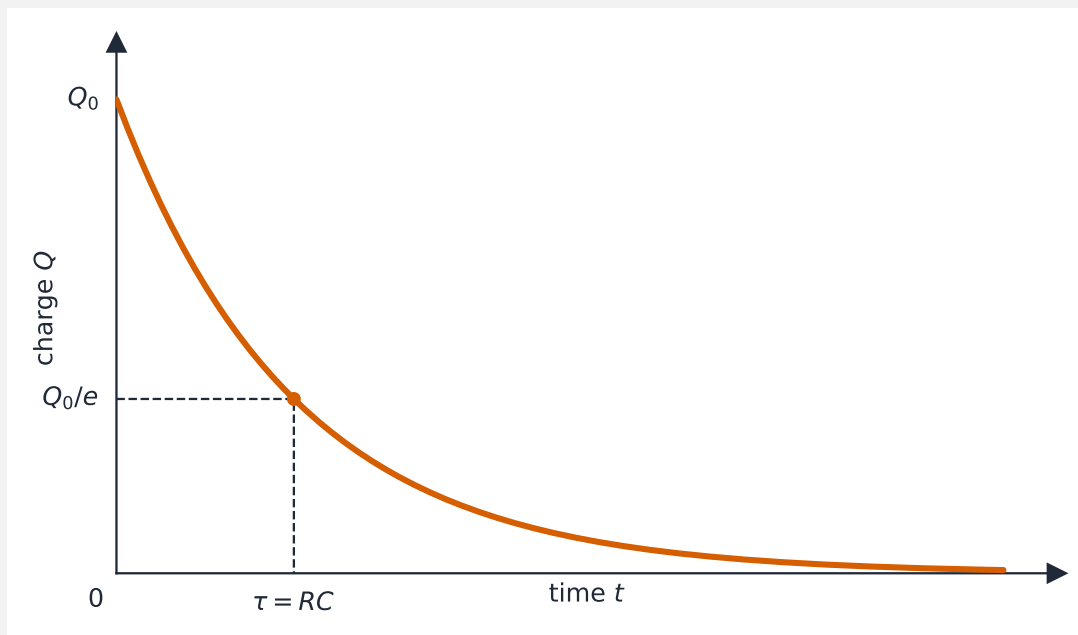

Exponential discharge of a capacitor

$$Q = Q_0 e^{-t/RC}, \quad V = V_0 e^{-t/RC}, \quad I = I_0 e^{-t/RC}.$$

The **time constant** $\tau = RC$ is the time for the charge to fall to $\frac{1}{e} \approx 37\%$ of its initial value.

Worked example. 470 μF through 2.0 $\text{k}\Omega$: $\tau = RC = (2000)(470 \times 10^{-6}) = 0.94 \text{ s}$.

■ Finding the time —take logs

To find the **time** for the charge (or V , or I) to fall to a given value, take the **natural log** of both sides of $V = V_0 e^{-t/RC}$:

$$\ln \frac{V}{V_0} = -\frac{t}{RC} \quad \Rightarrow \quad t = -RC \ln \frac{V}{V_0}.$$

Worked example. For the capacitor above (charged to 6.0 V, $\tau = 0.94 \text{ s}$), the time for the p.d. to fall to 2.0 V is $t = -0.94 \ln \frac{2.0}{6.0} = -0.94 \times (-1.10) = 1.0 \text{ s}$.

2 Practice

Now apply the methods above.

2.1 Write the formula for the **time constant**.

[1]

2.2 A $100\ \mu\text{F}$ capacitor discharges through a $10\ \text{k}\Omega$ resistor. Find the **time constant**. [2]

2.3 State what happens to the **charge** as a capacitor discharges. [1]

2.4 Write the discharge equation for **charge**. [1]

3 Exam-style questions

3.1 The time constant RC is the time for the charge to fall to: [1]

- **A** zero
- **B** half its initial value
- **C** $1/e$ (about 37%) of its initial value
- **D** $1/2e$ of its initial value

3.2 A $470\ \mu\text{F}$ capacitor charged to $6.0\ \text{V}$ discharges through a $2.0\ \text{k}\Omega$ resistor. Calculate (a) the time constant, (b) the p.d. after $1.0\ \text{s}$. [4]

3.3 Sketch a graph of **charge against time** for a discharging capacitor. [2]

3.4 State what happens to the time constant if the **resistance** is doubled. [1]

3.5 A $220\ \mu\text{F}$ capacitor charged to $9.0\ \text{V}$ discharges through a $15\ \text{k}\Omega$ resistor. Calculate the **time** for the p.d. to fall to $3.0\ \text{V}$. [4]

4 Go further

You are now ready for the real exam questions on this subtopic. Open the **19.3 Discharging a capacitor** past-paper sheet in the Library, or try these in **Practice mode**:

- 9702/44 N25 —Q6 (capacitor discharge, structured)
- 9702/43 J25 —Q6 (exponential decay)
- 9702/42 J25 —Q7 (discharge through a resistor)
- 9702/44 J25 —Q8 (time constant)
- 9702/42 M25 —Q5 (capacitor discharge)

Solutions

2.1 $\tau = RC$.

2.2 $\tau = RC = (10 \times 10^3)(100 \times 10^{-6}) = 1.0 \text{ s}$.

2.3 It **decreases exponentially** towards zero.

2.4 $Q = Q_0 e^{-t/RC}$.

3.1 $C = 1/e$ (about 37%).

3.2 (a) $\tau = RC = (2.0 \times 10^3)(470 \times 10^{-6}) = 0.94 \text{ s}$. (b) $V = V_0 e^{-t/RC} = 6.0 e^{-1.0/0.94} = 6.0 \times 0.345 = 2.1 \text{ V}$.

3.3 A curve starting at the initial charge and **decaying exponentially** towards zero, with the same shape (never quite reaching zero).

3.4 It **doubles** ($\tau = RC$).

3.5 $\tau = RC = (15 \times 10^3)(220 \times 10^{-6}) = 3.3 \text{ s}$; $t = -RC \ln \frac{V}{V_0} = -3.3 \ln \frac{3.0}{9.0} = -3.3 \times (-1.10) = 3.6 \text{ s}$.