

# 10.1.1 e.m.f., internal resistance and the V-I graph

---

Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

Total: 30 marks

**KEY WORDS** resistance 电阻 • internal resistance 内阻 • potential difference 电势差  
• terminal p.d. 端电压 • circuit symbols 电路符号

## Objective

---

Sheet 10.1 is the thinnest sheet in this subject – four one-mark definitions – against a unit that the exam asks eleven-mark questions on. This sheet is the rest of 10.1: reading and **drawing circuit diagrams** 电路图 with the standard symbols, the **energy** definitions of **e.m.f.** 电动势 and **potential difference** 电势差 and the difference between them, what the **internal resistance** 内阻 of a source does to the **terminal p.d.** 端电压, and the  $V$ - $I$  experiment that measures both at once. This sheet covers syllabus 10.1.

**You must be able to:**


- recall, draw and interpret the standard **circuit symbols** 电路符号 and circuit diagrams
- define the e.m.f. of a source as the **energy transferred per unit charge** in driving charge round a complete circuit
- distinguish between e.m.f. and potential difference in terms of energy
- understand the effect of the internal resistance of a source on the terminal potential difference

## 1 Worked examples

---

Study these first. Each one shows a **method** that a question later on this sheet needs.

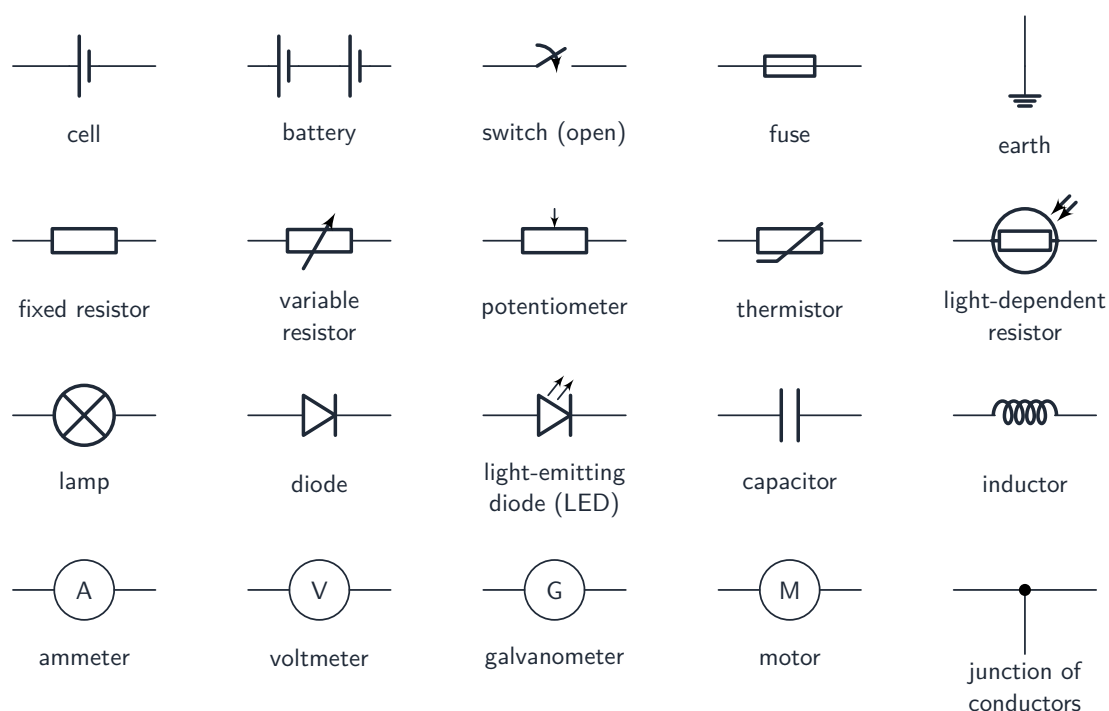- The symbols, and how a diagram is marked




- Draw with a **ruler**, with straight wires and square corners; a wire that simply ends is a lost mark.
- An **ammeter** goes **in series** with the component whose current you want; a **voltmeter** goes **in parallel** across the component whose p.d. you want. Swapping them is the commonest diagram error.
- Junctions that are connected get a **dot**; wires that cross without connecting do not.

#### ■ Two definitions, and they differ only in direction

|                                            | definition                                                                                                                          | where the energy goes                                              |
|--------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------|
| <b>electromotive force</b><br>(e.m.f.) $E$ | the energy transferred <b>to</b> each unit of charge, from some other form into electrical, in driving it around a complete circuit | chemical $\rightarrow$ electrical, inside the source               |
| <b>p.d.</b> $V$                            | the energy transferred <b>from</b> each unit of charge into another form, in a component                                            | electrical $\rightarrow$ thermal, light, kinetic, in the component |

- Both are **joules per coulomb**, so both are measured in **volts**. That is why the distinction has to be made in words about **energy**, and why “e.m.f. is the voltage of the battery” earns nothing.
- E.m.f. is **not a force**, despite its name.

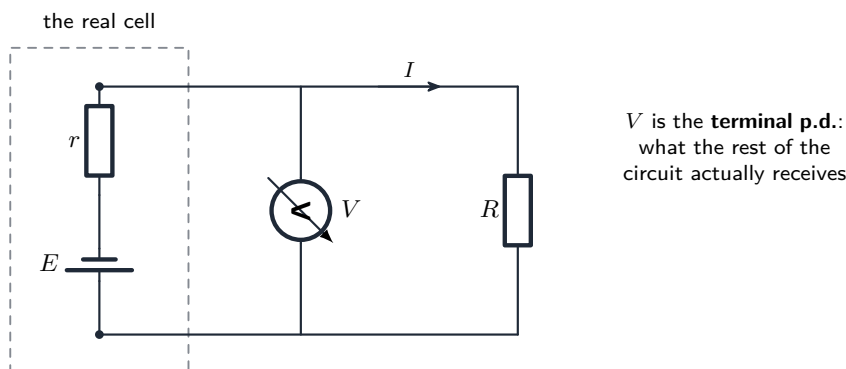■ A real cell: an ideal source with a resistance in series



Each coulomb is given  $E$  joules by the source, gives up  $Ir$  joules inside the cell and  $V$  joules outside it, so  $E = V + Ir$ , or  $V = E - Ir$ . Nothing is lost – the missing energy is dissipated *inside* the cell, which is why a battery gets warm.

Follow one coulomb round the circuit:

$$E = V + Ir \quad \Longleftrightarrow \quad V = E - Ir \quad \Longleftrightarrow \quad E = I(R + r)$$

- It is given  $E$  joules by the source.
- It gives up  $Ir$  joules **inside** the cell, warming it – these are sometimes called the “lost volts”.
- It gives up  $V$  joules **outside**, in the rest of the circuit.  $V$  is the **terminal p.d.**: what the circuit actually receives.

Two limiting cases the exam likes:

| situation                               | what happens                                                                                                   |
|-----------------------------------------|----------------------------------------------------------------------------------------------------------------|
| <b>no current drawn</b><br>( $I = 0$ )  | $V = E$ : the terminal p.d. <b>equals</b> the e.m.f., because nothing is lost inside                           |
| <b>terminals shorted</b><br>( $R = 0$ ) | $I = \frac{E}{r}$ , the <b>largest current</b> the cell can deliver, and all of the energy is wasted inside it |

*Worked example.* A cell of e.m.f.  $1.5\text{ V}$  and internal resistance  $0.50\ \Omega$  is connected to a  $2.5\ \Omega$  resistor. Find the current and the terminal p.d.


- the e.m.f. drives the current through **both** resistances

$$I = \frac{E}{R + r} = \frac{1.5\text{ V}}{2.5\ \Omega + 0.50\ \Omega} = 0.50\text{ A}$$

- then the terminal p.d. is what is left after the internal drop

$$V = E - Ir = 1.5\text{ V} - 0.50\text{ A} \times 0.50\ \Omega = \mathbf{1.25\text{ V}}$$
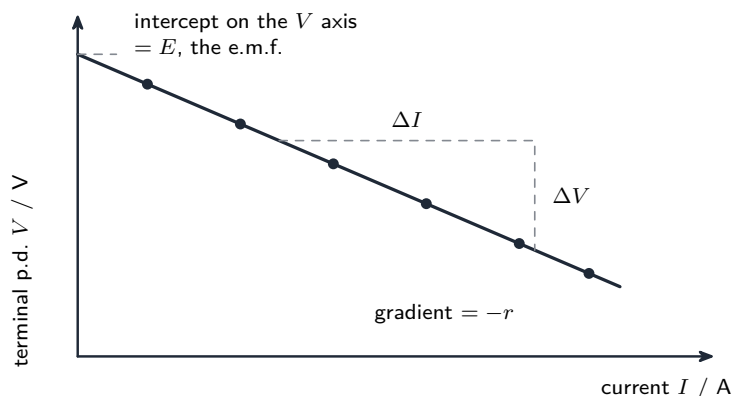
## ■ The experiment: one graph, two answers



Vary the external resistance, plot  $V$  against  $I$ , and  $V = E - Ir$  gives a straight line: the **intercept** is the e.m.f. and the **gradient** is minus the internal resistance. Extrapolating back to  $I = 0$  is how you measure an e.m.f. you can never read directly, because any real voltmeter draws some current.

Vary the external resistance, record  $V$  and  $I$  each time, and plot  $V$  against  $I$ . Since

$$V = E - rI$$

is  $y = c + mx$ :

- the **intercept** on the  $V$  axis is the **e.m.f.**  $E$ ;
- the **gradient** is  $-r$ , so the internal resistance is **minus** the gradient, and it is positive.
- This is how an e.m.f. is measured, because a real voltmeter always draws a **small current**, so the reading straight across the cell is always slightly **less** than  $E$ . The graph extrapolates to the  $I = 0$  case that cannot quite be reached.
- **Power:** the source supplies  $EI$  in total, of which  $I^2r$  is wasted inside and  $VI$  is delivered outside.

## 2 Practice

Now use the methods above.

2.1 Define the **e.m.f.** of a source.

[2]

**2.2** Explain, in terms of energy, the difference between the e.m.f. of a cell and the potential difference across a resistor. [2]

---

---

---

**2.3** A cell of e.m.f. 1.5 V and internal resistance  $0.40\ \Omega$  delivers a current of 0.60 A. Calculate the terminal p.d. [2]

**2.4** Explain why the terminal p.d. of a cell falls as the current drawn from it increases. [2]

---

---

---

**2.5** State the terminal p.d. of a cell when **no** current is drawn from it, and explain your answer. [2]

---

---

**2.6** Calculate the largest current the cell in **2.3** could deliver, and state the condition under which this happens. [2]

### 3 Exam-style questions

**3.1** As the current drawn from a cell increases, the terminal potential difference [1]

|   |   |
|---|---|
| A | B |
| C | D |

**A** increases, because more energy is transferred each second.


**B** stays the same, because the e.m.f. of the cell is fixed.

**C** decreases, because more energy is dissipated in the internal resistance.


**D** decreases, because the e.m.f. of the cell falls.

**3.2** A battery of e.m.f.  $12\text{ V}$  and internal resistance  $0.50\ \Omega$  is connected to a  $2.5\ \Omega$  resistor in series with a parallel combination of a  $6.0\ \Omega$  and a  $3.0\ \Omega$  resistor.

 
(a) Draw a circuit diagram of this arrangement, including an ammeter to measure the current from the battery and a voltmeter to measure the terminal p.d. [2]



 (b) Calculate the total resistance of the external circuit. [2]



 (c) Calculate the current delivered by the battery. [2]



**3.3** A student varied the resistance of the external circuit and recorded the terminal p.d.  $V$  and the current  $I$ .

| $I / \text{A}$ | 0.20 | 0.45 | 0.70 | 0.95 | 1.20 |
|----------------|------|------|------|------|------|
| $V / \text{V}$ | 5.72 | 5.45 | 5.18 | 4.91 | 4.64 |

(a) State the equation relating  $V$  and  $I$  for this circuit, and state what the gradient and the intercept of a graph of  $V$  against  $I$  represent. [3]

---

---

---

(b) Use the first and last pairs of readings to calculate the internal resistance of the source. [3]

(c) Calculate the e.m.f. of the source. [2]

(d) Calculate the power dissipated inside the source when the current is 1.20 A. [2]

(e) Explain why connecting a voltmeter directly across the terminals of the source does not give exactly its e.m.f. [1]

---

---