

# 10.1 Practical circuits

Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

Total: 14 marks

**KEY WORDS** resistance 电阻 • internal resistance 内阻 • terminal p.d. 端电压  
• open circuit 开路 • cell 电池

## Objective

Build the skills to answer exam questions on **practical circuits** — e.m.f., p.d., and internal resistance.

You must be able to:

- define **e.m.f.** and distinguish it from **p.d.**
- explain **internal resistance** and use  $V = \varepsilon - Ir$
- describe how to measure internal resistance

## 1 Worked examples



Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.

### ■ e.m.f. and p.d.

**e.m.f.**  $\varepsilon$  = energy given to each coulomb by the source (in driving it round the whole circuit). **p.d.** = energy transferred from electrical form by each coulomb in a component. Both in volts.
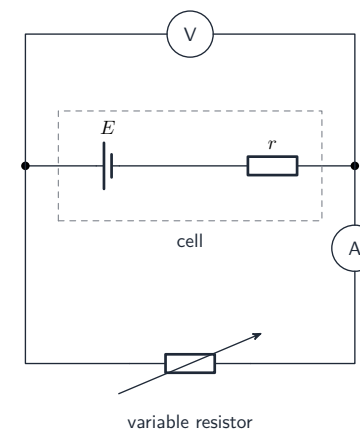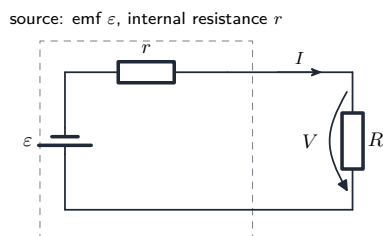
### ■ Internal resistance

A real cell has **internal resistance**  $r$ . When current flows,  $Ir$  is "lost" inside it, so the **terminal p.d.** is:



Internal resistance in a practical cell

$$V = \varepsilon - Ir.$$

- $I = 0$  (open circuit):  $V = \varepsilon$ ;
- larger current  $\rightarrow$  smaller terminal p.d.

**Worked example.**  $\varepsilon = 1.5 \text{ V}$ ,  $r = 0.50 \text{ } \Omega$ ,  $R = 2.5 \text{ } \Omega$ :  $I = \frac{\varepsilon}{R + r} = \frac{1.5}{3.0} = 0.50 \text{ A}$ ;  
 $V = \varepsilon - Ir = 1.5 - 0.25 = 1.25 \text{ V}$ .

To **measure**  $r$ : vary  $R$ , plot  $V$  against  $I$  — the intercept is  $\varepsilon$  and the gradient is  $-r$ .

## 2 Practice

Now apply the methods above.

**2.1** Define the **e.m.f.** of a source. [1]

**2.2** Write the equation linking **terminal p.d.**, e.m.f., current and internal resistance. [1]

**2.3** State the terminal p.d. of a cell when **no current** flows. [1]

2.4 State **one** cause of a cell's internal resistance. [1]

### 3 Exam-style questions

3.1 A battery of e.m.f.  $9.0\text{ V}$  drives two resistors, of  $12\ \Omega$  and  $6.0\ \Omega$ , connected in **parallel** with each other. The terminal p.d. is measured as  $8.0\text{ V}$ . **Determine** the internal resistance of the battery, and the energy wasted inside it each second. [5]

3.2 As the current drawn from a cell **increases**, the terminal p.d.: [1]

- |   |   |
|---|---|
| A | B |
| C | D |
- A increases
  - B decreases
  - C stays the same
  - D becomes equal to the e.m.f.

3.3 Explain, in terms of **energy**, the difference between e.m.f. and p.d. [2]

3.4 Describe how a graph can be used to find the **internal resistance** of a cell. [2]