

9.2 Potential difference and power

Name: _____ Class: _____ Date: _____

Total: 25 marks

KEY WORDS potential difference 电势差 • power 功率 • resistance 电阻 • energy 能量
• volt 伏特

Objective

Build the skills to answer exam questions on **potential difference and power**.

You must be able to:


- define **potential difference** and use $V = W/Q$
- distinguish **e.m.f.** from **p.d.**
- use $P = VI = I^2R = V^2/R$


1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.

■ Potential difference and e.m.f.

Potential difference is the energy transferred **per unit charge**: $V = W/Q$ (unit $V = J\ C^{-1}$).

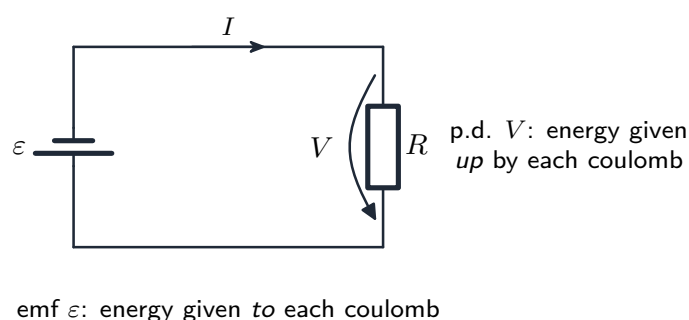

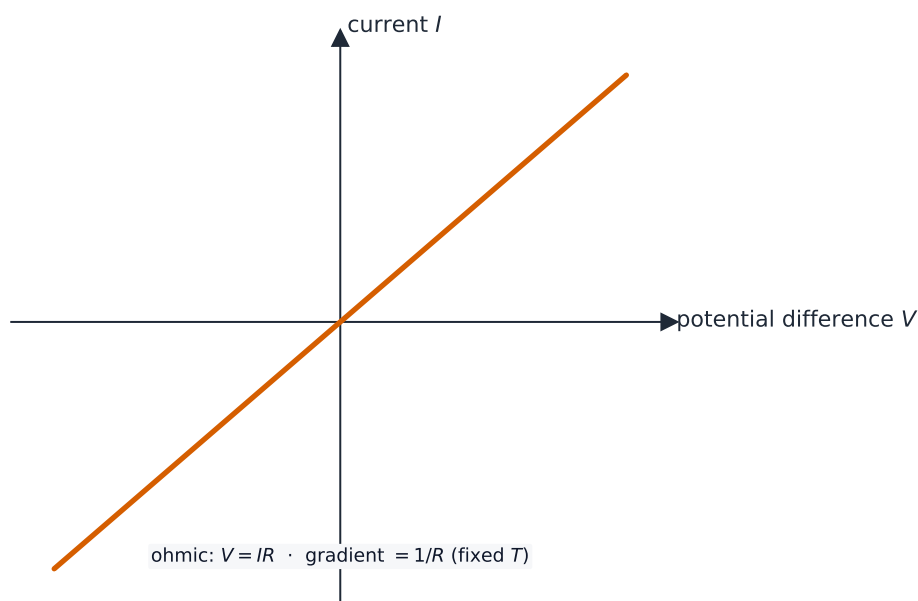

The I-V graph of an ohmic conductor

e.m.f. is the energy given **to** each coulomb by the source; **p.d.** is the energy given **up** by each coulomb in a component. Same formula, opposite direction of energy transfer.

■ Power

$$P = \frac{W}{t} = VI = I^2R = \frac{V^2}{R}.$$

Pick the form with the quantities you know. Energy: $E = Pt$.

Worked example. A kettle "2.4 kW, 240 V": $I = P/V = 10 \text{ A}$; $R = V^2/P = 24 \Omega$.

2 Practice

Now apply the methods above.

2.1 Define **potential difference**.

[1]

2.2 State the difference between **e.m.f.** and **p.d.**

[1]

2.3 Write the **three** forms of the electrical power equation. [2]

2.4 A 12 V supply drives a current of 2.0 A. Find the **power**. [1]

3 Exam-style questions

3.1 A lamp has 240 V across it and a current of 0.50 A. Its power is: [1]

A	B
C	D

A 120 W

B 480 W

C 0.50 W

D 240 W

3.2 A kettle is marked "2.4 kW, 240 V". Calculate (a) the current it draws, (b) its resistance. [4]

3.3 A $10\ \Omega$ and a $20\ \Omega$ resistor are each connected, separately, across the **same** 12 V supply. State which dissipates **more power**, and why. [2]

3.4 A 60 W lamp runs for 5.0 minutes. Calculate the **energy** transferred. [2]

3.5 A battery of negligible internal resistance supplies 9.0 V to a circuit that splits into two parallel branches. The **upper** branch contains a $150\ \Omega$ resistor in series with an unknown resistor R . The **lower** branch contains a $360\ \Omega$ resistor in series with a $540\ \Omega$ resistor. The battery delivers a total current of 0.040 A.

(a) **Define** the electric potential difference across a component. [1]

(b) **Determine** the charge that passes through the battery in 3.0 minutes. [2]

(c) **Calculate** the current I_2 in the **lower** branch. [2]

(d) **Calculate** the current I_1 in the **upper** branch. [1]

(e) **Determine** the resistance R . [2]

(f) **Determine** the total power delivered by the battery, and the power dissipated in the $150\ \Omega$ resistor. [3]