

Week 41

A-Level Physics

Homework bundle for this week

本周作业合集

exercises.lol

Contents 目录

Topic 19 quiz	2
Exercise sheet 19.1	5
Past-paper questions 19.1	11
Exercise sheet 19.2	15
Past-paper questions 19.2	20
Exercise sheet 19.3	22
Past-paper questions 19.3	28

A-Level Physics

Name: _____ Score: _____

1. Capacitance is the charge stored per unit:

- ☐ potential difference
- ☐ current
- ☐ resistance
- ☐ time

2. The energy stored in a capacitor is:

- ☐ $\frac{1}{2}CV^2$
- ☐ CV^2
- ☐ $\frac{1}{2}CV$
- ☐ $\frac{1}{2}QV^2$

3. During discharge through a resistor, the charge on a capacitor:

- ☐ decays exponentially
- ☐ falls in a straight line
- ☐ stays constant
- ☐ rises steadily

4. A capacitor holds 0.012 C at 4.0 V. What is its capacitance, in mF?

_____ mF

5. A 2.0 μF capacitor is charged to 1000 V. How much energy does it store?

_____ J

6. The charge during discharge is given by:

- ☐ $Q_0 e^{-t/RC}$
- ☐ $Q_0 e^{t/RC}$
- ☐ $Q_0(1 - e^{-t/RC})$
- ☐ $\frac{Q_0}{t}$

7. Doubling the charge on a capacitor doubles the voltage, so its capacitance stays the same.

- ☐ True ☐ False

8. Why is there a factor of $\frac{1}{2}$ in the stored-energy formula?

- ☐ the average p.d. during charging is only $V/2$
- ☐ half the charge leaks away
- ☐ the capacitor is only half full
- ☐ energy is always halved

9. A capacitor of $500\ \mu\text{F}$ discharges through a $2000\ \Omega$ resistor. What is the time constant?

_____ s

10. A $2.0\ \mu\text{F}$ and a $3.0\ \mu\text{F}$ capacitor are in parallel. What is the total capacitance, in μF ?

_____ μF

A-Level Physics

1. potential difference

$C = \frac{Q}{V}$ — charge per volt, in farads.

2. $\frac{1}{2}CV^2$

Equivalent forms: $W = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}$.

3. decays exponentially

The bigger the charge, the bigger the current — giving an exponential decay.

4. 3 mF

$C = \frac{Q}{V} = \frac{0.012}{4.0} = 0.0030 \text{ F} = 3.0 \text{ mF}$.

5. 1 J

$W = \frac{1}{2}CV^2 = \frac{1}{2} \times 2.0 \times 10^{-6} \times (1000)^2 = 1.0 \text{ J}$.

6. $Q_0e^{-t/RC}$

Discharge falls toward zero: $Q = Q_0e^{-t/RC}$ (the $1 - e^{-t/RC}$ form is for *charging*).

7. True

$C = \frac{Q}{V}$ is fixed by the capacitor's size and dielectric — Q and V rise together.

8. the average p.d. during charging is only $V/2$

The p.d. rises from 0 to V as it charges, so the average is $V/2$ — hence the triangle area $\frac{1}{2}QV$.

9. 1 s

$\tau = RC = 2000 \times 500 \times 10^{-6} = 1.0 \text{ s}$.

10. 5 μF

In parallel capacitances add: $2.0 + 3.0 = 5.0 \mu\text{F}$.

19.1 Capacitors and capacitance

Name: _____ Class: _____ Date: _____

Total: 24 marks

KEY WORDS capacitance 电容 • capacitor 电容器 • potential difference 电势差 • resistor 电阻器
• farad 法拉

Objective

Build the skills to answer exam questions on **capacitance** — $C = Q/V$ and combining capacitors.

You must be able to:


- define **capacitance** and use $C = Q/V$
- combine capacitors in **series** and **parallel**


1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.

■ Capacitance

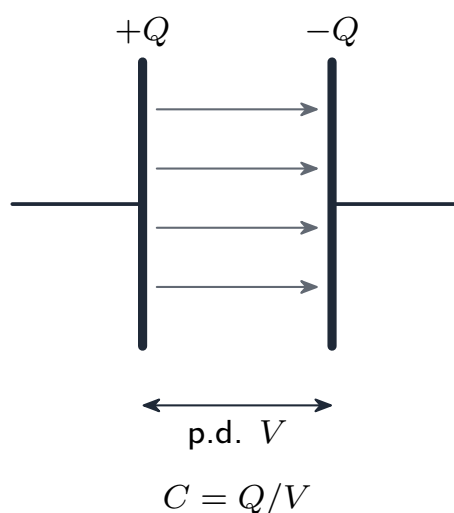A **capacitor** stores charge: $+Q$ on one plate, $-Q$ on the other, with p.d. V across the gap:



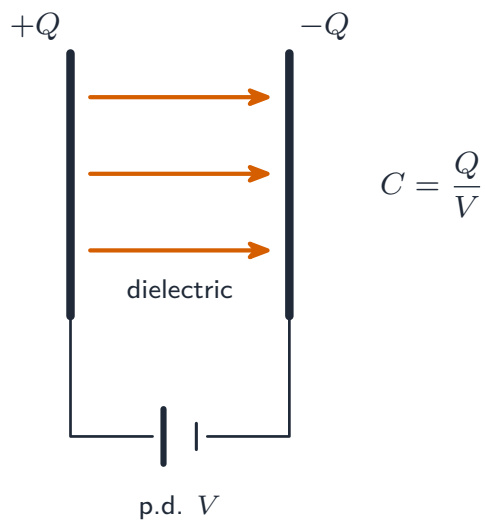

A parallel-plate capacitor

$$C = \frac{Q}{V} \quad (\text{farad, } \text{F} = \text{C V}^{-1}).$$

■ **Combining capacitors (opposite to resistors)**

- **parallel:** $C = C_1 + C_2 + \dots$
- **series:** $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

2 Practice

Now apply the methods above.

2.1 Define **capacitance**. [1]

2.2 State the **unit** of capacitance. [1]

2.3 A capacitor holds $60\ \mu\text{C}$ of charge at 12 V. Find its **capacitance**. [2]

2.4 Write the formula for capacitors in **parallel**. [1]

3 Exam-style questions

3.1 The unit of capacitance is the: [1]

- **A** coulomb
 - **B** farad
 - **C** volt
 - **D** ohm
-

3.2 A $100\ \mu\text{F}$ capacitor is charged to $9.0\ \text{V}$. Calculate the **charge** stored. [2]

3.3 A $4.0\ \mu\text{F}$ and a $2.0\ \mu\text{F}$ capacitor are connected in **series**. Calculate the combined capacitance. [3]

3.4 Write the formula for capacitors in **series**. [1]

3.5 Three capacitors are available: $C_1 = 120\ \mu\text{F}$, $C_2 = 180\ \mu\text{F}$ and $C_3 = 220\ \mu\text{F}$.

(a) C_1 and C_2 are connected in **series** across a supply. **Complete** the table to show how the charge on each and the p.d. across each relate to the total charge Q_S and the supply p.d. V_S . [2]

quantity	relationship
charges Q_1 , Q_2 and Q_S	_____
p.d.s V_1 , V_2 and V_S	_____

(b) **Determine** the combined capacitance of C_1 and C_2 in series. [2]

(c) The supply provides 12 V. **Calculate** the charge stored by that series combination, and the p.d. across C_1 . [3]

(d) C_3 is now connected in **parallel** with the series pair. **Determine** the total capacitance of the whole network, and the total charge it now stores at 12 V. [3]

(e) **State and explain** which single capacitor in the network stores the **most** charge. [2]

Solutions

2.1 The **charge stored per unit potential difference** ($C = Q/V$).

2.2 The **farad** (F).

2.3 $C = Q/V = (60 \times 10^{-6})/12 = 5.0 \mu\text{F}$.

2.4 $C = C_1 + C_2 + \dots$

3.1 **B** — farad.

3.2 $Q = CV = (100 \times 10^{-6})(9.0) = 9.0 \times 10^{-4} \text{ C}$.

3.3 $\frac{1}{C} = \frac{1}{4.0} + \frac{1}{2.0} = \frac{3}{4.0}$; $C = 1.3 \mu\text{F}$.

3.4 $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

3.5 (a) Charges: $Q_1 = Q_2 = Q_s$ — the same charge passes through every capacitor in a series chain. P.d.s: $V_1 + V_2 = V_s$.

(b) $\frac{1}{C} = \frac{1}{120} + \frac{1}{180}$, so $C = \frac{120 \times 180}{300} = 72 \mu\text{F}$.

(c) $Q = CV = 72 \times 10^{-6} \times 12 = 8.6 \times 10^{-4} \text{ C}$; $V_1 = \frac{Q}{C_1} = \frac{8.64 \times 10^{-4}}{120 \times 10^{-6}} = 7.2 \text{ V}$. (The **smaller** capacitor takes the larger share of the p.d.)

(d) Capacitors in parallel add: $C_{\text{total}} = 72 + 220 = 292 \mu\text{F}$; $Q_{\text{total}} = 292 \times 10^{-6} \times 12 = 3.5 \times 10^{-3} \text{ C}$.

(e) C_3 — it has the full 12 V across it and the largest capacitance, so $Q = CV$ is largest; the series pair shares the same p.d. between two capacitors and behaves as only $72 \mu\text{F}$.

6 (a) Two parallel plate capacitors C_1 and C_2 are connected to a supply that has a potential difference (p.d.) V_S . The capacitors may be connected in series or in parallel.

The supply provides charge Q_S and the plates of the two capacitors acquire charges Q_1 and Q_2 respectively. The p.d.s across the plates of the capacitors are V_1 and V_2 respectively.

Complete Table 6.1 to indicate how Q_S , Q_1 and Q_2 relate to each other, and how V_S , V_1 and V_2 relate to each other, for series and parallel connections of the capacitors to the supply.

Table 6.1

	relationship between charges	relationship between p.d.s
series		
parallel		

[4]

(b) An isolated capacitor of capacitance $470\mu\text{F}$ stores 19 mJ of energy.

(i) Calculate the p.d. across the capacitor.

p.d. =V [2]

(ii) Calculate the charge on the capacitor.

charge = C [2]

(iii) The capacitor is now connected in parallel with a capacitor of capacitance $180\mu\text{F}$ that is initially uncharged.

Determine the total energy, in mJ, now stored in the two capacitors.

energy = mJ [3]

[Total: 11]

- 5 (a) A capacitor of capacitance C_1 is connected in series with a second capacitor of capacitance C_2 .

Show that the combined capacitance C of the two capacitors is given by

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}.$$

[2]

- (b) Three identical capacitors, each of capacitance C , are connected in a network as shown in Fig. 5.1.

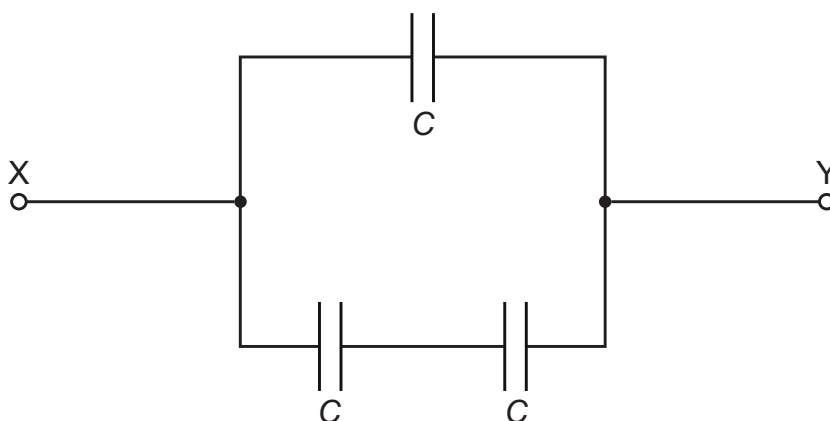


Fig. 5.1

The variation of the charge Q with the potential difference (p.d.) V between the terminals X and Y is shown in Fig. 5.2.

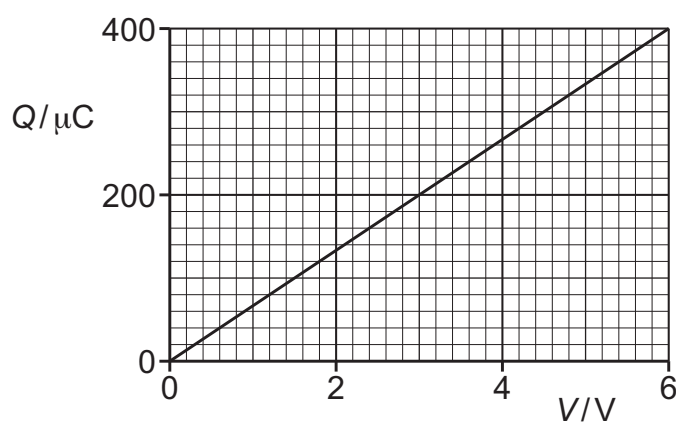


Fig. 5.2

Show that C is equal to $44\ \mu\text{F}$.

[3]

(c) The capacitor network in Fig. 5.1 is charged and then connected to a resistor of resistance $54\ \text{k}\Omega$. The capacitor network discharges through the resistor.

(i) Determine the time constant τ of the circuit. Give a unit with your answer.

$\tau =$ unit [2]

(ii) Determine the time taken for the discharge current to reduce to 15% of the initial discharge current.

time = s [2]

[Total: 9]

19.2 Energy stored in a capacitor

Name: _____ Class: _____ Date: _____

Total: 23 marks

KEY WORDS energy 能量 • capacitor 电容器

Objective

Build the skills to answer exam questions on the **energy stored in a capacitor**.

You must be able to:


- find energy from the **area under the potential–charge graph**
- use $W = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}$


1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.

■ Energy stored

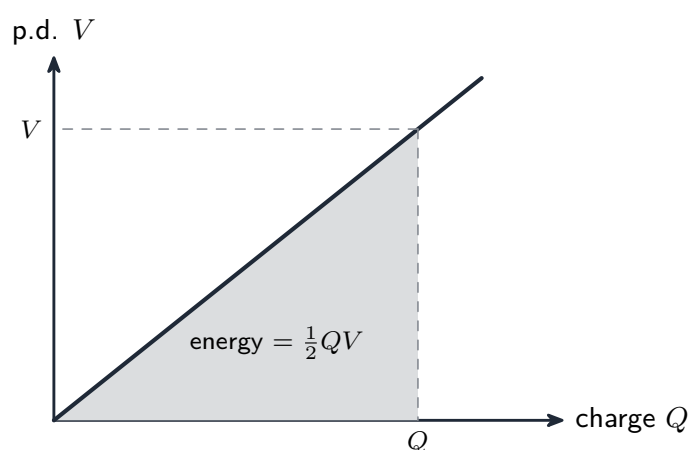The energy is the **area under the V – Q graph** — a triangle:



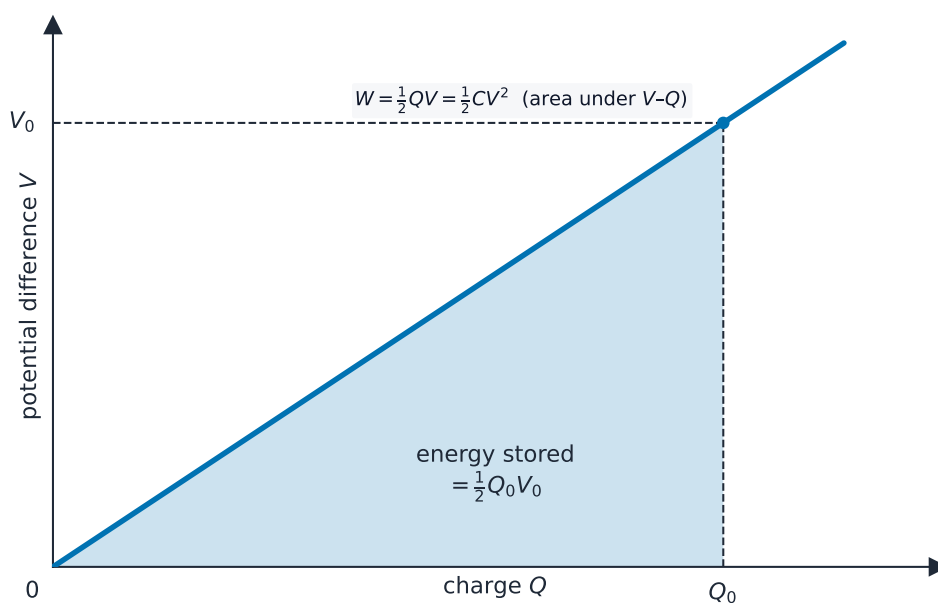

Energy stored is the area under the Q-V graph

$$W = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}.$$

The factor $\frac{1}{2}$ appears because the **average** p.d. during charging is $V/2$ (it grows from 0 to V).

Worked example. 100 μF at 12 V: $W = \frac{1}{2}CV^2 = \frac{1}{2}(100 \times 10^{-6})(12)^2 = 7.2 \times 10^{-3} \text{ J}.$

2 Practice

Now apply the methods above.

2.1 Write the **three** forms of the capacitor energy formula. [1]

2.2 Find the energy stored in a 100 μF capacitor charged to 12 V. [2]

2.3 State what the **area** under a potential–charge graph represents. [1]

3 Exam-style questions

3.1 The energy stored in a capacitor is: [1]

- A QV
 - B $\frac{1}{2}QV$
 - C CV
 - D Q^2C
-

3.2 A $220\ \mu\text{F}$ capacitor stores $4.0\ \text{mJ}$ of energy. Calculate the **voltage** across it. [3]

3.3 Explain why the energy stored is $\frac{1}{2}QV$ and **not** QV . [2]

3.5 A defibrillator stores energy in a $32\ \mu\text{F}$ capacitor charged to $2.5\ \text{kV}$, and delivers it to a patient in a pulse lasting $8.0\ \text{ms}$.

(a) **Determine** the energy stored by the capacitor when fully charged. [2]

(b) **Determine** the charge stored. [2]

(c) In the pulse, 75% of the stored energy is delivered to the patient. **Determine** the

average power delivered.

[3]

(d) The capacitor is charged instead to 1.8 kV. **Determine** the percentage by which the stored energy falls, and **explain** why it is not the same percentage as the fall in p.d. [3]

(e) On the same axes, **sketch** how the energy stored varies with the p.d. across the capacitor, and how the **charge** stored varies with it. **Label** each line. [3]

Solutions

2.1 $W = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}.$

2.2 $W = \frac{1}{2}CV^2 = \frac{1}{2}(100 \times 10^{-6})(12)^2 = 7.2 \times 10^{-3} \text{ J}.$

2.3 The **energy stored** in the capacitor.

3.1 $B = \frac{1}{2}QV.$

3.2 $W = \frac{1}{2}CV^2 \Rightarrow V = \sqrt{\frac{2W}{C}} = \sqrt{\frac{2(4.0 \times 10^{-3})}{220 \times 10^{-6}}} = 6.0 \text{ V}.$

3.3 As the capacitor charges, the p.d. rises from 0 to V ; the **average** p.d. is $V/2$, so the work done is $Q \times (V/2) = \frac{1}{2}QV$, not QV .

3.5 (a) $E = \frac{1}{2}CV^2 = \frac{1}{2}(32 \times 10^{-6})(2500)^2 = 100 \text{ J}.$

(b) $Q = CV = 32 \times 10^{-6} \times 2500 = 8.0 \times 10^{-2} \text{ C}.$

(c) Energy delivered $= 0.75 \times 100 = 75 \text{ J}$; $P = \frac{E}{t} = \frac{75}{8.0 \times 10^{-3}} = 9.4 \times 10^3 \text{ W}.$ (About nine kilowatts, for eight milliseconds.)

(d) New energy $= \frac{1}{2}(32 \times 10^{-6})(1800)^2 = 51.8 \text{ J}$, a fall of $\frac{100 - 51.8}{100} = 48\%$ — while the p.d. fell by only 28%, because $E \propto V^2$, so the fractional change in energy is roughly **twice** the fractional change in p.d..

(e) Charge: a **straight line through the origin**, since $Q = CV$. Energy: a **curve through the origin** getting steeper, since $E \propto V^2$. Both labelled, with axes labelled.

6 (a) Two parallel plate capacitors C_1 and C_2 are connected to a supply that has a potential difference (p.d.) V_S . The capacitors may be connected in series or in parallel.

The supply provides charge Q_S and the plates of the two capacitors acquire charges Q_1 and Q_2 respectively. The p.d.s across the plates of the capacitors are V_1 and V_2 respectively.

Complete Table 6.1 to indicate how Q_S , Q_1 and Q_2 relate to each other, and how V_S , V_1 and V_2 relate to each other, for series and parallel connections of the capacitors to the supply.

Table 6.1

	relationship between charges	relationship between p.d.s
series		
parallel		

[4]

(b) An isolated capacitor of capacitance $470\mu\text{F}$ stores 19 mJ of energy.

(i) Calculate the p.d. across the capacitor.

p.d. =V [2]

(ii) Calculate the charge on the capacitor.

charge = C [2]

(iii) The capacitor is now connected in parallel with a capacitor of capacitance $180\mu\text{F}$ that is initially uncharged.

Determine the total energy, in mJ, now stored in the two capacitors.

energy = mJ [3]

[Total: 11]

19.3 Discharging a capacitor

Name: _____ Class: _____ Date: _____

Total: 29 marks

KEY WORDS time constant 时间常数 • exponential decay 指数衰减 • resistor 电阻器 • resistance 电阻
• capacitor 电容器

Objective

Build the skills to answer exam questions on a **capacitor discharging** through a resistor.

You must be able to:


- use the **time constant** $\tau = RC$
- use $x = x_0 e^{-t/RC}$ for charge, p.d. or current
- interpret the discharge graphs


1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.

■ Exponential decay

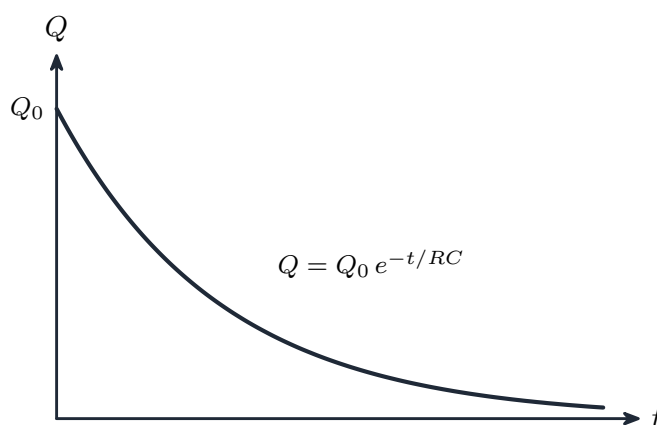When a charged capacitor discharges through a resistor, the charge (and V , I) decays **exponentially**:



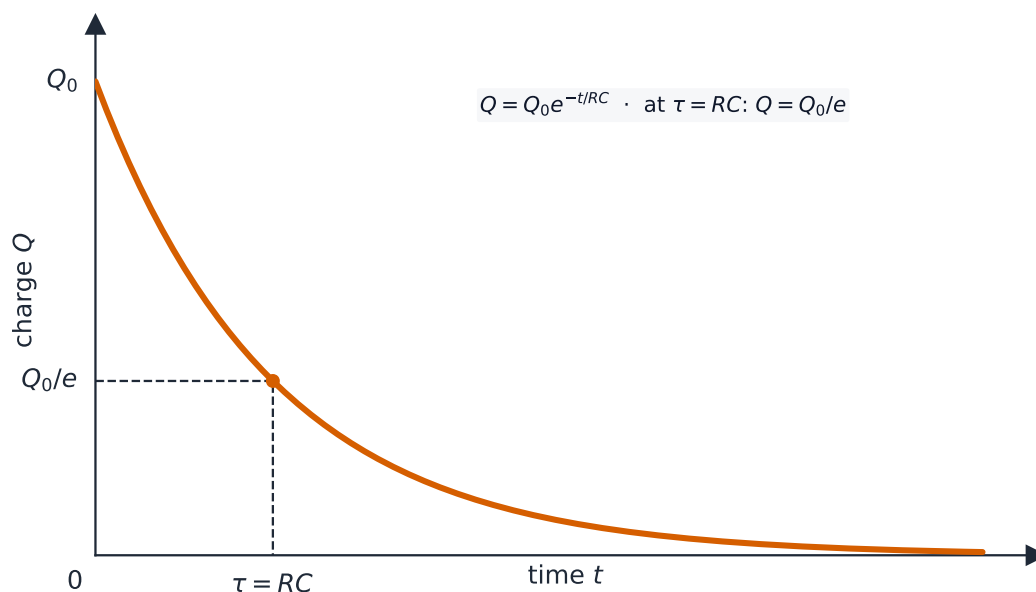

Exponential discharge of a capacitor

$$Q = Q_0 e^{-t/RC}, \quad V = V_0 e^{-t/RC}, \quad I = I_0 e^{-t/RC}.$$

The **time constant** $\tau = RC$ is the time for the charge to fall to $\frac{1}{e} \approx 37\%$ of its initial value.

Worked example. $470 \mu\text{F}$ through $2.0 \text{ k}\Omega$: $\tau = RC = (2000)(470 \times 10^{-6}) = 0.94 \text{ s}$.

■ Finding the time — take logs

To find the **time** for the charge (or V , or I) to fall to a given value, take the **natural log** of both sides of $V = V_0 e^{-t/RC}$:

$$\ln \frac{V}{V_0} = -\frac{t}{RC} \quad \Rightarrow \quad t = -RC \ln \frac{V}{V_0}.$$

Worked example. For the capacitor above (charged to 6.0 V , $\tau = 0.94 \text{ s}$), the time for the p.d. to fall to 2.0 V is $t = -0.94 \ln \frac{2.0}{6.0} = -0.94 \times (-1.10) = 1.0 \text{ s}$.

2 Practice

Now apply the methods above.

2.1 Write the formula for the **time constant**. [1]

2.2 A $100\ \mu\text{F}$ capacitor discharges through a $10\ \text{k}\Omega$ resistor. Find the **time constant**. [2]

2.3 State what happens to the **charge** as a capacitor discharges. [1]

2.4 Write the discharge equation for **charge**. [1]


3 Exam-style questions

3.1 The time constant RC is the time for the charge to fall to: [1]

- **A** zero
 - **B** half its initial value
 - **C** $1/e$ (about 37%) of its initial value
 - **D** $1/2e$ of its initial value
-


3.2 A $470\ \mu\text{F}$ capacitor charged to $6.0\ \text{V}$ discharges through a $2.0\ \text{k}\Omega$ resistor. Calculate (a) the time constant, (b) the p.d. after $1.0\ \text{s}$. [4]

 3.3 Sketch a graph of **charge against time** for a discharging capacitor. [2]



3.4 State what happens to the time constant if the **resistance** is doubled. [1]

 3.5 A $220\ \mu\text{F}$ capacitor charged to $9.0\ \text{V}$ discharges through a $15\ \text{k}\Omega$ resistor. Calculate the **time** for the p.d. to fall to $3.0\ \text{V}$. [4]




3.6 A capacitor C is charged and then discharged through a resistor R . A data logger records the p.d. V_R across the resistor and the p.d. V_C across the capacitor. At $t = 0$ the p.d. across the capacitor is $9.0\ \text{V}$, and the initial current is $1.8\ \text{mA}$. The p.d. across the capacitor falls to $3.3\ \text{V}$ after $12\ \text{s}$.

(a) **State** the relationship between V_C and V_R during the discharge, and give a reason. [2]



(b) **Determine** the resistance R . [2]

 

(c) **Determine** the time constant τ of the circuit. [3]

(d) Hence **determine** the capacitance C , in μF . [2]

(e) **Explain**, in terms of the current in the circuit, why the decay of the charge on the capacitor is **exponential**. [3]

Solutions

2.1 $\tau = RC$.

2.2 $\tau = RC = (10 \times 10^3)(100 \times 10^{-6}) = 1.0 \text{ s}$.

2.3 It **decreases exponentially** towards zero.

2.4 $Q = Q_0 e^{-t/RC}$.

3.1 $C = 1/e$ (about 37%).

3.2 (a) $\tau = RC = (2.0 \times 10^3)(470 \times 10^{-6}) = 0.94 \text{ s}$. (b) $V = V_0 e^{-t/RC} = 6.0 e^{-1.0/0.94} = 6.0 \times 0.345 = 2.1 \text{ V}$.

3.3 A curve starting at the initial charge and **decaying exponentially** towards zero, with the same shape (never quite reaching zero).

3.4 It **doubles** ($\tau = RC$).

3.5 $\tau = RC = (15 \times 10^3)(220 \times 10^{-6}) = 3.3 \text{ s}$; $t = -RC \ln \frac{V}{V_0} = -3.3 \ln \frac{3.0}{9.0} = -3.3 \times (-1.10) = 3.6 \text{ s}$.

3.6 (a) They are **equal** at every instant, $V_C = V_R$, because the capacitor and resistor form a single loop with no other source, so the p.d. driving the current is the capacitor's own p.d..

(b) $R = \frac{V}{I} = \frac{9.0}{1.8 \times 10^{-3}} = 5.0 \times 10^3 \Omega$.

(c) $V = V_0 e^{-t/\tau}$, so $\frac{3.3}{9.0} = e^{-12/\tau}$; $\ln(0.367) = -\frac{12}{\tau}$, giving $-1.003 = -\frac{12}{\tau}$ and $\tau = 12 \text{ s}$. (The p.d. has fallen to $1/e$ of its start, which is what the time constant means.)

(d) $\tau = RC$, so $C = \frac{12}{5.0 \times 10^3} = 2.4 \times 10^{-3} \text{ F} = 2.4 \times 10^3 \mu\text{F}$.

(e) The current is $I = \frac{V_C}{R}$, and $V_C \propto Q$, so the current — the rate at which charge leaves — is **proportional to the charge still on the capacitor**. A quantity whose rate of decrease is proportional to itself decays exponentially; so as the charge falls the current falls with it, the discharge slows, and Q never quite reaches zero.

- 7 Fig. 7.1 shows a circuit containing a capacitor of capacitance C and a resistor of resistance R .

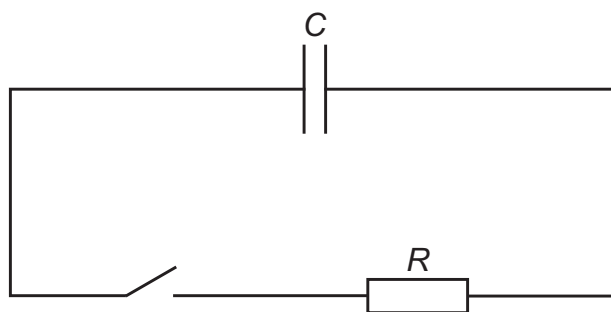


Fig. 7.1

Initially, the switch is open and the potential difference (p.d.) across the capacitor is 12 V.

The switch is closed at time $t = 0$ and the capacitor discharges through the resistor.

Fig. 7.2 shows the variation of the charge Q on the capacitor with the p.d. V_C across the capacitor as the capacitor discharges. Fig. 7.3 shows the variation of the current I in the resistor with the p.d. V_R across the resistor as the capacitor discharges.

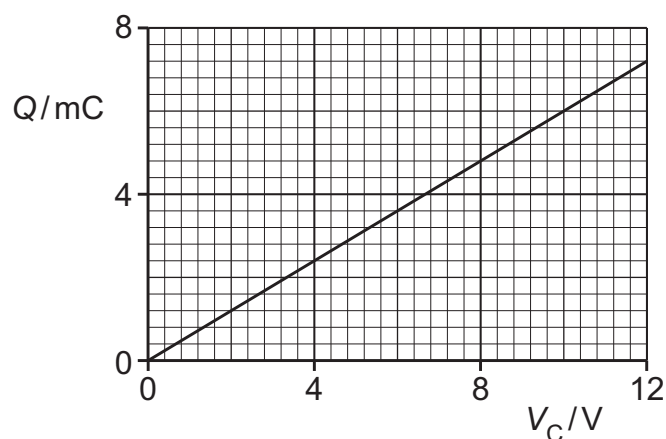


Fig. 7.2

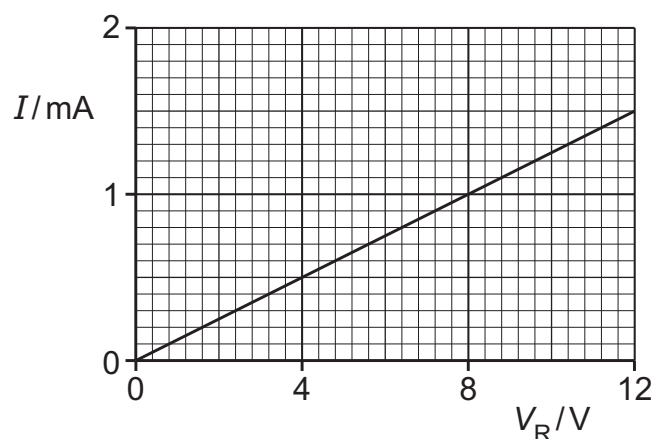


Fig. 7.3

- (a) State the relationship between V_C and V_R .

..... [1]

- (b) Determine:

- (i) the capacitance C , in μF

$C =$ μF [2]

(ii) the resistance R , in $\text{k}\Omega$

$R = \dots\dots\dots \text{k}\Omega$ [2]

(iii) the time constant τ of the circuit.

$\tau = \dots\dots\dots \text{s}$ [2]

(c) Use Fig. 7.2, Fig. 7.3 and your answer in (a) to explain why the variation of Q with t is exponential in nature.

[3]

[Total: 10]