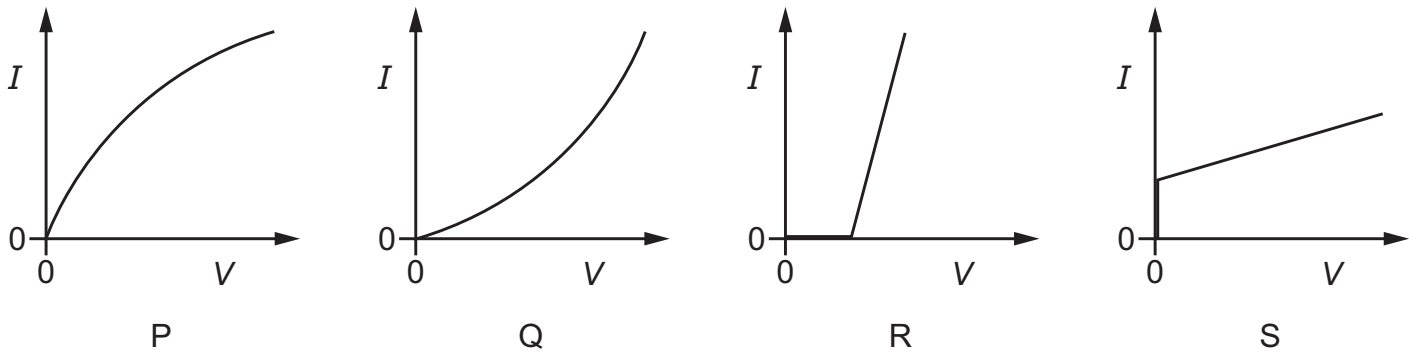


33 The graphs show possible current–voltage ( $I$ – $V$ ) characteristics for a filament lamp and for a semiconductor diode.



Which row identifies the  $I$ – $V$  graphs for the lamp and for the diode?

|   | filament lamp | semiconductor diode |
|---|---------------|---------------------|
| A | P             | R                   |
| B | P             | S                   |
| C | Q             | R                   |
| D | Q             | S                   |


33 A piece of wire X has resistivity  $\rho$ , length  $L$  and cross-sectional area  $A$ . Wire X has a resistance  $R$ .

A second piece of wire Y is made of a different metal. It has the same resistance as X but has twice the length of X.

Which row gives possible values for the resistivity and the cross-sectional area of Y?

|   | resistivity       | cross-sectional area |
|---|-------------------|----------------------|
| A | $\frac{1}{2}\rho$ | $\frac{1}{2}A$       |
| B | $\frac{1}{2}\rho$ | $A$                  |
| C | $\rho$            | $\frac{1}{2}A$       |
| D | $2\rho$           | $A$                  |

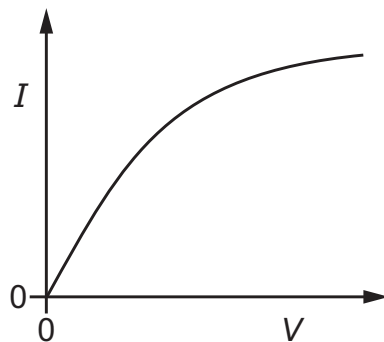**32** Which component has the  $I$ – $V$  graph shown?



- A** filament lamp
- B** metallic conductor at constant temperature
- C** resistor of fixed resistance
- D** semiconductor diode
- 34** A copper wire of length 2 m has a circular cross-section. There is a constant current in the wire when it is connected to a mobile phone in order to charge the battery.

The wire has a fault. A 1 m length of the wire has half the diameter of the other 1 m length.

The power dissipated in the thicker length of wire is  $P$ .

What is the power dissipated in the thinner length of wire?

- A**  $\frac{1}{4}P$                       **B**  $\frac{1}{2}P$                       **C**  $2P$                       **D**  $4P$

5 A student uses a circuit containing an ammeter, a voltmeter and a cell to take measurements to determine the resistance of a length of nichrome wire.

(a) (i) Define resistance.

.....

..... [1]

(ii) Draw a circuit diagram to show how the components should be connected. Use the symbol for a resistor to represent the nichrome wire.

[2]

(b) The student also measures the length and the diameter of the wire. Table 5.1 shows the measurements recorded for each quantity.

Table 5.1

| quantity          | measurement                  |
|-------------------|------------------------------|
| length            | $(0.864 \pm 0.001)\text{m}$  |
| diameter          | $(0.496 \pm 0.002)\text{mm}$ |
| voltmeter reading | $(1.38 \pm 0.02)\text{V}$    |
| ammeter reading   | $(0.276 \pm 0.001)\text{A}$  |

(i) Show that the resistance of the wire is  $5.00\,\Omega$ .

[1]

**(ii)** Calculate, to three significant figures, the resistivity  $\rho$  of the nichrome.

$$\rho = \dots\dots\dots \Omega \text{ m} \quad [3]$$

**(iii)** Calculate the percentage uncertainty in  $\rho$ .

$$\text{percentage uncertainty} = \dots\dots\dots \% \quad [2]$$

**(iv)** Determine the absolute uncertainty in  $\rho$ .


$$\text{absolute uncertainty} = \dots\dots\dots \Omega \text{ m} \quad [1]$$

[Total: 10]

**32** Which expression gives the definition of resistance?

- A** current divided by potential difference
- B** current multiplied by potential difference
- C** potential difference divided by current
- D** resistivity multiplied by length

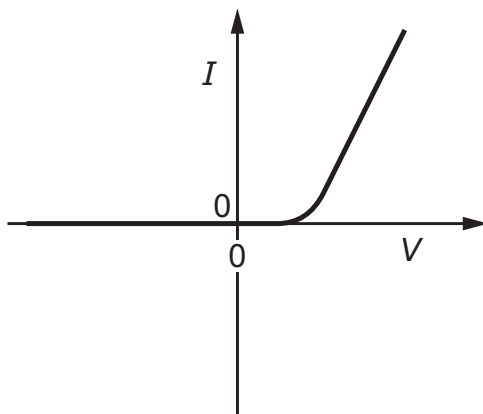**33** The graph shows the  $I$ – $V$  characteristic of an electrical component.




What is the component?

- A** a filament lamp
- B** a metallic conductor at constant temperature
- C** a resistor
- D** a semiconductor diode

**35** The diagram shows a circuit containing a thermistor, a fixed resistor and a battery.

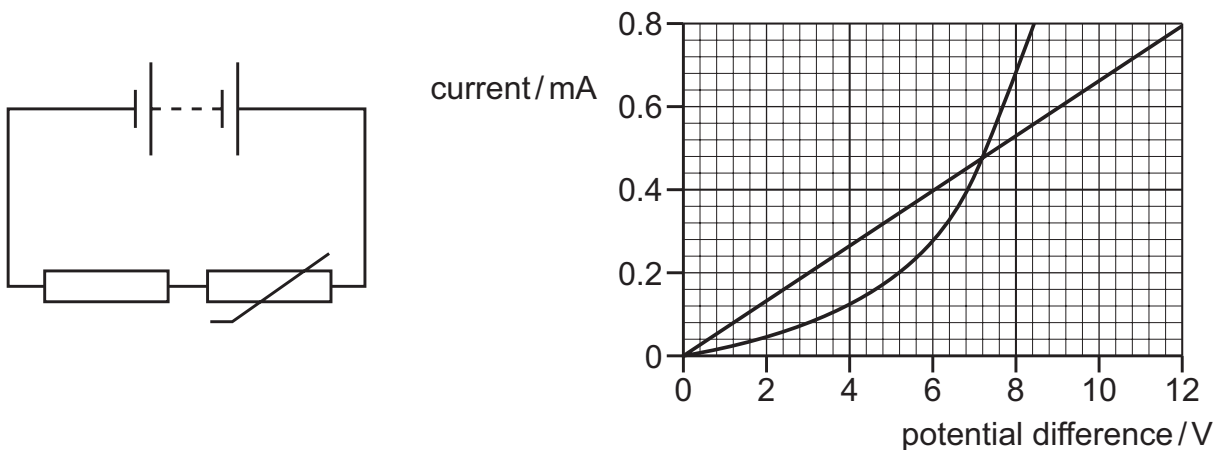The graph shows the  $I$ – $V$  characteristics of both components.




The battery has an e.m.f. of 12 V and negligible internal resistance.


What is the current in the fixed resistor?

- A** 0.36 mA      **B** 0.40 mA      **C** 0.48 mA      **D** 0.80 mA

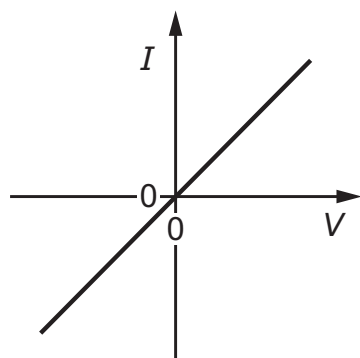
**33** The  $I$ - $V$  characteristics for three electrical components are shown.



1

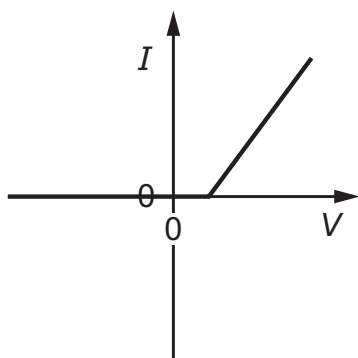

2

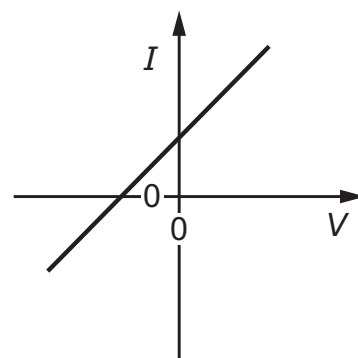


3

Which components obey Ohm's law?

- A** 1, 2 and 3      **B** 1 and 2 only      **C** 1 and 3 only      **D** 1 only

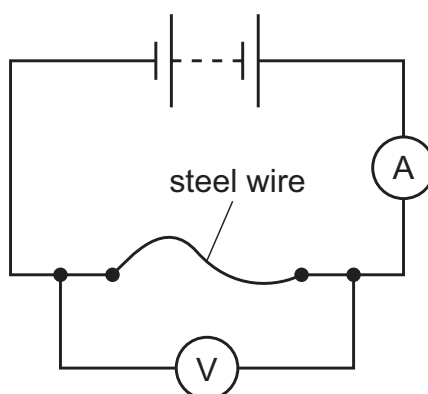**34** A steel wire with a length of 2.20 m is connected to a battery as shown.



The reading on the voltmeter is 1.50 V and the reading on the ammeter is 4.90 A.

The resistivity of steel is  $6.90 \times 10^{-7} \Omega \text{ m}$ .

What is the diameter of the steel wire?

- A**  $1.76 \times 10^{-4} \text{ m}$       **B**  $3.52 \times 10^{-4} \text{ m}$       **C**  $1.26 \times 10^{-3} \text{ m}$       **D**  $2.51 \times 10^{-3} \text{ m}$

- 7 A nichrome resistance wire has length 150 cm, cross-sectional area  $2.45 \times 10^{-7} \text{ m}^2$  and resistivity  $1.12 \times 10^{-6} \Omega \text{ m}$ .

(a) Calculate, to three significant figures, the resistance of the wire.

resistance = .....  $\Omega$  [3]

- (b) The nichrome wire forms part of a potentiometer circuit together with a cell of electromotive force (e.m.f.) 1.2 V and negligible internal resistance, as shown in Fig. 7.1.

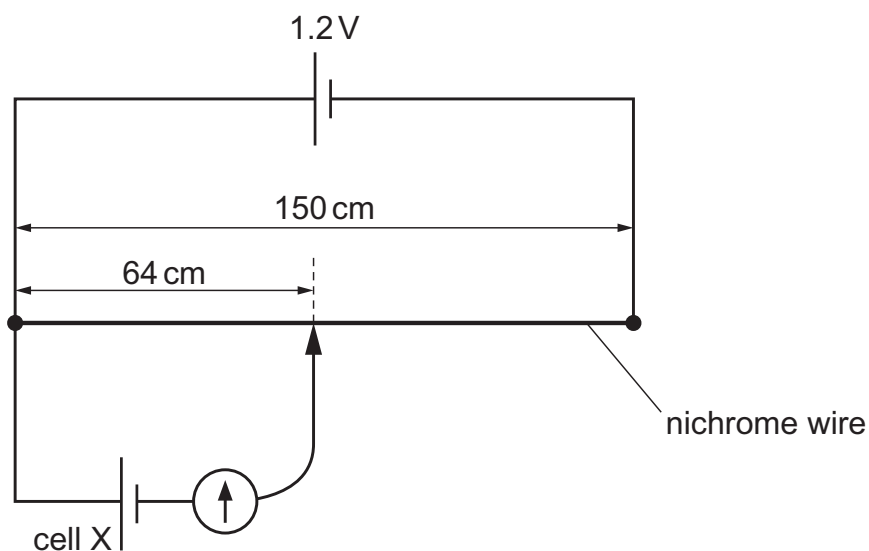


Fig. 7.1 (not to scale)

The circuit is used to determine the e.m.f. of cell X.

The galvanometer is used in a null method to find the null point 64 cm from the left-hand end of the nichrome wire.

- (i) Explain what is meant by a null method.

.....  
..... [1]

(ii) Calculate the e.m.f. of cell X.

e.m.f. = ..... V [2]

(iii) The cell of e.m.f. 1.2V is replaced by a new cell with the same e.m.f. but with an internal resistance that is **not** negligible.

State and explain the effect, if any, of the internal resistance of the new cell on the position of the null point.

.....

.....

.....

..... [2]

[Total: 8]

- 5 (a) (i) State and explain the effect, if any, on the resistance of a filament wire in a lamp as the current in the wire decreases.

.....  
..... [1]

- (ii) On Fig. 5.1, sketch the  $I$ – $V$  characteristic of a filament lamp.

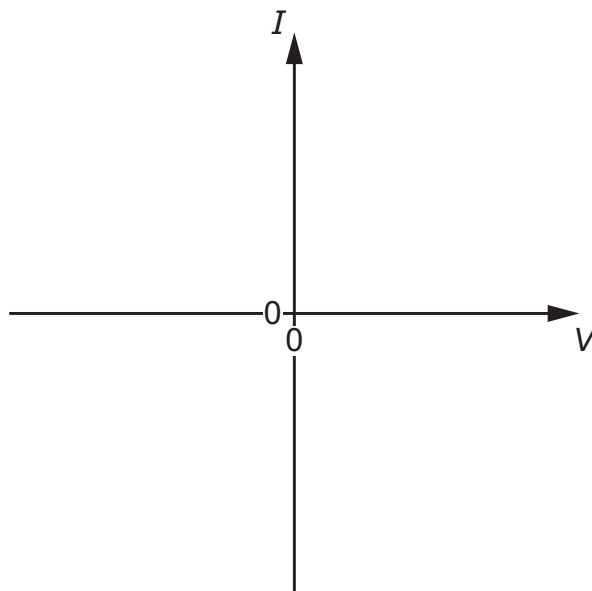


Fig. 5.1

[2]

- (b) A battery of electromotive force (e.m.f.)  $E$  and negligible internal resistance is connected in parallel with two filament lamps A and B, as shown in Fig. 5.2.

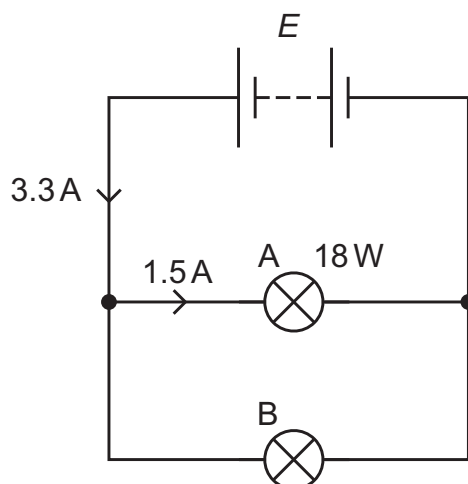


Fig. 5.2

The current in the battery is 3.3A and the current in lamp A is 1.5A. The power dissipated in lamp A is 18W.

- (i) Calculate the e.m.f.  $E$  of the battery.

$$E = \dots\dots\dots \text{ V [2]}$$

- (ii) The filament wire of lamp B has a cross-sectional area of  $1.4 \times 10^{-9} \text{ m}^2$ . The number of free (conduction) electrons per unit volume in the metal of the filament wire is  $3.4 \times 10^{28} \text{ m}^{-3}$ .

Calculate the average drift speed of the free electrons in the filament wire of lamp B.

$$\text{average drift speed} = \dots\dots\dots \text{ m s}^{-1} \text{ [3]}$$

[Total: 8]