

A-Level Physics

Name: _____ Score: _____

- The e.m.f. is the energy given to each unit of charge by the _____.

- 5.0 A flows into a junction and splits into two branches; one carries 2.0 A. What does the other carry?
_____ A
- A 12 V supply is across $R_1 = 2.0 \text{ k}\Omega$ and $R_2 = 4.0 \text{ k}\Omega$ in series. What is the output across R_2 ?
_____ V
- A cell of e.m.f. 12 V and internal resistance $0.50 \text{ }\Omega$ drives a current of 2.0 A. What is the terminal p.d.?
_____ V
- A $3.0 \text{ }\Omega$ and a $6.0 \text{ }\Omega$ resistor are in series. What is the total resistance?
_____ Ω
- In a potential divider, the p.d. across each resistor is proportional to its resistance.
☐ True ☐ False
- A cell of e.m.f. 6.0 V and internal resistance $0.50 \text{ }\Omega$ is short-circuited. What current flows?
_____ A
- Replacing one resistor in a divider with an LDR makes the output voltage depend on:
☐ the light level
☐ the temperature
☐ the time of day only
☐ nothing
- An ideal ammeter has:
☐ zero resistance, connected in series
☐ infinite resistance, connected in series
☐ zero resistance, connected in parallel
☐ infinite resistance, connected in parallel
- A parallel combination is always smaller than the smallest resistor in it.
☐ True ☐ False

A-Level Physics

- source**
The source (battery, cell, generator) supplies energy to the charge; a component takes it back out (the p.d.).
- 3 A**
Current in = current out: $5.0 = 2.0 + I$, so $I = 3.0 \text{ A}$.
- 8 V**
 $V_{\text{out}} = V_{\text{in}} \frac{R_2}{R_1 + R_2} = 12 \times \frac{4.0}{2.0 + 4.0} = 8.0 \text{ V}$.
- 11 V**
 $V = \varepsilon - Ir = 12 - 2.0 \times 0.50 = 11 \text{ V}$.
- 9 Ω**
 $R = R_1 + R_2 = 3.0 + 6.0 = 9.0 \text{ }\Omega$.
- True**
The same current flows through both, so $V = IR$ means the bigger resistor takes the bigger share.
- 12 A**
With $R_{\text{ext}} \rightarrow 0$, $I = \frac{\varepsilon}{r} = \frac{6.0}{0.50} = 12 \text{ A}$.
- the light level**
An LDR's resistance changes with light, so its share of the voltage — the output — tracks the brightness.
- zero resistance, connected in series**
An ammeter goes in series and should add no resistance, so an ideal one has zero resistance.
- True**
Yes — adding a parallel path gives the current another route, lowering the overall resistance.