

21. Alternating currents

Starter Quiz · 课前小测

A-Level Physics

Name: _____ Score: _____

1. An alternating current:

- ☐ reverses direction periodically
- ☐ flows one way only
- ☐ never changes
- ☐ has no frequency

2. A diode conducts current:

- ☐ in one direction only
- ☐ in both directions
- ☐ never
- ☐ only at very high voltage

3. In $V = V_0 \sin(\omega t)$ the coefficient of t is the _____ frequency, equal to $2\pi f$.

4. Half-wave rectification uses _____ diode.

5. Mains supply is 50 Hz. What is its period?

_____ s

6. Where does a smoothing capacitor go?

- ☐ in parallel with the load
- ☐ in series with the load
- ☐ in series with the diode
- ☐ across the a.c. supply, before the diodes

7. On a CRO trace one complete cycle spans 4.0 divisions with the time-base at 5.0 ms per division. What is the frequency, in Hz?

8. How many diodes are in a bridge (full-wave) rectifier?

9. The average power of a.c. in a resistor is _____ the peak power.

☐ half

☐ equal to

☐ double

☐ a quarter of

10. A full-wave rectified output repeats at twice the frequency of the a.c. input.

☐ True ☐ False

1. **reverses direction periodically**

a.c. keeps swapping direction — mains does so 50 (or 60) times a second.

2. **in one direction only**

This one-way behaviour is what lets diodes rectify a.c. into d.c.

3. **angular**

omega is $2\pi f$, so a supply written $\sin(100\pi t)$ has $f = 50$ Hz, not 100π Hz. The angle is in radians, so a calculator left in degrees turns every such step into nonsense.

4. **one**

A single diode passes the positive half-cycles and blocks the negative ones (leaving gaps).

5. **0.02 s**

$$T = \frac{1}{f} = \frac{1}{50} = 0.020 \text{ s.}$$

6. **in parallel with the load**

It must discharge THROUGH the load between peaks, which needs it in parallel. In series it would block the d.c. entirely, which is the opposite of the point.

7. **50.0**

$T = 4.0 \times 5.0 \text{ ms} = 20 \text{ ms}$, so $f = 1/0.020 = 50$ Hz. Count divisions for a WHOLE cycle, not a half.

8. **4**

Four diodes, arranged so the load current always flows the same way whichever input terminal is positive.

9. **half**

The mean of $\sin^2$ over a cycle is $\frac{1}{2}$, so $\langle P \rangle = \frac{1}{2} P_{\text{peak}}$.

10. **True**

Both half-cycles become positive humps, so the output ripples at double the input frequency.