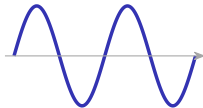


Alternating Current


A2 Physics ■ Topic 21

A-Level Physics




What we will cover

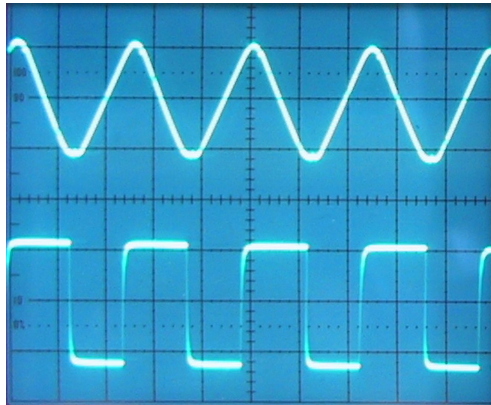- 1 AC basics
- 2 Power in a resistor
- 3 Root-mean-square values
- 4 Rectification
- 5 Smoothing
- 6 Recap



Alternating current

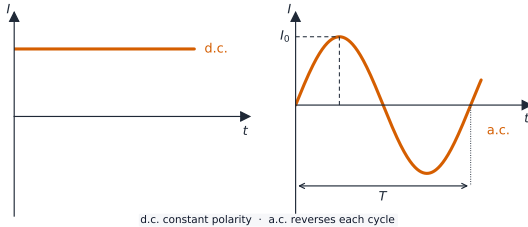

substation

Power delivered to a resistor


The instantaneous power is $P = I^2 R$, which is **always positive** (squaring loses the sign):

$$P = I_0^2 R \sin^2(2\pi ft)$$


Over a cycle $\sin^2$ averages to $\frac{1}{2}$, so

$$\langle P \rangle = \frac{1}{2} I_0^2 R$$

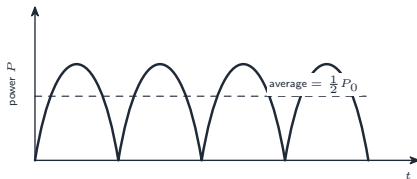Power peaks **twice** per cycle – once each polarity – because the heating does not care which way the current flows.



R.m.s. values

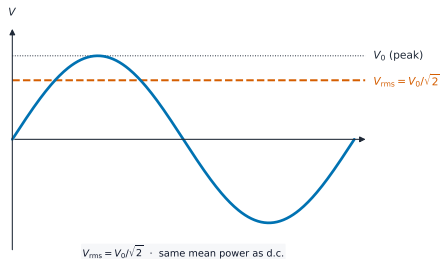

The **r.m.s.** 均方根 value is the **steady DC** that would deliver the same average power:

$$I_{rms} = \frac{I_0}{\sqrt{2}}, \quad V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$\langle P \rangle = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

Divide by $\sqrt{2}$ only for a **sine** wave.
R.m.s. is what a meter reads and what “230 V” means.

Worked example – r.m.s. and power


A sinusoidal supply has a peak voltage of 325 V across a 100 Ω resistor. Find V_{rms} and the mean power.

$$V_{\text{rms}} = \frac{325}{\sqrt{2}} \approx 230 \text{ V}$$

$$\langle P \rangle = \frac{V_{\text{rms}}^2}{R} = \frac{230^2}{100} \approx 530 \text{ W}$$

Use **r.m.s.** values in every power formula. Using the peak would overstate the power by a factor of two.

Rectification

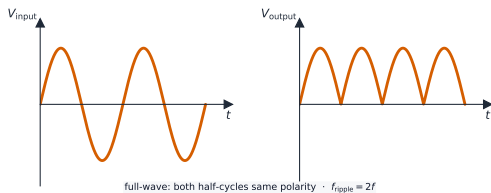


A **diode** 二极管 conducts one way only, turning AC into one-directional DC:

- **half-wave**: one diode, blocks the reverse half
- **full-wave**: a **bridge** of four diodes flips the reverse half up

Full-wave uses **both** halves, so the output is smoother and delivers more power.

Smoothing with a capacitor

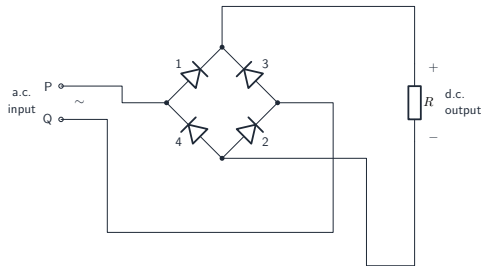

A capacitor across the output **charges** on each peak and **discharges** through the load between peaks:

- it fills in the dips, leaving a small **ripple** 纹波
- bigger C (or R) $\Rightarrow$ slower discharge $\Rightarrow$ smaller ripple

The smoothing time constant RC must be **long** compared with the time between peaks.

Topic 21 – key takeaways

1 AC

$I = I_0 \sin(2\pi ft)$ – reverses each cycle

2 R.m.s.

$I_0/\sqrt{2}$ – the DC-equivalent for power

3 Rectify


diodes make DC; a bridge is full-wave

4 Smooth

a capacitor fills the dips; big RC = small ripple

Check yourself

- 1 Peak voltage 325 V – what is V_{rms} ?
- 2 Why is mean power $\frac{1}{2} I_0^2 R$?
- 3 How many diodes in a bridge rectifier?
- 4 What makes the ripple smaller?

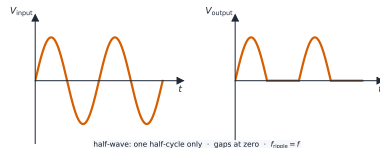

Answers 1. $\approx 230 \text{ V}$ 2. $\langle \sin^2 \rangle = \frac{1}{2}$ 3. four 4. a larger C (longer RC)