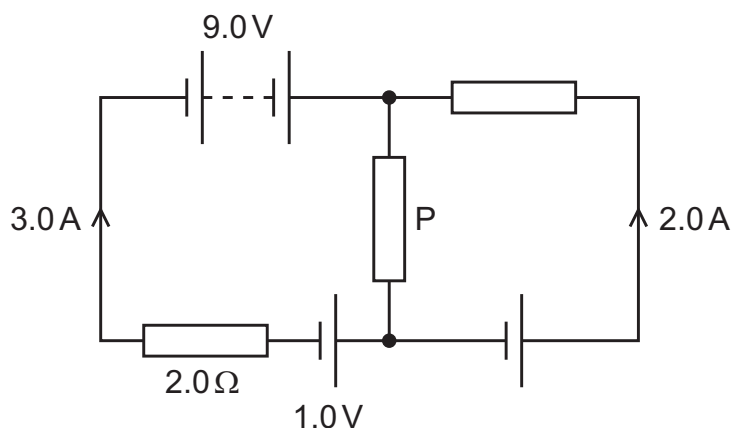


34 The diagram shows a circuit containing a battery and cells with negligible internal resistance.

Some values of current, electromotive force (e.m.f.) and resistance are shown.


One resistor is labelled P.



What is the resistance of resistor P?

- A** $0.40\ \Omega$ **B** $0.80\ \Omega$ **C** $2.0\ \Omega$ **D** $2.8\ \Omega$

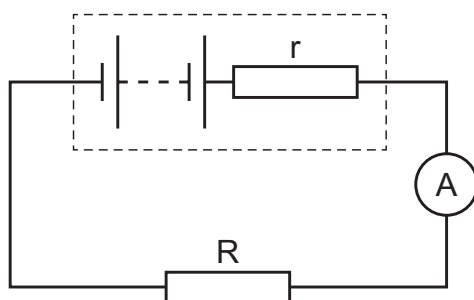35 The diagram shows a circuit with a battery connected to a resistor R. The battery has an internal resistance represented by resistor r.




A second resistor, identical to R, is connected in parallel with R.

Which row describes the changes to the potential difference (p.d.) across r and the current shown on the ammeter when the second resistor is connected?

	p.d. across r	current shown on ammeter
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases

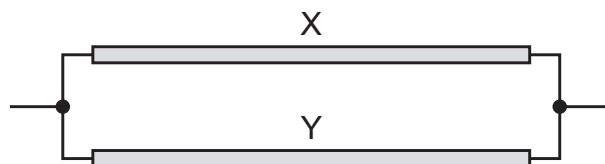- 36** Two identical wires X and Y, each of length L and radius r , are connected in parallel as shown.



The total resistance of this combination is R_1 .

Wire X is replaced with a wire of the same material with length L and radius $2r$.

The total resistance of the new combination is R_2 .

What is the ratio $\frac{R_1}{R_2}$?


A $\frac{2}{5}$

B $\frac{2}{3}$

C $\frac{3}{2}$

D $\frac{5}{2}$

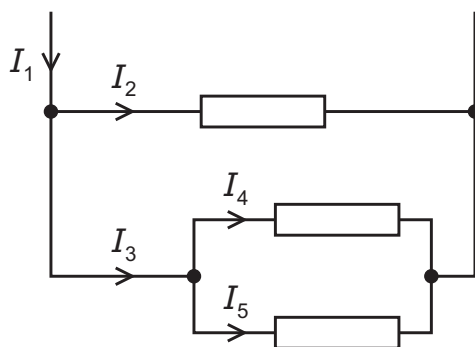- 37** The diagram shows the currents in part of an electric circuit.



The resistors are identical.

Which equation is **not** correct?

A $I_1 = I_2 + I_4 + I_5$

B $I_2 = I_1 - I_3$

C $I_2 = I_3 + I_4 + I_5$

D $I_4 = I_3 - I_5$

5 (a) State Kirchhoff's first law.

.....
..... [1]

(b) Fig. 5.1 shows a circuit containing a thermistor T that has a negative temperature coefficient.

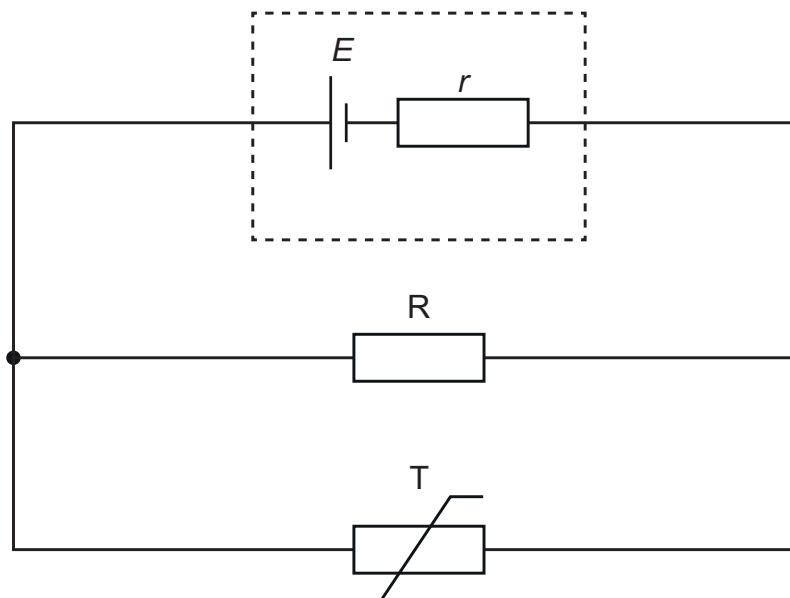


Fig. 5.1

(i) The thermistor has resistance R_0 at a temperature of 0°C .

On Fig. 5.2, sketch a possible variation of the resistance of the thermistor with temperature between 0°C and 100°C .

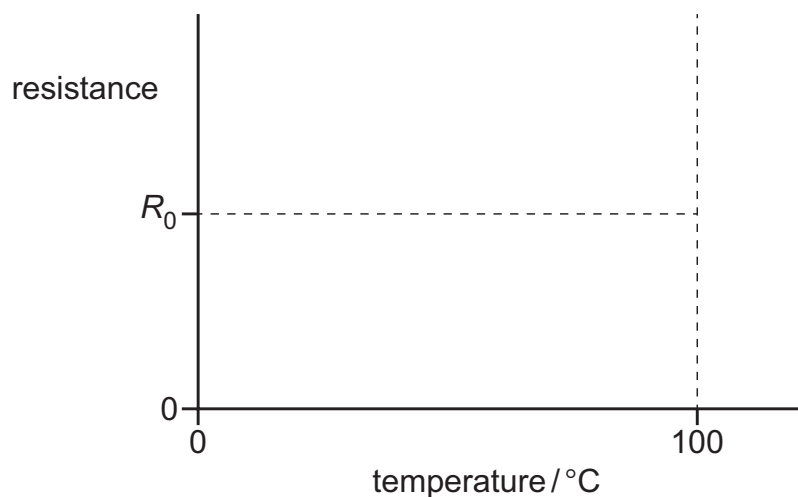


Fig. 5.2

[2]

(ii) With reference to the current in the cell, explain why the current in **resistor R** decreases with increasing temperature of the thermistor.

.....

.....

.....

.....

..... [3]

(c) The electromotive force (e.m.f.) E of the cell in Fig. 5.1 is 1.50 V. The internal resistance r of the cell is $0.12\,\Omega$.

Resistor R has a resistance of $6.00\,\Omega$.

At a particular temperature of the thermistor, the current in R is 0.200 A.

For this temperature of the thermistor, determine:

(i) the current in the cell

current = A [2]

(ii) the resistance of the thermistor.

resistance = Ω [2]

[Total: 10]

- 5 Fig. 5.1 shows a circuit containing a battery, two fixed resistors X and Y, and a light-dependent resistor (LDR) Z.

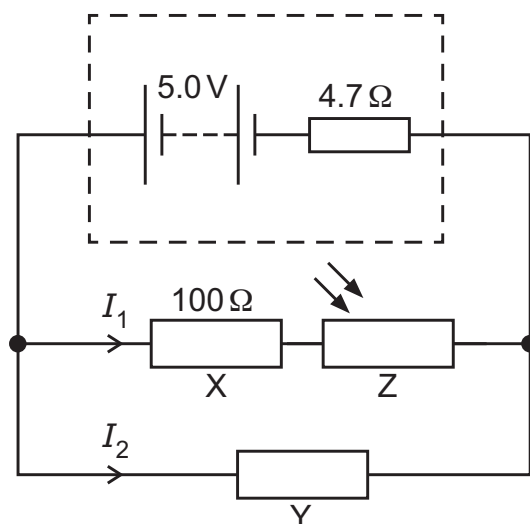


Fig. 5.1

The battery has electromotive force (e.m.f.) 5.0 V and internal resistance $4.7\ \Omega$. The current in X is I_1 and the current in Y is I_2 .

The resistance of X is $100\ \Omega$. The resistance of Z varies with the intensity of light incident on it as shown in Fig. 5.2.

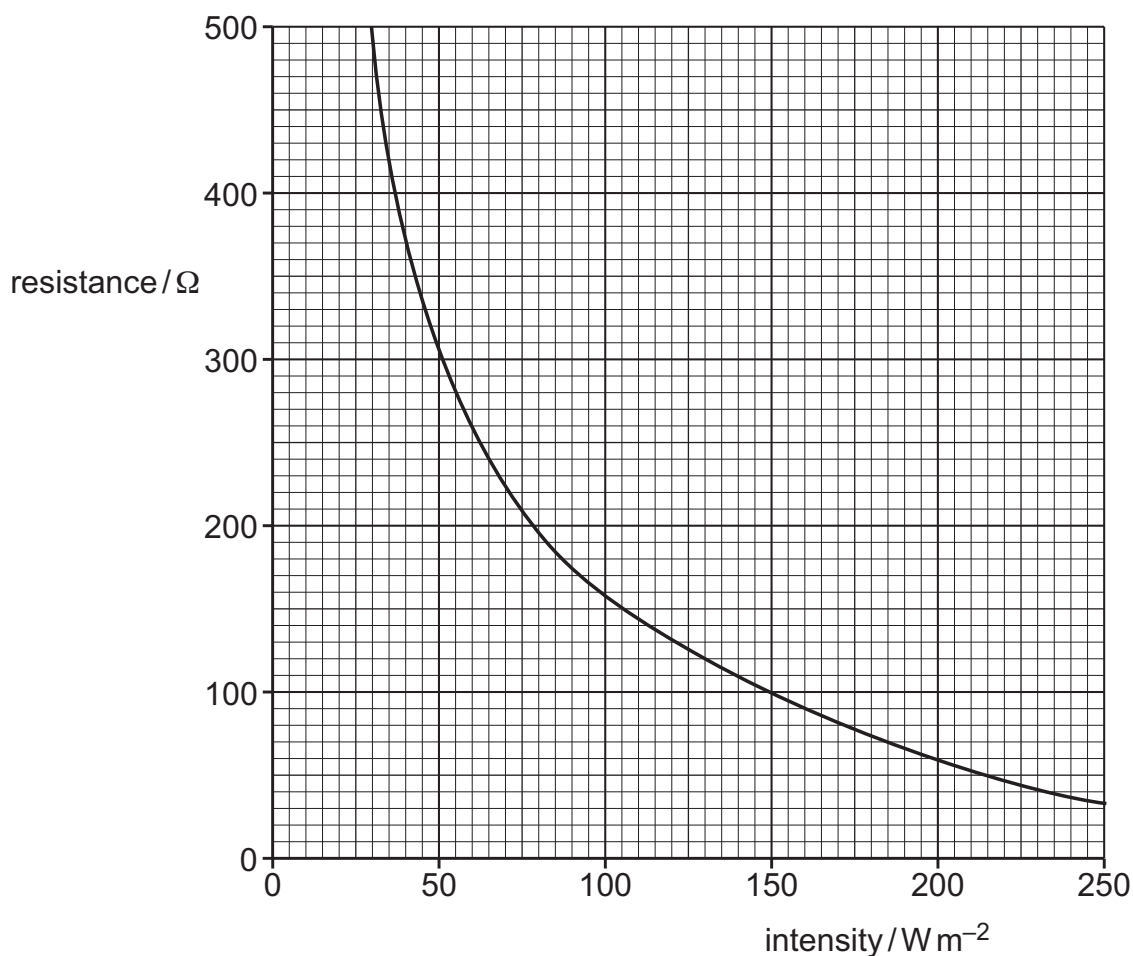


Fig. 5.2

(a) State Kirchhoff’s first law.

.....
..... [1]

(b) The intensity of light incident on Z is 130 W m^{-2} . The current in the battery is 38 mA.

(i) Show that the terminal potential difference of the battery is 4.8 V.

[2]

(ii) Calculate the current I_2 in Y.

$I_2 =$ A [3]

(iii) Calculate the power dissipated in Y.

power = W [2]

(iv) The intensity of the light incident on Z decreases.

State and explain the effect on the terminal potential difference of the battery.

.....
.....
.....
.....
..... [3]

- 1 Fig. 1.1 shows a model wind turbine with blades, each of length L , placed in moving air.

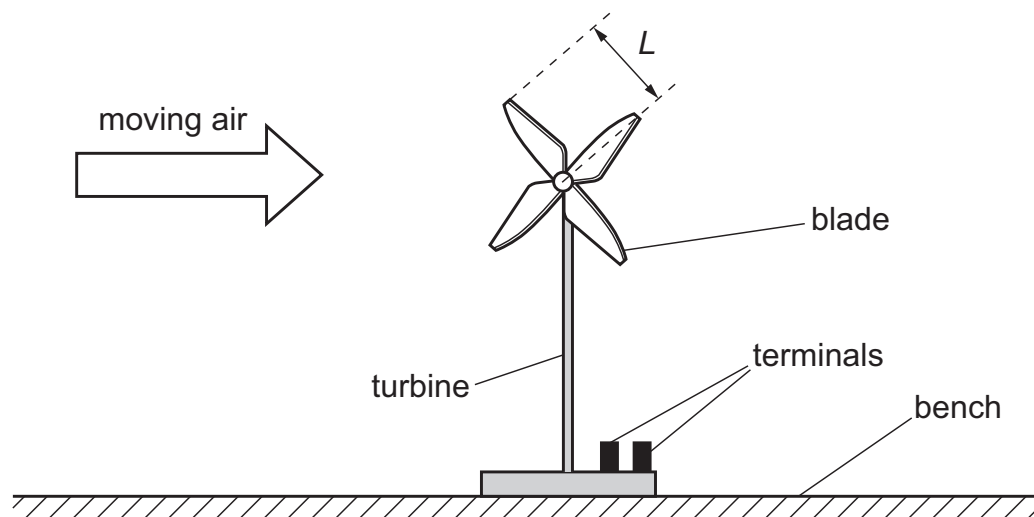


Fig. 1.1

The area of the circle swept by the blades of the turbine is A .

The output of the turbine has two terminals. The turbine is connected to a resistor of resistance R . At a speed v of the moving air, the current in the resistor is I .

The atmospheric pressure is P and the thermodynamic temperature of the air is T .

It is suggested that I is related to v by the relationship

$$\frac{I^2 R}{Q} = \frac{APv^3}{2T}$$

where Q is a constant.

Plan a laboratory experiment to test the relationship between I and v .

Draw a diagram showing the arrangement of your equipment.

Explain how the results could be used to determine a value for Q .

In your plan you should include:


- the procedure to be followed
- the measurements to be taken
- the control of variables
- the analysis of the data
- any safety precautions to be taken.

Diagram

[illegible]

[illegible]

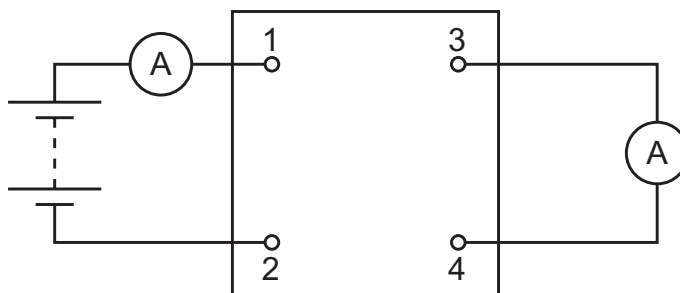
36 The diagram shows a four-terminal box connected to a battery and two ammeters.




The currents in the two ammeters are identical.

Which circuit, within the box, gives this result?


A

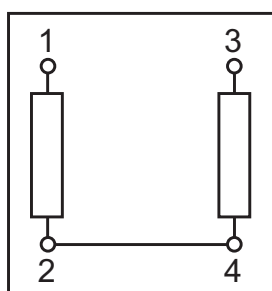

B

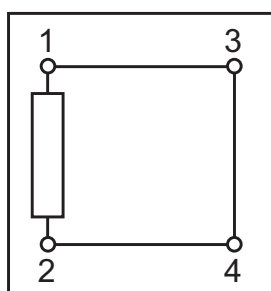

C

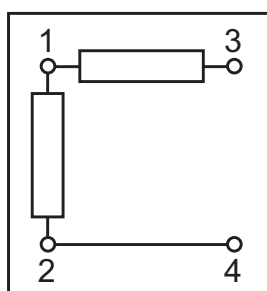

D

