

7 An alternating voltage V varies with time t according to

$$V = 18 \cos 40\pi t$$

where V is in V and t is in s.

(a) For the alternating voltage:

(i) show that the period is 0.050 s

[1]

(ii) determine the root-mean-square (r.m.s.) voltage.

r.m.s. voltage = V [1]

(b) On Fig. 7.1, sketch the variation of V with t for values of t from $t = 0$ to $t = 100$ ms.

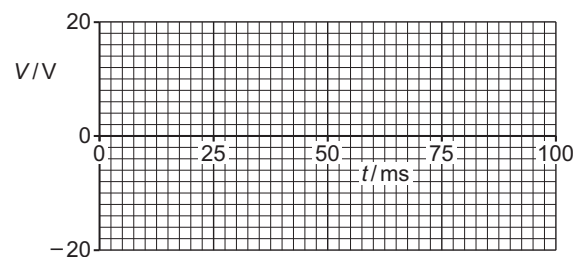


Fig. 7.1

[3]

(c) The alternating voltage is rectified to produce an output voltage across a load resistor R , as shown in Fig. 7.2.

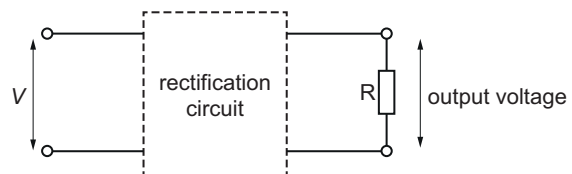


Fig. 7.2

①

Fig. 7.3 shows the variation with t of the power P in the load resistor.

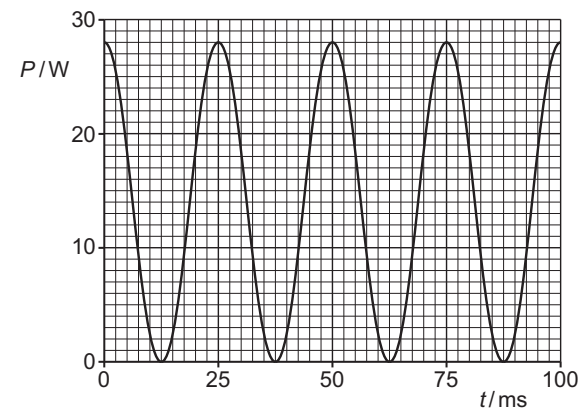


Fig. 7.3

State **three** conclusions that can be drawn from Fig. 7.3. The conclusions may be qualitative or quantitative. Use the space for any working.

- 1
- 2
- 3

[3]

[Total: 8]

②

- 6 Fig. 6.1 shows part of a bridge rectifier circuit that can be used for rectification of an alternating input voltage V_{IN} .

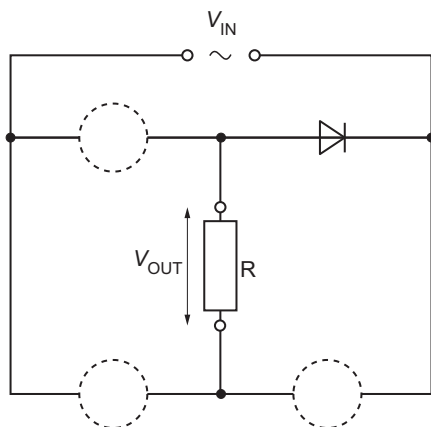


Fig. 6.1

The circuit contains four diodes, one of which is shown.
The rectified output voltage V_{OUT} is applied across load resistor R .

- (a) (i) State what is meant by rectification.
.....
..... [1]
- (ii) State the name of the type of rectification produced by a bridge rectifier circuit.
..... [1]
- (iii) Complete the circuit in Fig. 6.1 by drawing the three missing diodes inside the dashed circles. [2]

- (b) The input voltage varies with time t according to the equation

$$V_{IN} = 34 \sin 18t$$

where V_{IN} is in V and t is in s.

- (i) Show that the period of the input voltage is 0.35 s.

[2]

- (ii) Calculate the root-mean-square (r.m.s.) input voltage.

r.m.s. voltage = V [1]

- (iii) On Fig. 6.2, sketch the variation of V_{OUT} with t from $t = 0$ to $t = 0.35$ s.

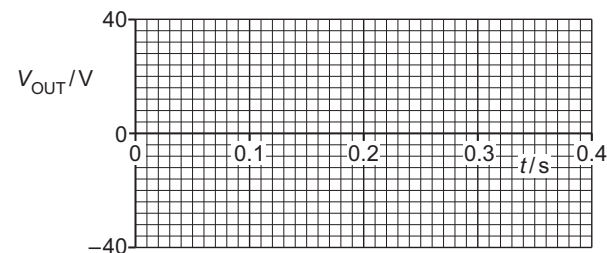


Fig. 6.2

[3]

(c) Resistor R has a resistance of $56\text{ k}\Omega$. A capacitor of capacitance $12\text{ }\mu\text{F}$ is connected into the circuit of Fig. 6.1 in order to smooth the output voltage.

(i) On Fig. 6.1, draw the capacitor correctly connected into the circuit. [1]

(ii) Calculate the time constant of the smoothing circuit.

time constant = s [2]

(iii) During each discharge cycle, the time for which the capacitor is discharging is 0.14 s .

Determine the minimum value of the smoothed output voltage.

minimum voltage = V [2]

[Total: 15]

8 An incomplete circuit diagram of a bridge rectifier is shown in Fig. 8.1.

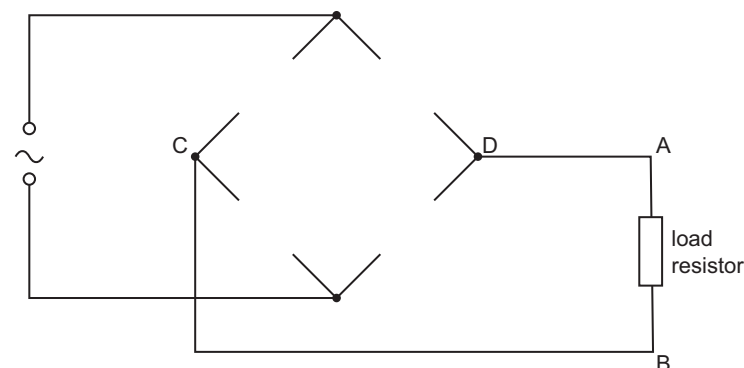


Fig. 8.1

(a) Complete Fig. 8.1 for the bridge rectifier such that the point A is at a positive potential with respect to point B. [2]

(b) The variation with time t of the potential difference (p.d.) V across the load resistor is shown in Fig. 8.2.

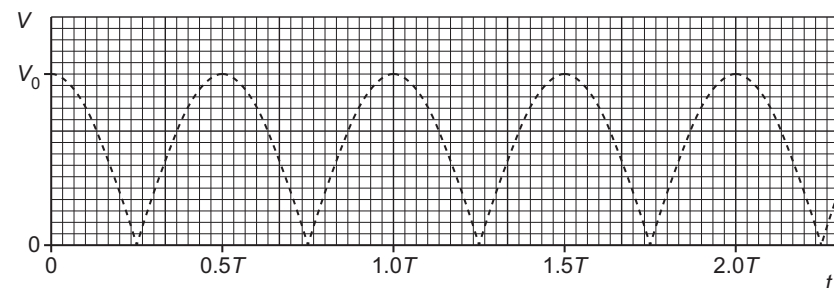


Fig. 8.2

A capacitor is now connected between points C and D of the bridge rectifier. This results in smoothing of the p.d. across the load resistor. The difference between the maximum and minimum values of the smoothed p.d. is 33% of the peak p.d. V_0 .

(i) On Fig. 8.2, draw a line to show the variation of the potential difference V across the load resistor with time t . Your line should extend from $t = 0.5T$ to $t = 2.0T$. [3]

- (ii) Use your line in (b)(i) to determine, in terms of T , the time constant of the smoothing circuit.

time constant = T [3]

- (iii) The resistance of the load resistor is now increased. The capacitance of the capacitor is unchanged.

State and explain the effect of this change on the smoothed output p.d.

.....

 [2]

[Total: 10]

- 1 Fig. 1.1 shows a thin coil of cross-sectional area A and length l connected to a resistor of resistance S and two terminals.

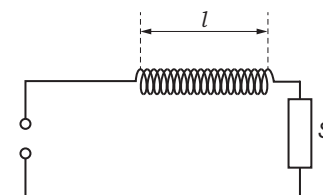


Fig. 1.1

An alternating voltage is applied to the terminals. The peak value of the alternating voltage is E and the frequency is f . The peak value of the potential difference V across the resistor is determined using an oscilloscope.

It is suggested that V is related to f by the relationship

$$\frac{ES}{V} = \frac{KAN^2f}{l}$$

where N is the number of turns on the coil and K is a constant.

Plan a laboratory experiment to test the relationship between V and f .

Draw a diagram showing the arrangement of your equipment.

Explain how the results could be used to determine a value for K .

In your plan you should include:

- the procedure to be followed
- the measurements to be taken
- the control of variables
- the analysis of the data
- any safety precautions to be taken.

[illegible][illegible]