

AP Physics 2

Name: _____ Score: _____

1. 6 C of charge flows past a point in 3 s. What is the current, in amperes?
_____ A
2. For current to flow in a circuit, the loop must be:
☐ made only of copper
☐ very long
☐ complete (closed)
☐ open
3. A resistor carries 0.5 A from a 6 V supply. What is its resistance, in Ω ?
_____ Ω
4. A bulb carries 0.5 A at 12 V. What power does it dissipate, in watts?
_____ W
5. Two 6 Ω resistors are in **series**. What is the total resistance, in Ω ?
_____ Ω
6. A 9 V battery drives current through $R_1 = 2 \Omega$ and $R_2 = 1 \Omega$ in series. Using the loop rule, what is the current, in A?
_____ A
7. Kirchhoff's junction rule is a statement of the conservation of:
☐ charge
☐ energy
☐ momentum
☐ voltage
8. As a capacitor charges through a resistor, its charge rises:
☐ exponentially toward a final value
☐ not at all
☐ instantly to full
☐ linearly (a straight line)
9. Electric current is defined as:

- ☐ charge per unit time
- ☐ charge times time
- ☐ voltage per unit charge
- ☐ resistance times charge

10. The voltage a battery provides – its energy per unit charge – is called its _____.

AP Physics 2

1. **2 A**

$$I = Q/t = 6/3 = 2 \text{ A.}$$

2. **complete (closed)**

A complete, closed loop is needed; any break stops the current.

3. **12 Ω**

$$R = V/I = 6/0.5 = 12 \text{ } \Omega.$$

4. **6 W**

$$P = IV = 0.5 \times 12 = 6 \text{ W.}$$

5. **12 Ω**

Series resistances add: $6 + 6 = 12 \text{ } \Omega$.

6. **3 A**

$$9 - 2I - I = 0 \Rightarrow 9 = 3I \Rightarrow I = 3 \text{ A.}$$

7. **charge**

Charge can't pile up at a point, so current in equals current out.

8. **exponentially toward a final value**

Charge rises exponentially toward $Q = CV$, fast at first then slowing.

9. **charge per unit time**

$I = Q/t$ – charge flowing per second.

10. **EMF**

The electromotive force (EMF) is the battery's energy per unit charge.