

Exercise walk-through

Compound DC Circuits ■ 11.5

eXercise

You must be able to

- combine resistors in **series** 串联 ($R_s = R_1 + R_2 + \dots$) and in **parallel** 并联 ($\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$)
- account for the **internal resistance** 内阻 of a real battery and its terminal voltage
- analyse a circuit with mixed series and parallel sections

Method — Series and parallel

- **Series:** same current, $R_s = R_1 + R_2 + \dots$ (resistance adds up).
- **Parallel:** same voltage, $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$ (total is **less** than the smallest).

Method — Internal resistance

A real cell has internal resistance r , so the terminal voltage is $V = \varepsilon - Ir$.

Method — Example

Two $4.0\ \Omega$ resistors in parallel: $\frac{1}{R_p} = \frac{1}{4} + \frac{1}{4} \Rightarrow R_p = 2.0\ \Omega$.

Practice 2.1 ■ 1 mark

Two $6.0\ \Omega$ resistors are connected in series. Find the total resistance.

Solution 2.1

Method: Series and parallel

Worked steps

$$R_s = 6.0 + 6.0 = 12 \, \Omega \quad \text{B1}.$$

Practice 2.2 ■ 2 marks

The same two $6.0\ \Omega$ resistors are connected in parallel. Find the total resistance.

Solution 2.2

Method: Series and parallel

Worked steps

$$\frac{1}{R_p} = \frac{1}{6.0} + \frac{1}{6.0} = \frac{2}{6.0} \Rightarrow R_p = 3.0 \, \Omega \quad \text{M1 A1}.$$

Practice 2.3 ■ 2 marks

A battery of emf 12 V and internal resistance $0.50\ \Omega$ drives a current of 2.0 A. Find the terminal voltage.

Solution 2.3

Method: Internal resistance

Worked steps

$$V = \varepsilon - Ir = 12 - 2.0(0.50) = 11 \text{ V} \quad \text{M1} \quad \text{A1}.$$

Exam-style 3.1 ■ 1 mark

Resistors in series have a total resistance equal to

- A** less than the smallest
- B** the sum of the individual resistances
- C** their average
- D** their product

Solution 3.1

Method: Series and parallel

- A less than the smallest
- B the sum of the individual resistances
- C their average
- D their product



Worked steps

B.

Exam-style 3.2 ■ 1 mark

Adding another resistor in parallel makes the total resistance

- A** larger
- B** smaller
- C** unchanged
- D** infinite

Solution 3.2

Method: Series and parallel

A larger

B smaller



C unchanged

D infinite

Worked steps

B.

Exam-style 3.3 ■ 2 marks

A $3.0\ \Omega$ and a $6.0\ \Omega$ resistor are in parallel across a $12\ \text{V}$ supply.

- (a) Find the combined resistance.
- (b) Find the total current drawn from the supply.

Solution 3.3

Method: Series and parallel

Worked steps

$$(a) \frac{1}{R_p} = \frac{1}{3.0} + \frac{1}{6.0} = \frac{3}{6.0} \Rightarrow R_p = 2.0 \, \Omega \quad \text{M1 A1.} \quad (b) I = \frac{V}{R_p} = \frac{12}{2.0} = 6.0 \, \text{A}$$

M1 A1.