

Exercise walk-through

RC Circuits ■ 11.8

eXercise

You must be able to

- describe how a **capacitor** 电容器 charges and discharges through a resistor over time
- relate the **time constant** 时间常数 $\tau = RC$ to how quickly the circuit responds
- describe the current and voltage at the start and after a long time

Method — Charging and discharging

A capacitor charges up through a resistor, its voltage rising toward the supply value; it discharges the same way in reverse.

Method — Time constant

$\tau = RC$ (seconds) sets the pace: a bigger R or C means slower charging.

Method — Start and steady state

At $t = 0$ the uncharged capacitor acts like a **wire** (maximum current); after a long time it is **fully charged** and the current is **zero**.

Practice 2.1 ■ 2 marks

Find the time constant of a $2000\ \Omega$ resistor and a $50\ \mu\text{F}$ capacitor.

Solution 2.1

Worked steps

$$\tau = RC = 2000 \times 50 \times 10^{-6} = 0.10 \text{ s} \quad \text{M1} \quad \text{A1}.$$

Practice 2.2 ■ 1 mark

State the current through the capacitor a long time after charging begins.

Solution 2.2

Method: Start and steady state

Worked steps

zero (the capacitor is fully charged) **B1**.

Practice 2.3 ■ 1 mark

State what happens to the charging rate if the resistance is increased.

Solution 2.3

Worked steps

it slows down (a larger $\tau = RC$) **B1**.

Exam-style 3.1 ■ 1 mark

The time constant of an RC circuit is

A R/C

B RC

C $R + C$

D C/R

Solution 3.1

Method: Time constant

A R/C

B RC



C $R + C$

D C/R

Worked steps

B.

Exam-style 3.2 ■ 1 mark

A long time after charging begins, the current in an RC circuit is

- A** at its maximum
- B** zero
- C** constant and large
- D** negative

Solution 3.2

Method: Start and steady state

A at its maximum

B zero



C constant and large

D negative

Worked steps

B.

Exam-style 3.3 ■ 2 marks

A $10\text{ k}\Omega$ resistor charges a $100\text{ }\mu\text{F}$ capacitor from a 9.0 V supply.

- (a) Find the time constant.
- (b) State the final voltage across the capacitor.

Solution 3.3

Method: Charging and discharging

Worked steps

(a) $\tau = RC = (10 \times 10^3)(100 \times 10^{-6}) = 1.0 \text{ s}$ **M1** **A1**. (b) 9.0 V (the supply voltage) **B1**.