

## Question 2

12 points total

Distribution  
of points

(a)

i. 5 points

- |                                                                                                                                         |         |
|-----------------------------------------------------------------------------------------------------------------------------------------|---------|
| For drawing a circuit with the battery, rod, and ammeter in series (rods can be drawn to look like rods, or schematically as resistors) | 1 point |
| For drawing the voltmeter parallel to the rod, or indicating that the setting on the power supply will be used                          | 1 point |
| For measuring potential difference and current for a rod                                                                                | 1 point |
| For measuring the length and diameter of a rod                                                                                          | 1 point |
| For including multiple trials with appropriate controls                                                                                 | 1 point |
| Examples: 1) Use one rod and apply different potential differences                                                                      |         |
| 2) Use different rods                                                                                                                   |         |

ii. 2 points


- |                                                                                                            |         |
|------------------------------------------------------------------------------------------------------------|---------|
| For graphing appropriate quantities whose slope can be used to calculate resistance directly or indirectly | 1 point |
| For correctly stating how the slope relates to the resistivity                                             | 1 point |

## 2017 SCORING GUIDELINES

## Question 2 (continued)

Distribution  
of points

(b) 3 points

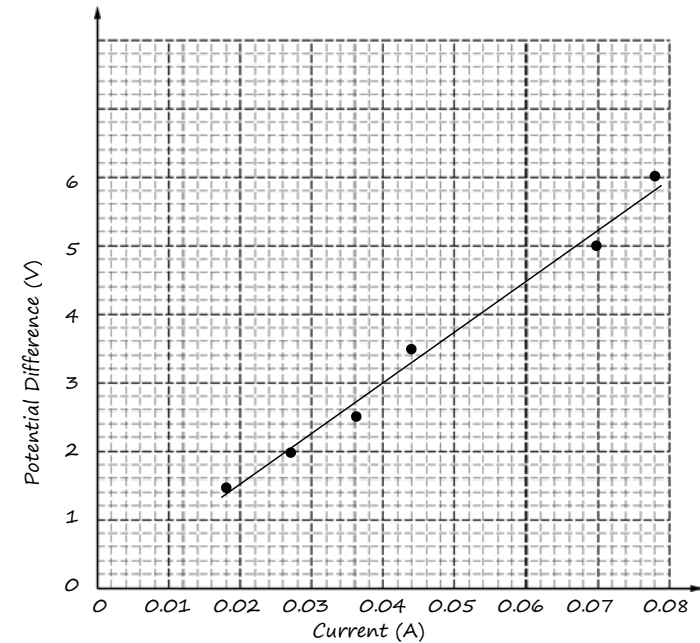

- |                                                                                                                                                 |         |
|-------------------------------------------------------------------------------------------------------------------------------------------------|---------|
| For plotting the data on the graph with potential difference on one axis and current on the other, labeled with units, using a reasonable scale | 1 point |
| For a clearly shown calculation of slope from a reasonable best-fit line                                                                        | 1 point |
| For a correct answer with units                                                                                                                 | 1 point |
- Acceptable range is  $70 - 79 \, \Omega$ .

For a graph of  $I$  as a function of  $V$ , the slope should end up near  $0.013 \, \Omega^{-1}$  and the resistance is the inverse

For a graph of  $V$  as a function of  $I$ , the slope should end up near  $74 \, \Omega$  and equals the resistance

For the example shown above

$$\text{slope} = \frac{(5.8 - 2.4) \, \text{V}}{(0.078 - 0.032) \, \text{A}} = 73.9 \, \Omega$$

**2017 SCORING GUIDELINES****Question 2 (continued)****Distribution  
of points**

(c)

i. 1 point

For indicating that the internal resistance of the power supply will not affect the data acquired, with correct reasoning

1 point

Example: Because potential difference is measured across each rod,  $\Delta V/I$  is not affected by the internal resistance of the battery.

ii. 1 point

For indicating either:

The students should be concerned because a change in temperature causes a change in the resistance or resistivity.

1 point

OR

The students should not be concerned because any change in resistivity as the temperature increases is small compared to measurement error.