

Exercise walk-through

11.6

Kirchhoff's Loop Rule

AP Physics C: Electricity and Magnetism

You must be able to

- state **Kirchhoff's loop rule** $\sum \Delta V = 0$ around any closed loop
- explain it as a consequence of **conservation of energy**
- assign consistent **sign conventions** for emf sources and resistors
- write and solve **loop equations**

1

The method

Method — The loop rule

Around any closed loop, $\sum \Delta V = 0$ – the rises across the emf sources balance the drops across the resistors.

Exercises 2.1-2.2

2.1 State Kirchhoff's loop rule.

[1]

2.2 State the conservation law the loop rule expresses.

[1]

Exercises 2.1-2.2

2.1 State Kirchhoff's loop rule.

[1]

2.1

- the sum of the potential differences around any closed loop is zero

2.2 State the conservation law the loop rule expresses.

[1]

2.2

- conservation of energy

Exercises 2.3-3.1

2.3 A single loop has a 10 V battery and resistors $2.0\ \Omega$ and $3.0\ \Omega$ in series. Find the current. [2]

3.1 Kirchhoff's loop rule sums the potential differences around a closed loop to [1]

☐

A the emf

B zero

C a maximum

D infinity

Exercises 2.3-3.1

2.3 A single loop has a 10 V battery and resistors $2.0\ \Omega$ and $3.0\ \Omega$ in series. Find the current. [2]

2.3

- loop rule: the emf equals the sum of the drops:

$$\varepsilon = IR_1 + IR_2 \quad \Rightarrow \quad I = \frac{10\ \text{V}}{2.0\ \Omega + 3.0\ \Omega}$$

- $I = 2.0\ \text{A}$

3.1 Kirchhoff's loop rule sums the potential differences around a closed loop to [1]

☐

A the emf

B zero

C a maximum

D infinity

3.1 B

- zero.

Exercise 3.2

3.2 The loop rule expresses conservation of

[1]

☐

A charge

B energy

C momentum

D mass

Exercise 3.2

3.2 The loop rule expresses conservation of

[1]

☐

A charge

B energy

C momentum

D mass

3.2 B

- energy.

Exercise 3.3 (a)

3.3 A single loop contains a 12 V battery and resistors of $3.0\ \Omega$ and $1.0\ \Omega$ in series.

(a) Write the loop equation.

[2]

Exercise 3.3 (a)

3.3 A single loop contains a 12 V battery and resistors of $3.0\ \Omega$ and $1.0\ \Omega$ in series.

(a) Write the loop equation.

[2]

(a)

- going round the loop, the emf rise equals the two drops:



$$12\text{ V} - I(3.0\ \Omega) - I(1.0\ \Omega) = 0$$

Exercise 3.3 (b)

3.3 A single loop contains a 12 V battery and resistors of $3.0\ \Omega$ and $1.0\ \Omega$ in series.

(b) Find the current.

[1]

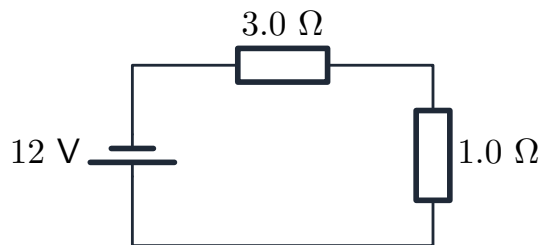
 


Exercise 3.3 (b)

3.3 A single loop contains a 12 V battery and resistors of $3.0\ \Omega$ and $1.0\ \Omega$ in series.

(b) Find the current.

[1]

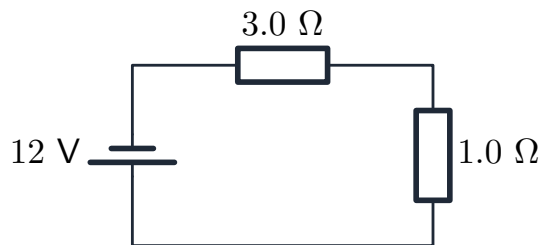 

(b)

- $$I = \frac{12\text{ V}}{4.0\ \Omega} = \mathbf{3.0\text{ A}}$$