

Exercise walk-through

Electric Circuits ■ 11.2

eXercise

You must be able to

- identify the components of a circuit: **source of emf** 电动势源, resistors, wires, switches
- distinguish an **open**, a **closed**, and a **short circuit** 短路
- describe an **ideal battery** as a source of constant potential difference
- state how **ammeters** and **voltmeters** are connected

Method — Components

A source of emf, resistors, connecting wires, and switches — each with a standard schematic symbol.

Method — Circuit states

- **Open** — broken loop, no current.
- **Closed** — complete loop, current flows.
- **Short** — a very low-resistance path that lets a large current bypass a component.

Method — Meters

An **ammeter** goes **in series** (to read the current through a branch); a **voltmeter** goes **in parallel** (to read the potential difference across a component).

Practice 2.1 ■ 1 mark

State how an ammeter is connected in a circuit.

Solution 2.1

Worked steps

in series **B1**.

Practice 2.2 ■ 1 mark

State how a voltmeter is connected.

Solution 2.2

Worked steps

in parallel with the component **B1**.

Practice 2.3 ■ 2 marks

State the difference between an open and a closed circuit.

Solution 2.3

Method: Circuit states

Worked steps

a closed circuit is a complete loop that carries current; an open circuit is broken, so no current flows **B1** **B1**.

Exam-style 3.1 ■ 1 mark

An ammeter is connected in

- A** series
- B** parallel
- C** either way
- D** neither way

Solution 3.1

A series



B parallel

C either way

D neither way

Worked steps

A.

Exam-style 3.2 ■ 1 mark

A short circuit is a path of

A very high resistance

B very low resistance

C no current at all

D infinite voltage

Solution 3.2

Method: Circuit states

A very high resistance

B very low resistance



C no current at all

D infinite voltage

Worked steps

B.

Exam-style 3.3 ■ 1 mark

A circuit has a battery, a resistor, an ammeter, and a voltmeter across the resistor.

- (a) State how the ammeter is connected.
- (b) State how the voltmeter is connected.
- (c) Explain why a voltmeter should have a very high resistance.

Solution 3.3

Worked steps

(a) in series **B1**. (b) in parallel with the resistor **B1**. (c) so it draws almost no current and does not disturb the circuit it measures **B1**.