

Exercise walk-through

Circuits with Capacitors and Inductors (LC Circuits) ■ 13.6

eXercise

You must be able to

- describe the **oscillation** 振荡 of charge and current in an LC circuit
- explain the **energy exchange** between the capacitor's electric field and the inductor's magnetic field
- relate the **angular frequency** 角频率 to the elements, $\omega = \frac{1}{\sqrt{LC}}$
- compare LC oscillations with the **simple harmonic motion** of a mass on a spring

Method — LC oscillation

With no resistance, the charge and current **oscillate**: energy sloshes back and forth between the capacitor's electric field and the inductor's magnetic field.

Method — Angular frequency

$$\omega = \frac{1}{\sqrt{LC}}.$$

Method — Like a mass on a spring

The LC circuit is the electrical analogue of simple harmonic motion (L plays the role of mass, $1/C$ the role of stiffness). Conservation of energy links the maximum charge to the maximum current: $\frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} L I^2$.

Practice 2.1 ■ 2 marks

Find the angular frequency of an LC circuit with $L = 2.0 \text{ H}$ and $C = 8.0 \mu\text{F}$.

Solution 2.1

Method: Angular frequency

Worked steps

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2.0)(8.0 \times 10^{-6})}} = 250 \text{ rad s}^{-1} \quad \text{M1 A1}.$$

Practice 2.2 ■ 1 mark

State what oscillates in an LC circuit.

Solution 2.2

Worked steps

the charge on the capacitor and the current in the inductor **B1**.

Practice 2.3 ■ 1 mark

State the mechanical system that an LC circuit is analogous to.

Solution 2.3

Worked steps

a mass on a spring (simple harmonic motion) **B1**.

Exam-style 3.1 ■ 1 mark

The angular frequency of an LC circuit is

A $\frac{1}{LC}$

B $\frac{1}{\sqrt{LC}}$

C $\sqrt{LC}$

D LC

Solution 3.1

Method: Angular frequency

A $\frac{1}{LC}$

B $\frac{1}{\sqrt{LC}}$



C $\sqrt{LC}$

D LC

Worked steps

B.

Exam-style 3.2 ■ 1 mark

In an LC circuit, energy is exchanged between the

- A** resistor and the battery
- B** capacitor and the inductor
- C** two resistors
- D** two batteries

Solution 3.2

- A** resistor and the battery
- B** capacitor and the inductor
- C** two resistors
- D** two batteries



Worked steps

B.

Exam-style 3.3 ■ 3 marks

An LC circuit has $L = 0.50 \text{ H}$ and $C = 20 \mu\text{F}$.

- (a) Find the angular frequency of oscillation.
- (b) State the mechanical system this behaves like.

Solution 3.3

Worked steps

$$(a) \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.50)(20 \times 10^{-6})}} = \frac{1}{\sqrt{1.0 \times 10^{-5}}} = 316 \text{ rad s}^{-1} \quad \text{M1 M1 A1}.$$

(b) a mass oscillating on a spring **B1**.