

11.8 Resistor-Capacitor (RC) Circuits

Name: _____ Class: _____ Date: _____ **Total: 10 marks****KEY WORDS** time constant 时间常数 • steady state 稳态 • rc circuit RC 电路 • resistance 电阻

Objective

Build the skills to answer exam questions on **resistor-capacitor (RC) circuits**.**You must be able to:**

- describe the **charging** and **discharging** of a capacitor through a resistor
- define the **time constant** 时间常数 $\tau = RC$
- use $q(t) = Q(1 - e^{-t/\tau})$ (charging) and $q(t) = Qe^{-t/\tau}$ (discharging)
- analyse the **initial** and **steady-state** behaviour

1 Worked examples

Study these first. Each one shows the method for a question type used later.

■ Charging and discharging

$$q(t) = Q(1 - e^{-t/\tau}) \text{ (charging),} \quad q(t) = Qe^{-t/\tau} \text{ (discharging).}$$

■ Time constant

$\tau = RC$ is the characteristic time; after one τ the charge reaches about 63% (charging) or falls to 37% (discharging).

■ Start and steady state

At $t = 0$ an uncharged capacitor acts like a **wire** (current $I_0 = V/R$); at steady state it is fully charged and carries **no** current.

2 Practice

2.1 Find the time constant of a 5.0 k Ω resistor and a 20 μ F capacitor. [2]

2.2 State the current a long time after charging begins. [1]

2.3 Write the expression for the charge on a **discharging** capacitor. [1]

3 Exam-style questions

3.1 The time constant of an RC circuit is [1]

- | | |
|---|---|
| A | B |
| C | D |
- A** R/C
B RC
C $R + C$
D $1/(RC)$

3.2 At $t = 0$, an uncharged capacitor in an RC circuit behaves like a [1]

- | | |
|---|---|
| A | B |
| C | D |
- A** break in the circuit
B plain wire
C battery
D resistor of infinite resistance

3.3 A 2.0 k Ω resistor charges a 50 μ F capacitor from a 10 V supply.

(a) Find the time constant. [2]

(b) Find the initial current (at $t = 0$). [2]