

13.5 Circuits with Resistors and Inductors (LR Circuits)

Name: _____ Class: _____ Date: _____

Total: 10 marks

KEY WORDS time constant 时间常数 • inductor 电感器 • emf 电动势

Objective

Build the skills to answer exam questions on **circuits with resistors and inductors (LR circuits)**.

You must be able to:

- describe the **growth** and **decay** of current in an LR circuit
- explain how an inductor **opposes changes** in current
- define the **time constant** 时间常数 $\tau = \frac{L}{R}$
- analyse the **initial** and **steady-state** behaviour

1 Worked examples

Study these first. Each one shows the method for a question type used later.

■ Growth and decay

$$I(t) = \frac{\varepsilon}{R} (1 - e^{-t/\tau}) \quad (\text{rising}), \quad I(t) = I_0 e^{-t/\tau} \quad (\text{falling}).$$

■ Time constant

$\tau = \frac{L}{R}$ sets how quickly the current settles.

■ Start and steady state

At $t = 0$ the inductor **opposes** the sudden change, so the current is 0 (it acts like a break); at steady state it passes current freely (like a plain wire), and $I = \varepsilon/R$.

2 Practice

2.1 Find the time constant of a 0.40 H inductor and a 20 Ω resistor. [2]

2.2 State the current in an LR circuit immediately after the switch closes. [1]

2.3 State the steady-state current for an emf of 12 V and $R = 6.0 \Omega$. [1]

3 Exam-style questions

3.1 The time constant of an LR circuit is [1]

- | | |
|---|-------|
| A | RC |
| B | L/R |
| C | LR |
| D | R/L |

3.2 At $t = 0$ in an LR circuit, an inductor behaves like [1]

- | | |
|---|----------------------|
| A | a plain wire |
| B | a break (no current) |
| C | a battery |
| D | a capacitor |

3.3 An LR circuit has $\varepsilon = 10$ V, $R = 5.0 \Omega$, and $L = 0.25$ H.

(a) Find the time constant. [2]

(b) Find the final (steady-state) current. [2]