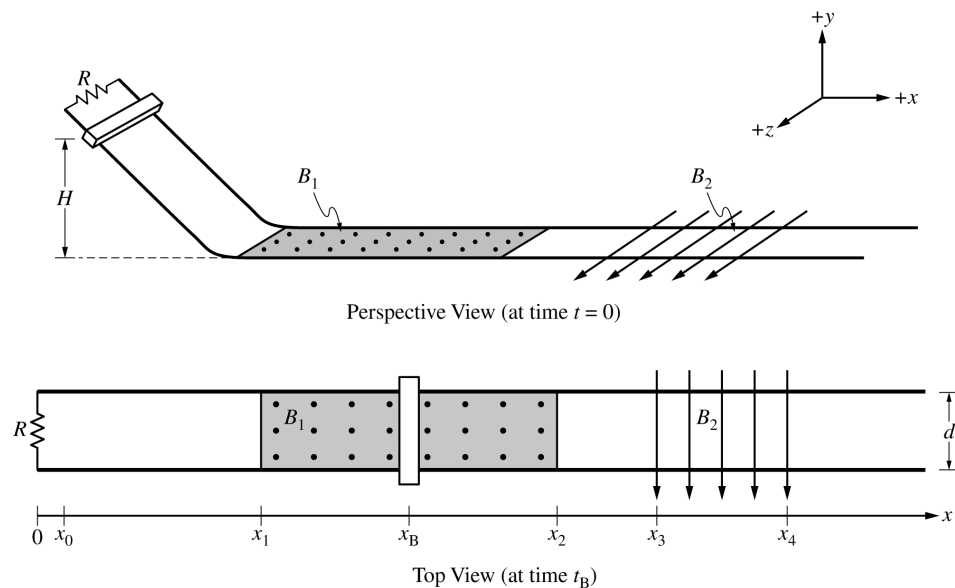




Two parallel conducting rails are separated by distance $d = 0.30$ m. A resistor of resistance $R = 0.20\ \Omega$ connects the rails. A conducting bar is placed on a sloped section of the rails at height H above the horizontal section of the rails. Frictional forces and the resistances of the bar and rails are negligible.

- At time $t = 0$, the bar is released from rest from position x_0 and slides down the sloped section of the rails, as shown in the Perspective View.
- At time t_1 , the bar reaches position x_1 and smoothly transitions to the horizontal section of the rails and enters a uniform magnetic field of magnitude $B_1 = 0.40$ T that is directed in the $+y$ -direction.
- At time t_2 , the bar reaches position x_2 and enters a region with no magnetic field.
- At time t_3 , the bar reaches position x_3 and enters a uniform magnetic field of magnitude $B_2 = 0.60$ T that is directed in the $+z$ -direction.
- At time t_4 , the bar reaches position x_4 and enters a region with no magnetic field.

The bar is at position x_B (shown in Top View) at time t_B such that $t_1 < t_B < t_2$.

GO ON TO THE NEXT PAGE.

- (a) On the following diagram of the bar, as observed from the Top View, draw an arrow indicating the direction of the net force F_{net} exerted on the bar at time t_B . If the net force is zero, write $F_{\text{net}} = 0$.




- (b) At time t_B , the speed of the bar is $v = 2.5$ m/s.

i. Calculate the magnitude of the current in the bar at time t_B .

ii. Calculate the magnitude of the net force F_{net} exerted on the bar at time t_B .

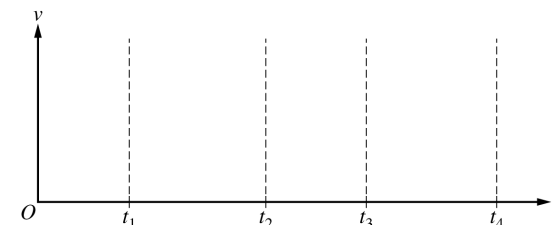- (c) On the following axes, sketch a graph of the speed v of the bar as a function of time t between $t = 0$ and t_4 .



GO ON TO THE NEXT PAGE.

- (d) The original scenario is repeated but with a new bar that has the same mass but with a nonnegligible resistance $R = 0.20 \, \Omega$. The new bar is released from rest and smoothly transitions to the horizontal section of the rails and enters the first uniform magnetic field.

i. Determine the total resistance of the closed circuit.

ii. In the original scenario, the magnitude of the acceleration of the bar immediately after the bar enters the first uniform magnetic field is a_{original} . In the new scenario, the magnitude of the acceleration of the bar immediately after the bar enters the first uniform magnetic field is a_{new} . Is a_{new} greater than, less than, or equal to a_{original} ? Justify your answer.

- (e) Describe a modification to H , B_1 , or d that will result in a larger induced current in the new bar immediately after the bar enters the first uniform magnetic field. Justify your answer.

GO ON TO THE NEXT PAGE.


PHYSICS C: ELECTRICITY AND MAGNETISM

SECTION II

Time—45 minutes

3 Questions

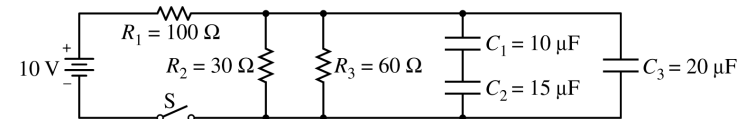Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.



1. The circuit shown above is composed of an ideal 10 V battery, three resistors and three capacitors with the values shown, and an open switch S. The capacitors are initially uncharged. Switch S is now closed.

(a) Calculate the current through R_1 immediately after switch S is closed.

Switch S has been closed for a long time, and the circuit has reached a steady state.

(b) Calculate the potential difference across R_1 .

(c)

i. Calculate the charge stored on the positive plate of capacitor C_2 .

ii. Is the charge stored on capacitor C_3 greater than, less than, or equal to the charge stored on capacitor C_2 ?

_____ Greater than _____ Less than _____ Equal to

Justify your answer.


GO ON TO THE NEXT PAGE.

Use a pencil or pen with black or dark blue ink only. Do NOT write your name. Do NOT write outside the box.

Write your responses to questions 1–3 on this page.

Switch S is then opened.

(d)

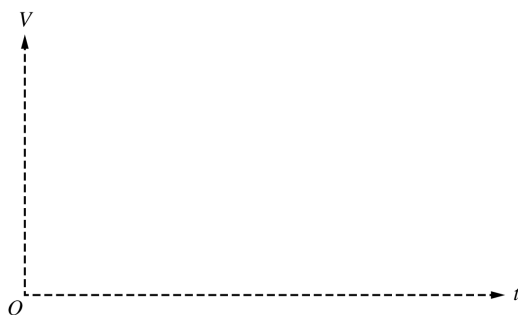
i. Determine the current through R_1 immediately after the switch is opened.ii. Calculate the current through R_2 immediately after the switch is opened.(e) On the axes below, sketch a graph of the potential difference V across capacitor C_2 as a function of time t if switch S is opened at time $t = 0$. Label the maximum value.Capacitor C_3 is replaced by two $10\ \mu\text{F}$ capacitors connected in series, switch S is closed, and the circuit reaches equilibrium. Switch S is then opened at time $t = 0$.(f) For $t > 0$, would the sketch of a graph of the new voltage across C_2 as a function of time be above, below, or the same as the sketch for part (e)?

_____ Above _____ Below _____ The same

Justify your answer.

GO ON TO THE NEXT PAGE.

Use a pencil or pen with black or dark blue ink only. Do NOT write your name. Do NOT write outside the box.

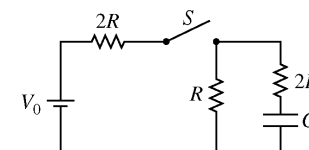PHYSICS C: ELECTRICITY AND MAGNETISM**SECTION II****Time—45 minutes****3 Questions****Directions:** Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.1. The circuit represented above is composed of three resistors with the resistances shown, a battery of voltage V_0 , a capacitor of capacitance C , and a switch S . The switch is closed, and after a long time, the circuit reaches steady-state conditions. Answer the following questions in terms of V_0 , R , C , and fundamental constants, as appropriate.

(a) Derive an expression for the steady-state current supplied by the battery.

(b) Derive an expression for the charge on the capacitor.

(c) Derive an expression for the energy stored in the capacitor.

Now the switch is opened at time $t = 0$.(d) Write, but do NOT solve, a differential equation that could be used to solve for the charge $q(t)$ on the capacitor as a function of the time t after the switch is opened.

(e)


- Calculate the current in resistor R immediately after the switch is opened.
- On the axes below, sketch the current in the circuit as a function of time from time $t = 0$ to a long time after the switch is opened. Explicitly label the maxima with numerical values or algebraic expressions, as appropriate.



- (f) Is the total amount of energy dissipated in the resistors after the switch is opened greater than, less than, or equal to the amount of energy stored in the capacitor calculated in part (c) ?

_____ Greater than _____ Less than _____ Equal to

Justify your answer.

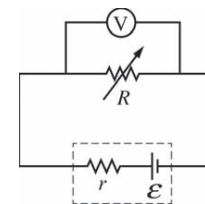

E&M.2.


A student performs an experiment to determine the emf $\mathcal{E}$ and internal resistance r of a given battery. The student connects the battery in series to a variable resistance R , with a voltmeter across the variable resistor, as shown in the figure above, and measures the voltmeter reading V as a function of the resistance R . The data are shown in the table below.

Trial #	Resistance (Ω)	Voltage (V)	$1/R$ ($1/\Omega$)	$1/V$ ($1/V$)
1	0.50	5.6	2.00	0.179
2	1.0	7.4	1.00	0.135
3	2.0	9.4	0.50	0.106
4	3.0	10.6	0.33	0.094
5	5.0	10.9	0.20	0.092
6	10	11.4	0.10	0.088

(a)

- Derive an expression for the measured voltage V . Express your answer in terms of R , $\mathcal{E}$, r , and physical constants, as appropriate.
- Rewrite your expression from part (a)-i to express $1/V$ as a function of $1/R$.

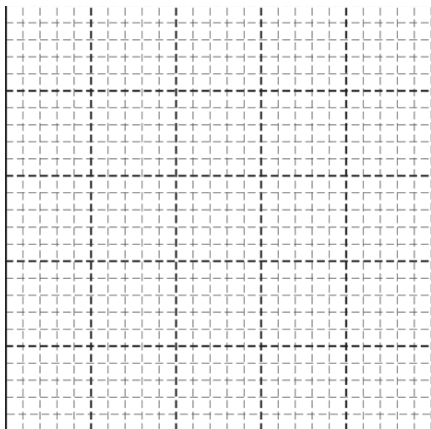- (b) On the grid below, plot data points for the graph of $1/V$ as a function of $1/R$. Clearly scale and label all axes, including units as appropriate. Draw a straight line that best represents the data.



- (c) Use the straight line from part (b) to obtain values for the following.

- i. $\mathcal{E}$
- ii. r

- (d) Using the results of the experiment, calculate the maximum current that the battery can provide.

- (e) A voltmeter is to be used to determine the emf of the battery after removing the battery from the circuit. Two voltmeters are available to take this measurement—one with low internal resistance and one with high internal resistance. Indicate which voltmeter will provide the most accurate measurement.

- ____ The voltmeter with low resistance will provide the most accurate measurement.
 ____ The voltmeter with high resistance will provide the most accurate measurement.
 ____ The two voltmeters will provide equal accuracy.

Justify your answer.


PHYSICS C: ELECTRICITY AND MAGNETISM

SECTION II

Time—45 minutes

3 Questions

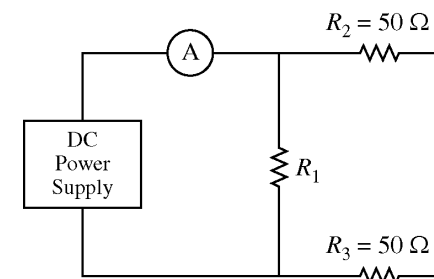Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.




E&M. 1.

Physics students are analyzing the circuit above. A variable DC power supply is connected to an ammeter and three resistors. The resistances of two of the resistors are known to be $R_2 = R_3 = 50 \, \Omega$, but the resistance of the third resistor is unknown. The students collect data on the potential difference across the power supply and the current measured by the ammeter, as follows.

Potential Difference (V)	2	4	6	8	10
Current (mA)	40	55	97	138	155

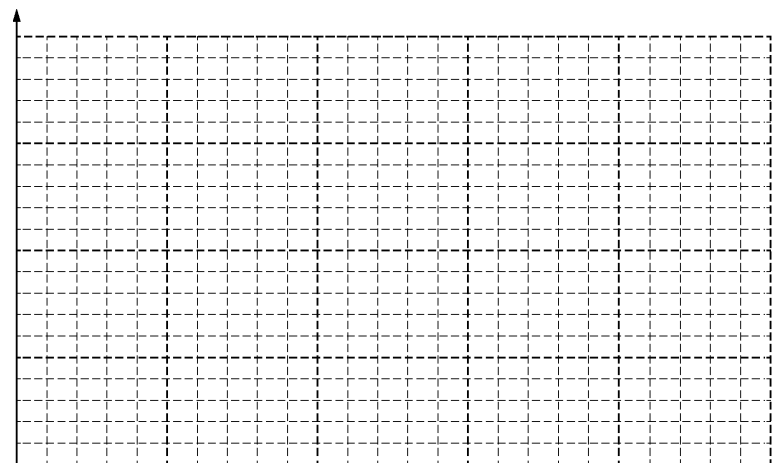- (a) On the grid below, plot the data points for the current as a function of the potential difference. Clearly scale and label all axes, including units if appropriate. Draw a straight line that best represents the data.




(b) Using the straight line from part (a), calculate the total resistance of the three-resistor combination.

(c) Calculate the value of R_1 .

The power supply is now fixed at 12 V.

(d) Calculate the current through R_2 .

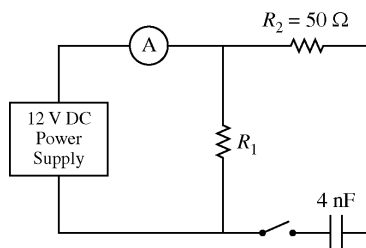(e) Resistor 3 is now removed and replaced by an open switch in series with an uncharged 4 nF capacitor, as shown below. The power supply is still fixed at 12 V.



i. Calculate the current in R_2 immediately after the switch is closed.

ii. A long time after the switch is closed, will the magnitude of the current in R_2 be greater than, less than, or equal to the current through R_2 found in part (d) ?

___ Greater than ___ Less than ___ Equal to

Justify your answer.

(f) The 4 nF capacitor is replaced with an uncharged 10 nF capacitor. Will the magnitude of the current in R_2 immediately after the switch is closed be greater than, less than, or equal to the current in part (e)i?

___ Greater than ___ Less than ___ Equal to

Justify your answer.