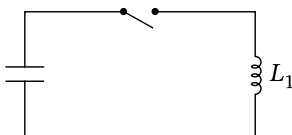


**Question 3**

The following information applies to parts A and B.

3. In Experiment 1, students are asked to collect data that can be graphed to determine the inductance  $L_1$  of an inductor. The students have access to multiple charged capacitors, each of a different known capacitance, and a voltmeter that measures potential difference as a function of time. In each trial, the inductor is connected to a charged capacitor and an initially open switch, as shown in Figure 1.

Figure 1

**Part A**

- Indicate** quantities that could be measured by the students that would allow them to determine  $L_1$  using a linear graph.
- Briefly **describe** a method to reduce experimental uncertainty.


**Part B**

- Indicate** what quantities the students could graph on the horizontal and vertical axes to create a linear graph that can be used to determine  $L_1$ .
- Briefly **describe** the relationship between  $L_1$  and a feature of the graph from part B (i). Your answer may include an equation that relates  $L_1$  and the chosen feature of the graph.

The following information applies to parts C and D.

In Experiment 2, the students are asked to use a graph to determine the inductance  $L_2$  of a new inductor. The inductor is connected to a 12 V battery, a  $10\ \Omega$  resistor, and an initially open switch, as shown in Figure 2.

Figure 2

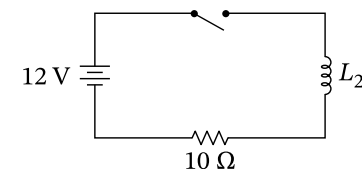

After the switch is closed, the current  $I$  in the circuit is measured at different times and the corresponding rate of change of the current,  $\frac{dI}{dt}$ , is determined. The collected data are shown in Table 1.

Table 1


| $I$ (A) | $\frac{dI}{dt}$ (A/s) |
|---------|-----------------------|
| 0.40    | 280                   |
| 0.50    | 230                   |
| 0.75    | 150                   |
| 0.90    | 100                   |
| 1.00    | 68                    |

**Part C**

- i. **Label** the axes of the grid provided with measured or calculated quantities. Include units, as appropriate. The graphed quantities should yield a linear graph that can be used to determine  $L_2$ .
- ii. On the grid provided, create a graph of the quantities indicated in part C (i).
- Clearly **label** each axis with a numerical scale.
  - Plot** the corresponding data points on the grid.
  - Table 2 is provided in your booklet for scratch work and will not be scored.

Quantity (units, if appropriate)

\_\_\_\_\_

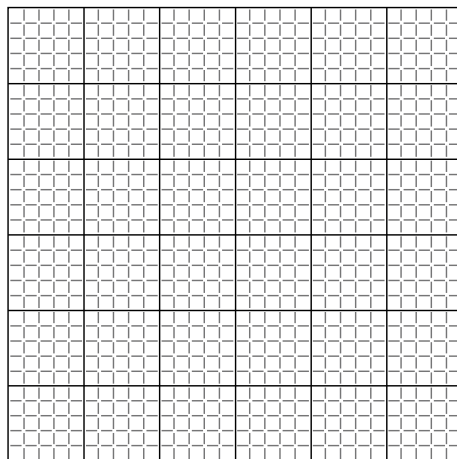

Quantity (units, if appropriate)

\_\_\_\_\_

- iii. **Draw** a best-fit line for the data plotted in part C (ii).

**Part D**

Using the best-fit line that you drew in part C (iii), **calculate** an experimental value for  $L_2$ .

Begin your response to **QUESTION 2** on this page.

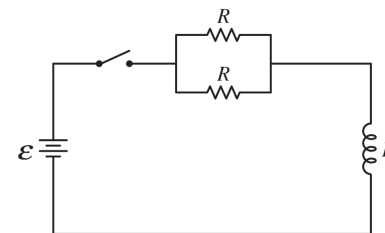


Figure 1

2. Students are asked to determine the resistance  $R$  of two identical resistors. The resistors are in parallel with each other and are connected in series to a battery of known emf  $\mathcal{E}$ , an inductor of known inductance  $L$ , and a switch, as shown in Figure 1. The students have access to a voltmeter that can measure potential difference as a function of time. The students are required to measure a quantity that decreases with time to determine  $R$ .

(a)

- i. On the circuit diagram shown in Figure 1, **draw** the voltmeter, using the following symbol, with connections that would allow the students to correctly measure a potential difference that decreases with time.



Voltmeter Symbol

- ii. **Describe** a procedure for collecting data that would allow the students to graphically determine the experimental value for  $R$  using the measured quantity that decreases with time. Provide enough detail so that another student could replicate the experiment.

**GO ON TO THE NEXT PAGE.**

Continue your response to **QUESTION 2** on this page.

(b)

i. On the axes shown in Figure 2, produce a graph that represents the expected trend of the data by completing the following tasks.

- **Label** the quantities graphed on the vertical and horizontal axes.
- **Sketch** a line or curve that represents the expected trend of the collected data.
- **Label** any appropriate intercepts and/or asymptotes in terms of the quantities provided.



Figure 2

ii. **Describe** how the information from the graph in part (b)(i) would be used to determine the experimental value for  $R$ .

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 2** on this page.

(c) Starting with an appropriate application of Kirchhoff's loop rule, **derive**, but do NOT solve, a differential equation that can be used to determine the current  $I$  in the inductor at time  $t$  after the switch is closed. Express your answer in terms of  $R$ ,  $\mathcal{E}$ ,  $L$ ,  $t$ , and physical constants, as appropriate.

After reaching steady state, the absolute value of the potential difference across the inductor is  $|\Delta V_1|$ . The students replace the original inductor with a new inductor that has nonnegligible resistance. The experiment is repeated. After a long time, the absolute value of the potential difference across the new inductor is  $|\Delta V_2|$ .

(d) **Indicate** whether  $|\Delta V_2|$  is greater than, less than, or equal to  $|\Delta V_1|$ .

\_\_\_\_\_  $|\Delta V_2| > |\Delta V_1|$       \_\_\_\_\_  $|\Delta V_2| < |\Delta V_1|$       \_\_\_\_\_  $|\Delta V_2| = |\Delta V_1|$

**Justify** your answer.

GO ON TO THE NEXT PAGE.


Begin your response to **QUESTION 2** on this page.

Figure 1

2. Students are asked to determine the resistance  $R$  of identical resistors  $R_A$  and  $R_B$ . The resistors are connected in series with each other, a battery of known emf  $\mathcal{E}$ , an inductor of known inductance  $L$ , and a switch, as shown in Figure 1. The students have access to a voltmeter that can measure potential difference as a function of time. The students are required to measure a quantity that increases with time to determine  $R$ .

(a)

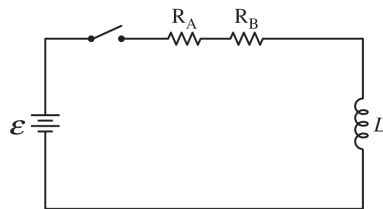- i. On the circuit diagram shown in Figure 1, **draw** the voltmeter, using the following symbol, with connections that would allow the students to correctly measure a potential difference that increases with time.



Voltmeter Symbol

- ii. **Describe** a procedure for collecting data that would allow the students to graphically determine the experimental value for  $R$  using a measured quantity that increases with time. Provide enough detail so that another student could replicate the experiment.

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 2** on this page.

(b)

- i. On the axes shown in Figure 2, produce a graph that represents the expected trend of the data by completing the following tasks.

- **Label** the quantities graphed on the vertical and horizontal axes.
- **Sketch** a line or curve that represents the expected trend of the collected data.
- **Label** any appropriate intercepts and/or asymptotes in terms of the quantities provided.

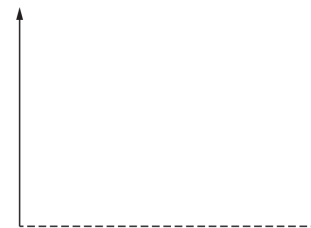


Figure 2

- ii. **Describe** how the information from the graph in part (b)(i) would be used to determine the experimental value for  $R$ .

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 2** on this page.

- (c) Starting with an appropriate application of Kirchhoff's loop rule, **derive**, but do NOT solve, a differential equation that can be used to determine the current  $I$  in the inductor at time  $t$  after the switch is closed. Express your answer in terms of  $R$ ,  $\mathcal{E}$ ,  $L$ ,  $t$ , and physical constants, as appropriate.

After reaching steady state, the absolute value of the potential difference across  $R_A$  is  $|\Delta V_1|$ . The students replace the original inductor with a new inductor that has nonnegligible resistance. The experiment is repeated. After a long time, the absolute value of the potential difference across  $R_A$  is  $|\Delta V_2|$ .

- (d) **Indicate** whether  $|\Delta V_2|$  is greater than, less than, or equal to  $|\Delta V_1|$ .

\_\_\_\_\_  $|\Delta V_2| > |\Delta V_1|$     \_\_\_\_\_  $|\Delta V_2| < |\Delta V_1|$     \_\_\_\_\_  $|\Delta V_2| = |\Delta V_1|$

**Justify** your answer.

GO ON TO THE NEXT PAGE.

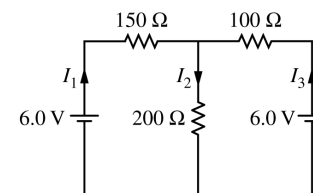


Figure 1

2. The circuit shown above is constructed with two 6.0 V batteries and three resistors with the values shown. The currents  $I_1$ ,  $I_2$ , and  $I_3$  in each branch of the circuit are indicated.

(a)

- Using Kirchhoff's rules, write, but DO NOT SOLVE, equations that can be used to solve for the current in each resistor.
- Calculate the current in the  $200\ \Omega$  resistor.
- Calculate the power dissipated by the  $200\ \Omega$  resistor.

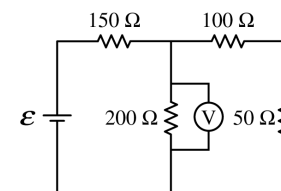



Figure 2

The two 6.0 V batteries are replaced with a battery with voltage  $\mathcal{E}$  and a resistor of resistance  $50\ \Omega$ , as shown above. The voltmeter V shows that the voltage across the  $200\ \Omega$  resistor is 4.4 V.


- Calculate the current through the  $50\ \Omega$  resistor.
- Calculate the voltage  $\mathcal{E}$  of the battery.

(d)

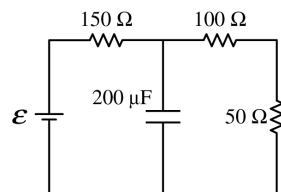- i. The  $200\ \Omega$  resistor in the circuit in Figure 2 is replaced with a  $200\ \mu\text{F}$  capacitor, as shown on the right, and the circuit is allowed to reach steady state. Calculate the current through the  $50\ \Omega$  resistor.



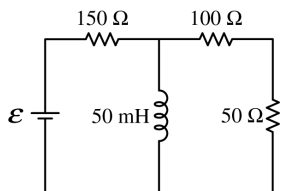- ii. The  $200\ \Omega$  resistor in the circuit in Figure 2 is replaced with an ideal  $50\ \text{mH}$  inductor, as shown on the right, and the circuit is allowed to reach steady state. Is the current in the  $50\ \Omega$  resistor greater than, less than, or equal to the current calculated in part (b) ?



\_\_\_\_ Greater than    \_\_\_\_ Less than    \_\_\_\_ Equal to

Justify your answer.