

Question 2: Version J

2. A rotating, circular, conducting loop of area A and resistance R is in an external uniform magnetic field of magnitude B that is directed in the $-z$ -direction. At time $t = 0$, the magnetic field is perpendicular to the plane of the loop, as shown in Figure 1. The loop is rotating with constant angular speed ω and period T about the dashed line that is along the diameter of the loop. The value of the magnetic flux through the loop as a function of time t is $\Phi = BA \cos(\omega t)$.

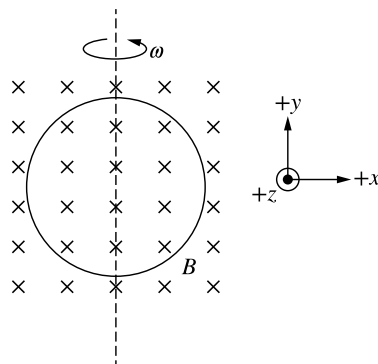


Figure 1

- A. The absolute value of the induced emf in the loop is $|\mathcal{E}|$. The partially completed bar chart in Figure 2 shows a bar that represents $|\mathcal{E}|$ at $t = \frac{3}{4}T$. In Figure 2, **draw** bars to represent $|\mathcal{E}|$ at times $t = 0$, $\frac{1}{4}T$, and $\frac{1}{2}T$ relative to $|\mathcal{E}|$ shown at $\frac{3}{4}T$. If $|\mathcal{E}| = 0$, **write** a “0” in that column.

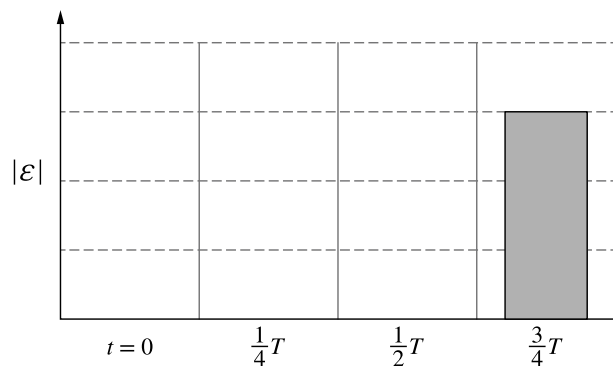


Figure 2

- B. **Derive** an expression for the maximum induced current in the loop in terms of A , R , B , ω , and physical constants, as appropriate. Begin your derivation by writing a fundamental physics principle or an equation from the reference information.
- C. On the axes shown in Figure 3, **sketch** a graph of the instantaneous power P dissipated by the loop as a function of t during the time interval $0 \leq t \leq T$.

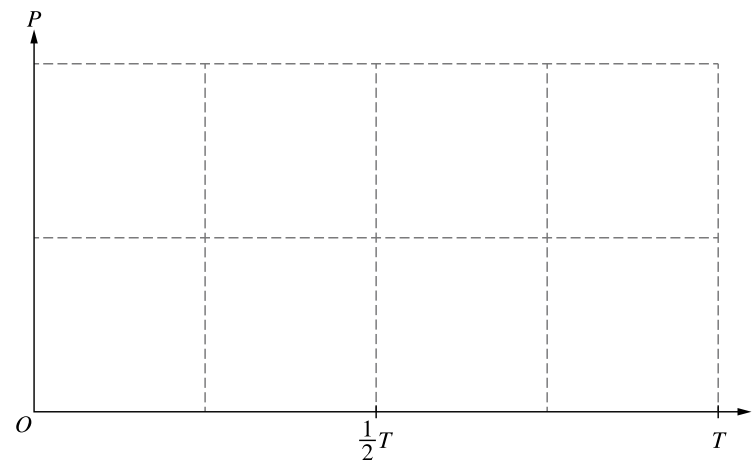


Figure 3

- D. **Indicate** whether the sketch you drew in part C is or is not consistent with the bars that you drew in part A. Briefly **justify** your answer by referencing the functional dependence between P and $|\mathcal{E}|$.


Begin your response to **QUESTION 2** on this page.

Figure 1

2. Students are asked to determine the resistance R of two identical resistors. The resistors are in parallel with each other and are connected in series to a battery of known emf $\mathcal{E}$, an inductor of known inductance L , and a switch, as shown in Figure 1. The students have access to a voltmeter that can measure potential difference as a function of time. The students are required to measure a quantity that decreases with time to determine R .

(a)

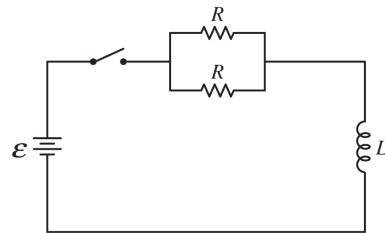- i. On the circuit diagram shown in Figure 1, **draw** the voltmeter, using the following symbol, with connections that would allow the students to correctly measure a potential difference that decreases with time.



Voltmeter Symbol

- ii. **Describe** a procedure for collecting data that would allow the students to graphically determine the experimental value for R using the measured quantity that decreases with time. Provide enough detail so that another student could replicate the experiment.

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 2** on this page.

(b)

- i. On the axes shown in Figure 2, produce a graph that represents the expected trend of the data by completing the following tasks.

- **Label** the quantities graphed on the vertical and horizontal axes.
- **Sketch** a line or curve that represents the expected trend of the collected data.
- **Label** any appropriate intercepts and/or asymptotes in terms of the quantities provided.



Figure 2

- ii. **Describe** how the information from the graph in part (b)(i) would be used to determine the experimental value for R .

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 2** on this page.

- (c) Starting with an appropriate application of Kirchhoff's loop rule, **derive**, but do NOT solve, a differential equation that can be used to determine the current I in the inductor at time t after the switch is closed. Express your answer in terms of R , $\mathcal{E}$, L , t , and physical constants, as appropriate.


After reaching steady state, the absolute value of the potential difference across the inductor is $|\Delta V_1|$. The students replace the original inductor with a new inductor that has nonnegligible resistance. The experiment is repeated. After a long time, the absolute value of the potential difference across the new inductor is $|\Delta V_2|$.

- (d) **Indicate** whether $|\Delta V_2|$ is greater than, less than, or equal to $|\Delta V_1|$.

_____ $|\Delta V_2| > |\Delta V_1|$ _____ $|\Delta V_2| < |\Delta V_1|$ _____ $|\Delta V_2| = |\Delta V_1|$

Justify your answer.

GO ON TO THE NEXT PAGE.

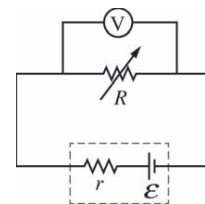

E&M.2.


A student performs an experiment to determine the emf $\mathcal{E}$ and internal resistance r of a given battery. The student connects the battery in series to a variable resistance R , with a voltmeter across the variable resistor, as shown in the figure above, and measures the voltmeter reading V as a function of the resistance R . The data are shown in the table below.

Trial #	Resistance (Ω)	Voltage (V)	$1/R$ ($1/\Omega$)	$1/V$ ($1/V$)
1	0.50	5.6	2.00	0.179
2	1.0	7.4	1.00	0.135
3	2.0	9.4	0.50	0.106
4	3.0	10.6	0.33	0.094
5	5.0	10.9	0.20	0.092
6	10	11.4	0.10	0.088

(a)

- Derive an expression for the measured voltage V . Express your answer in terms of R , $\mathcal{E}$, r , and physical constants, as appropriate.
- Rewrite your expression from part (a)-i to express $1/V$ as a function of $1/R$.

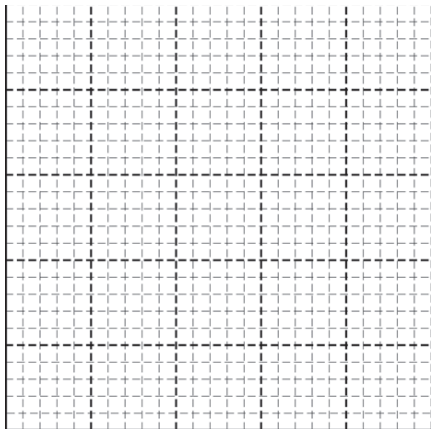- (b) On the grid below, plot data points for the graph of $1/V$ as a function of $1/R$. Clearly scale and label all axes, including units as appropriate. Draw a straight line that best represents the data.



- (c) Use the straight line from part (b) to obtain values for the following.
- $\mathcal{E}$
 - r
- (d) Using the results of the experiment, calculate the maximum current that the battery can provide.
- (e) A voltmeter is to be used to determine the emf of the battery after removing the battery from the circuit. Two voltmeters are available to take this measurement—one with low internal resistance and one with high internal resistance. Indicate which voltmeter will provide the most accurate measurement.
- ____ The voltmeter with low resistance will provide the most accurate measurement.
- ____ The voltmeter with high resistance will provide the most accurate measurement.
- ____ The two voltmeters will provide equal accuracy.

Justify your answer.