

Week 29

IGCSE Computer Science

Homework bundle for this week

本周作业合集

exercises.lol

Contents 目录

Topic 10 quiz 2

10. Boolean logic

Starter Quiz · 课前小测

IGCSE Computer Science

Name: _____ Score: _____

1. An AND gate gives output 1 when:
 - ☐ both inputs are 1
 - ☐ at least one input is 1
 - ☐ the inputs are different
 - ☐ both inputs are 0
2. The expression '(A AND B) OR (NOT C)' means:
 - ☐ do A AND B, do NOT C, then OR the two results
 - ☐ do A OR B only
 - ☐ invert A, B and C
 - ☐ A AND B AND C
3. An OR gate gives output 0 only when:
 - ☐ both inputs are 0
 - ☐ both inputs are 1
 - ☐ the inputs are different
 - ☐ one input is 1
4. How many rows does a truth table have for a circuit with 3 inputs?

5. A XOR gate gives output 1 when:
 - ☐ the two inputs are different
 - ☐ both inputs are 1
 - ☐ both inputs are 0
 - ☐ always
6. When drawing a circuit from a problem statement, you should:
 - ☐ draw it exactly as the statement says, without simplifying
 - ☐ always reduce it to one gate
 - ☐ add extra gates
 - ☐ ignore the NOT operations

7. A NOR gate with both inputs 0 gives what output (0 or 1)?

- ☐ 1
- ☐ 0
- ☐ cannot tell
- ☐ 2

10. Boolean logic

Answers · 答案

IGCSE Computer Science

1. both inputs are 1

AND outputs 1 only when every input is 1.

2. do A AND B, do NOT C, then OR the two results

Work out each part — (A AND B) and (NOT C) — then OR them together.

3. both inputs are 0

OR is 1 if at least one input is 1, so it is 0 only when both are 0.

4. 8

Each input doubles the combinations: $2^3 = 8$ rows (000 to 111).

5. the two inputs are different

XOR (exclusive OR) is 1 when the inputs differ.

6. draw it exactly as the statement says, without simplifying

At IGCSE you draw the circuit as described — simplification is not required.

7. 1

NOR = NOT OR. OR of (0,0) is 0, so NOR is 1. NOR is 1 only when both inputs are 0.

8. 1

A AND B = 0; 0 OR C(=1) = 1, so X = 1.