

4.3 Electric circuits

Name: _____ Class: _____ Date: _____

Total: 12 marks

KEY WORDS series and parallel 串联与并联 • electric circuits 电路 • potential divider 分压器
 • parallel 并联 • series 串联

Objective



Build the skills to answer exam questions on **electric circuits** 电路 — **series and parallel** 串联与并联 rules, combining resistors, and **potential dividers** 分压器.

You must be able to:


- use the current/p.d. rules for series and parallel circuits
- add series resistors and combine two parallel resistors
- use the potential-divider idea ($\frac{R_1}{R_2} = \frac{V_1}{V_2}$)

1 Worked examples

■ Combining resistors

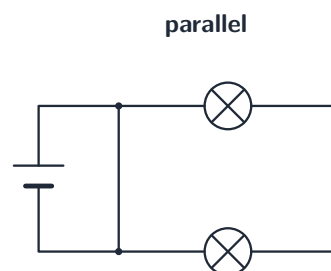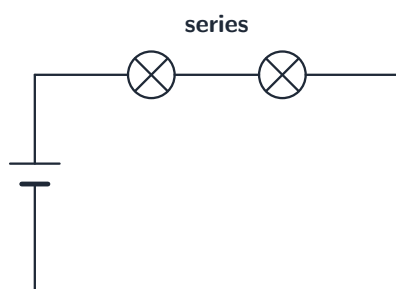

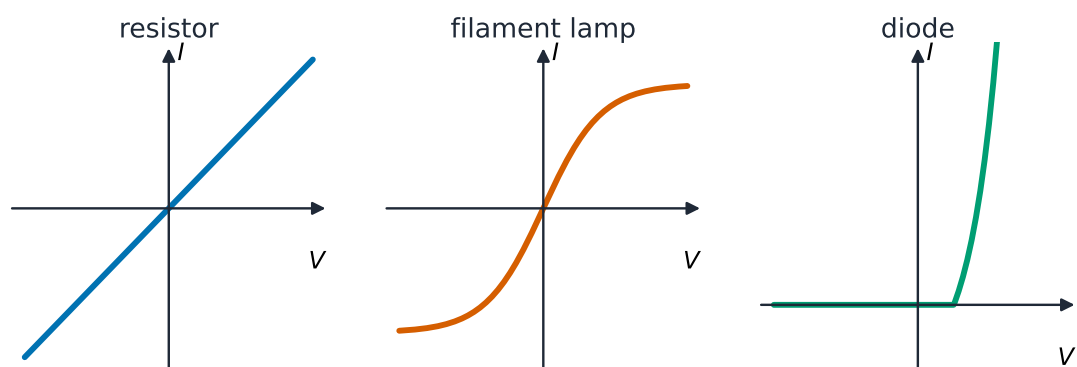Series: same current, shared p.d., $R_{total} = R_1 + R_2$. Parallel: same p.d., split current, smaller total R



resistor (ohmic): $V = IR$ straight · filament: resistance rises with heat · diode: one-way

A resistor gives a straight I–V line; a filament lamp curves as it heats

6 Ω and 3 Ω in parallel: $\frac{1}{R} = \frac{1}{6} + \frac{1}{3} = \frac{1}{2} \Rightarrow R = 2 \Omega$.

2 Practice

2.1 Two resistors of 4 Ω and 6 Ω are in series. Find the total resistance. [1]

2.2 State how the current behaves at every point in a series circuit. [1]

3 Exam-style questions

3.1 Compared with the smallest single resistor, two resistors in parallel give a total resistance that is: [1]

A	B
C	D

- A** larger
- B** smaller
- C** the same
- D** zero

3.2 A 12 V supply is connected to a $4\ \Omega$ and an $8\ \Omega$ resistor in series.

(a) Find the total resistance and the current. [3]

(b) Find the p.d. across the $8\ \Omega$ resistor. [2]

3.3 A $6\ \Omega$ and a $12\ \Omega$ resistor are connected in parallel across a 6 V supply. Find the total resistance and the total current from the supply. [4]
