

## 5.2 Rectifiers and dc supplies

Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

Total: 22 marks

**KEY WORDS** half-wave rectifier

• bridge rectifier

• filter capacitor

• ripple

• zener diode

### Objective

Analyse half- and full-wave rectifiers with capacitor filters, size a filter for a ripple specification, and check zener regulation against its current window and power limit.


### 1 Key knowledge and worked examples

#### ■ The rectifier family

A **half-wave rectifier**  
**wave bridge rectifier**

conducts one half-cycle (one diode drop). A **full-wave bridge rectifier** conducts both half-cycles through two diodes at a time (1.4 V total). Peak output =  $V_{peak} - \text{diodedrops}$ .

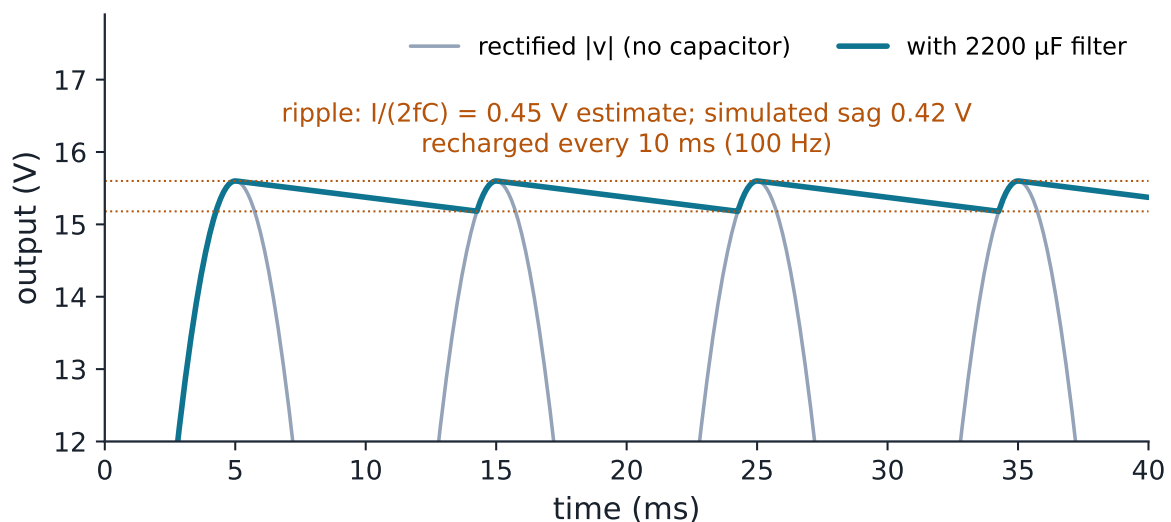**Worked example.** A 12 V RMS secondary at 50 Hz into a bridge: peak  $12\sqrt{2} = 17.0\text{V}$ , output peak  $17.0 - 1.4 = 15.6\text{ V}$ .



*Full-wave bridge with 2200  $\mu\text{F}$  at 100 mA: the capacitor bridges the gaps.*

### ■ The filter capacitor and ripple

A **filter capacitor** holds the output between recharge peaks. The **ripple**  $\Delta V \approx I/(f_r C)$  where  $f_r$  is the recharge rate (f for half-wave, 2f for full-wave).

**Worked example.** 100 mA load, 2200  $\mu\text{F}$ , bridge (recharges every 10 ms):  $\Delta V = 0.1/(100 \times 2200 \mu) = 0.45\text{V}$ . The output sits between 15.6 V (peak) and 15.1 V. Design rule: choose C from the spec –  $C \geq I/(f_r \cdot \Delta V)$ ; e.g. requiring 0.2 V at 150 mA needs  $C \geq 0.15/(100 \times 0.2) = 7500 \mu\text{F}$ .

### ■ Zener regulation, by the window

A **zener** regulator holds  $V_Z$  while  $I_Z$  stays within its window: above  $I_Z(\text{min})$  (regulation) and below  $P_Z(\text{max})/V_Z$  (survival). The check is two inequalities at the extreme loads – and the series resistor dissipates  $(V_{in} - V_Z) \times I_R$ , which is part of the design too.

## 2 Practice

**2.1** A half-wave rectifier on a 6 V RMS, 50 Hz secondary (one diode): compute the peak output voltage. [2]

**2.2** A bridge with 1000  $\mu\text{F}$  supplying 50 mA from a 50 Hz supply: compute the ripple and the recharge interval. [3]

**2.3** A 9 V zener regulator ( $R = 220 \Omega$  from 12 V) feeds a variable load. Give  $I_R$  and the zener current at open circuit. [3]

### 3 Exam-style questions

---

**3.1** Design a bridge supply: 15 V regulated output from a zener, load 0–120 mA, input 24 V DC, ripple at the filter  $\leq 1$  V.

Choose the series R for the zener path (zener needs  $\geq 5$  mA at full load), size the filter capacitor (from a 100 Hz recharge), and check the zener and resistor power at worst case. State which load case is worst for each component. [8]

---

---

---

---

---

---

---

---

---

---

**3.2** A half-wave supply must deliver 20 mA DC with ripple  $\leq 0.5$  V from a 9 V RMS, 50 Hz secondary (one diode, constant-drop), capacitor filter.

Compute the peak output, the required capacitance, and the diode's average current. Then explain (with the numbers) why the same capacitor on a bridge halves the ripple, and give the peak diode current rationale (the capacitor recharges in a brief slug near the peak). [6]

---

---

---

---

---

---

---

---

## Solutions

---

### 2.1

- Peak secondary:  $6\sqrt{2} = 8.49V$ ; minus 0.7: 7.79 V.

### 2.2

- $\Delta V = I/(2f \cdot C) = 0.05/(100 \times 1000\mu) = 0.5V$ .
- Recharge interval: 10 ms (every half-cycle).

### 2.3

- $I_R = (12 - 9)/220 = 13.6mA$ .
- Open circuit (no load current):  $I_Z = 13.6mA$  – all of it.

### 3.1

- Filter R sees the zener input node; design the zener chain from the DC side first: full load needs  $I_R(max) = 120 + 5 = 125mA$ .
- $R = (24 - 15)/0.125 = 72\Omega$  (use 68  $\Omega$  standard  $\rightarrow I_R = 9/68 = 132mA$ ).
- Zener current at full load:  $132 - 120 = 12 \text{ mA} \geq 5 \checkmark$ .
- Capacitor from the ripple spec at recharge 100 Hz:  $C \geq I/(f_r \Delta V) = 0.132/(100 \times 1) = 1320 \text{ }\mu F$  (use 1500  $\mu F$ ).
- Worst zener case = OPEN load:  $I_Z = 132mA$ ,  $P_Z = 15 \times 0.132 = 1.98W$  – needs a  $\geq 2 \text{ W}$  zener.
- Worst resistor case = same open load (max current both paths):  $P_R = 9 \times 0.132 = 1.19W$  – a 2 W resistor.

### 3.2

- Peak output:  $9\sqrt{2} - 0.7 = 12.0V$ .
- Capacitance:  $C \geq I/(f\Delta V) = 0.02/(50 \times 0.5) = 800\mu F$  (half-wave:  $f = 50 \text{ Hz}$ ).
- Diode average current = load DC = 20 mA (charge in = charge out).
- On a bridge the recharge is 100 Hz:  $\Delta V = I/(2fC) = 0.02/(100 \times 800\mu) = 0.25 \text{ V}$  – exactly half, because the capacitor waits only 10 ms instead of 20 ms.
- Peak diode current: the capacitor recharges only near the AC peak, replacing in  $\sim 1 \text{ ms}$  what the load took for a whole period – so the diode's peak current is several times its average (the reason diodes have a surge rating).