

## 4.4 Resonance

Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

Total: 22 marks

KEY WORDS resonance • bandwidth • Q factor

### Objective

Compute resonant frequency, bandwidth and Q for series and parallel RLC circuits; explain the impedance minimum/maximum; and verify resonant voltage/current magnifications numerically.


### 1 Key knowledge and worked examples

#### ■ Resonance: the imaginary parts cancel

A series RLC is at **resonance** when  $\omega_0 L = 1/(\omega_0 C)$ :

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad BW = \frac{R}{L} = \frac{\omega_0}{Q}, \quad Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$$

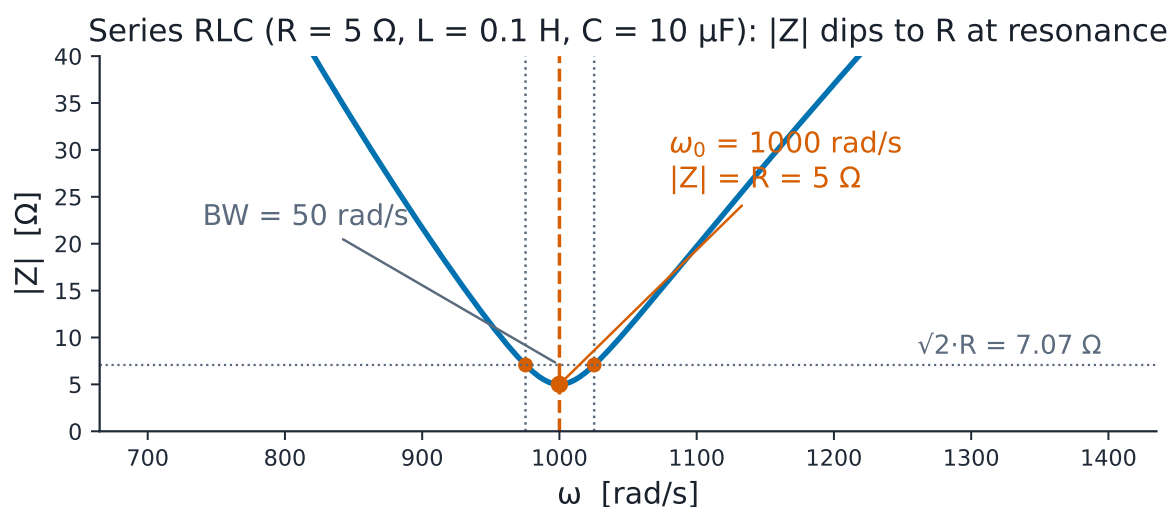At  $\omega_0$ :  $Z = R$  (purely resistive, minimum magnitude)  $\rightarrow$  maximum current; the **bandwidth** BW is the span between the half-power frequencies. In the PARALLEL RLC the dual holds: impedance is MAXIMUM at resonance.



*$|Z|$  dips to  $R$  at  $\omega_0$ ; the half-power band is marked.*

### ■ Worked example: voltage magnification

$R = 5\Omega$ ,  $L = 0.1H$ ,  $C = 10\mu F$ :  $\omega_0 = 1/\sqrt{10^{-6} \times 0.1} = 1000\text{rad/s}$ ,  $Q = 1000 \times 0.1/5 = 20$ .

At resonance with a 10 V source:  $I = 10/5 = 2A$ ;  $V_L = \omega_0 LI = 200V$  and  $V_C = I/(\omega_0 C) = 200V$  – twenty times the source,  $180^\circ$  apart, cancelling each other while each alone is huge. That is what Q means, measured in volts.

### ■ Selectivity and the frequency sweep

A frequency sweep past resonance shows the current peaking at  $\omega_0$  and falling on both sides at  $\pm BW/2$  to  $1/\sqrt{2}$  of peak. High Q = narrow peak = a selective tuner; the radio tuning dial IS this arithmetic – a station spacing of ~200 kHz at ~100 MHz needs  $Q \approx 500$ , and  $Q = \omega_0 L/R$  tells you how small R must be.

## 2 Practice

**2.1**  $L = 0.2H$ ,  $C = 20\mu F$ : compute  $\omega_0$  in rad/s and Hz. [2]

---

**2.2** A series RLC has  $R = 10\Omega$ ,  $\omega_0 = 500\text{rad/s}$ ,  $Q = 25$ . Compute L, C and the bandwidth. [3]

---

---

**2.3** At resonance the series circuit of 2.2 is driven by 5 V. Compute the current,  $V_L$  and  $V_C$ . [3]

---

---

### 3 Exam-style questions

---

**3.1** A series RLC has  $R = 2\Omega$ ,  $L = 0.05H$ ,  $C = 0.8\mu F$ .

Compute  $\omega_0$ ,  $Q$ , the bandwidth, and the half-power frequencies. With a 15 V source at resonance, compute the current and the capacitor voltage, and verify the magnification factor equals  $Q$ . Then state (with the reason) what happens to the bandwidth if  $R$  doubles with  $L$ ,  $C$  unchanged. [7]

---

---

---

---

---

---

---

---

**3.2** A parallel RLC ( $R = 40k\Omega$  in parallel with  $L = 0.4mH$  and  $C = 100nF$ ) is driven by a 2 mA source.

Compute  $\omega_0$  and the impedance at resonance; compute the  $Q$  for the parallel circuit ( $Q = R/(\omega_0 L)$ ) and the voltage across the tank at resonance. Verify that the tank current magnitudes in  $L$  and  $C$  each equal  $Q \times$  source current, and explain why the line current is only 2 mA while the branch currents are much larger. [7]

---

---

---

---

---

---

---

---