2.3 Linear algebra essentials

Name: _____ Class: _____ Date: _____ **Total: 23 marks**

KEY WORDS linear system • matrix inverse • determinant • singular

Objective

Solve 2×2 and 3×3 linear systems by elimination, invert a 2×2 matrix, detect singularity from the determinant, and verify every solution by substitution into the unused equations.

1 Key knowledge and worked examples

■ Elimination, and what the determinant says

A **linear system** `Ax = b` is solved by elimination: use one equation to remove a variable from another. The **determinant** of a 2×2 matrix,

$$\det \begin{pmatrix} a & b \\ c & d \end{pmatrix} = ad - bc,$$

is non-zero exactly when the rows are independent – a **singular** system (det = 0) has no unique solution: in circuits, a floating node or a loop of dependent sources.

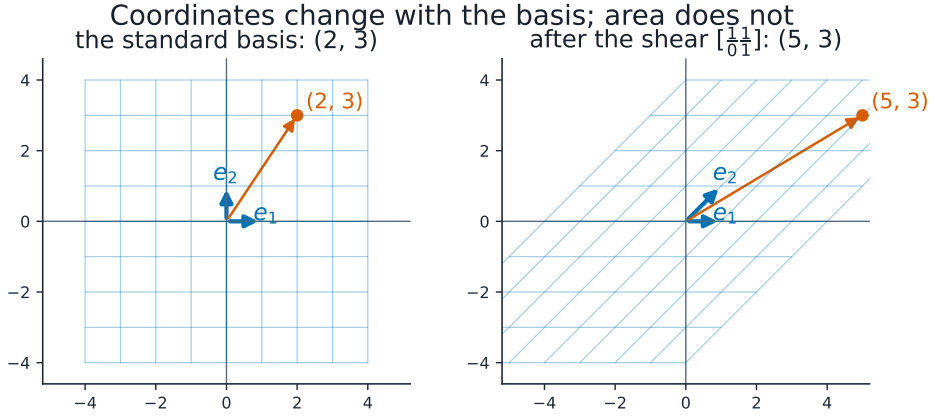

■ Worked example: two routes, each the other's check

Solve $x + 2y = 8$, $3x + y = 9$.

- Elimination: row2 − 3 · row1 → $-5y = -15$, so $y = 3$, back-substitute $x = 2$.
- Inverse: $det = 1{\cdot}1 - 2{\cdot}3 = -5$; $A^{-1} = (1/-5)(1 -2; -3 1)$, so $x = (8 - 2{\cdot}9)/(-5) = 2$, $y = (-24 + 9)/(-5) = 3$.

Substitution closes it: `2 + 2(3) = 8` ✓, `3(2) + 3 = 9` ✓. The **matrix inverse** route costs more arithmetic but verifies the elimination result with an independent method.

■ Scaling intuition for later courses

Nodal analysis IS `Ax = b`: `A` holds the conductances, `x` the node voltages, `b` the source currents. A well-posed circuit gives a non-singular `A`; a singular one means the modelling missed a ground or duplicated a source constraint – the determinant is a circuit-debugging tool, not just algebra.

2 Practice

2.1 Solve by elimination: $2x + y = 7$, $x - y = 2$. Verify by substitution. [3]

2.2 Compute the determinant of `(1 2; 3 1)` and use the inverse to solve $x + 2y = 8$, $3x + y = 9$. [4]

2.3 For which value of `k` is `(2 k; 4 6)` singular? Explain the geometric meaning in one sentence. [3]

3 Exam-style questions

3.1 A two-node circuit yields the system $3V_1 - V_2 = 12$, $-V_1 + 4V_2 = 0$ (conductances in siemens, currents in amps).

Solve for V_1 and V_2 by elimination, then verify by the determinant/inverse route. Finally compute the determinant of the coefficient matrix and state what it would mean for the circuit if it were zero. [7]

3.2 Mesh analysis of a two-loop network gives $5I_1 - 3I_2 = 12$ and $-3I_1 + 4I_2 = -6$.

Write the system in matrix form, compute the determinant, solve for both mesh currents, and check both original equations by substitution. State the physical meaning of $I_1 - I_2$. [6]